



UNIVERSITI TUNKU ABDUL RAHMAN
FACULTY OF INFORMATION & COMMUNICATION TECHNOLOGY
DEPARTMENT OF COMPUTER AND COMMUNICATION TECHNOLOGY

BACHELOR OF INFORMATION TECHNOLOGY (HONOURS)
COMPUTER ENGINEERING

YEAR TWO SEMESTER ONE

Session: 202502

UCCE2023 DIGITAL SYSTEMS DESIGN

PRACTICAL ASSIGNMENT:
Specifications

Instructor: Mok Kai Ming

Date of Submission: 16 May 2025

You are not allow to change the following grouping or sequence

| Group Members | Tutorial Group | Task (component) | Mobile Contact |
|-------------------------------|----------------|---|----------------|
| 1 Team work Cheah Lik Ding | 2 | Full Chip (Chip spec and verification) Hex keypad code generator, synchronizer | 011-59540693 |
| 2 Shu Mee Ang | 2 | ALU | 0175418434 |
| 3 Jayson Chen Min Xiang | 2 | Multiplier, Barrel shifter | 011-1141 9862 |
| 4 Chong Bing Hong | 2 | Storage + frequency generator Input / output converter | 010-9105719 |

Table of Content

| | |
|---|---|
| Table of Content | 1 |
| 1.Architecture Specification: Written Spec | 5 |
| 1.1 Functionality / Feature | 5 |
| 1.2 Operating Procedures and Application | 6 |
| 1.2.1 Examples of Application | 6 |
| 1.2.2 Operating Procedures (External Operations) | 6 |
| 1.3 Naming Convention | 8 |
| 1.4 Calculator Chip Interface and I/O Pin Description | 9 |
| 1.4.1 Calculator Interface | 9 |

| | |
|---|----|
| 1.4.2 I/O Pin Description | 9 |
| 1.4.3 Examples of Application (Include I/O Devices) in Block Diagram | 11 |
| 1.4.4 Timing Diagram for Handshaking / Communication with External Device | 11 |
| 1.5 Internal Operation | 12 |
| 1.5.1 Block Diagram with Information Flow | 12 |
| 1.5.2 Flowchart | 13 |
| 1.6 System Register | 14 |
| 2. Micro-Architecture Specification | 15 |
| 2.1 Design Hierarchy | 15 |
| 2.2 Block-level Functioning Partitioning | 15 |
| 2.3 Full chip verilog model | 16 |
| 3. Architecture Specification: Verification Specification | 19 |
| 3.1 Test Plan | 19 |
| 3.2 Testbench | 24 |
| 3.3 Test Simulation | 32 |
| 4 Micro-Architecture Specification (Block level) | 35 |
| 4.1 Synchronizer | 35 |
| 4.1.1 Functionality | 35 |
| 4.1.2 Features | 35 |
| 4.1.3 Block Interface | 36 |
| 4.1.4 I/O Pin Description | 36 |
| 4.1.5 Internal operational | 37 |
| 4.1.6 Timing Requirement | 38 |
| 4.1.7 Schematic | 39 |
| 4.1.9 Test Plan | 41 |
| 4.1.10 TestBench | 41 |
| 4.1.11 Test Result Timing Diagram | 43 |
| 4.2.1 Functionality | 44 |
| 4.2.2 Features | 44 |
| 4.2.3 Block Interface | 45 |
| 4.2.4 I/O Pin Description | 45 |
| 4.2.5 Internal operation | 46 |
| 4.2.6 Timing Requirement | 48 |
| 4.2.7 Schematic Predesign | 48 |
| 4.2.8 Vivado Model | 50 |
| 4.2.9 Test Plan | 54 |
| 4.2.10 TestBench | 55 |

| | |
|--|----|
| 4.2.11 Test Result Timing Diagram..... | 57 |
| 4.3.2 Features | 58 |
| 4.3.3 Block Interface..... | 59 |
| 4.3.4 I/O Pin Description | 59 |
| 4.3.5 Internal operation..... | 60 |
| 4.3.6 Timing Requirement | 61 |
| 4.3.7 Schematic..... | 61 |
| 4.3.8 Vivado Model | 61 |
| 4.3.9 Test Plan | 63 |
| 4.3.10 TestBench | 66 |
| 4.3.11 Result Simulation..... | 69 |
| 4.4 ALU | 70 |
| 4.4.1 Functionality | 70 |
| 4.4.2 Features | 71 |
| 4.4.3 Block Interface..... | 71 |
| 4.4.4 I/O Pin Description | 71 |
| 4.4.5 Internal operation..... | 72 |
| 4.4.6 Timing Requirement | 73 |
| 4.4.7 Schematic..... | 74 |
| 4.4.8 Vivado Model | 75 |
| 4.4.9 Test Plan | 77 |
| 4.4.10 TestBench | 80 |
| 4.5 Barrel Shifter..... | 85 |
| 4.5.1 Functionality | 85 |
| 4.5.2 Features | 85 |
| 4.5.3 Block Interface..... | 86 |
| 4.5.4 I/O Pin Description | 86 |
| 4.5.5 Internal Operation | 86 |
| 4.5.6 Timing Requirement | 87 |
| 4.5.7 Schematic..... | 88 |
| Postdesign | 88 |
| 4.5.9 Test Plan | 91 |
| 4.5.10 TestBench | 92 |
| 4.5.11 Test Result Timing Diagram..... | 96 |
| 4.6 Input / Output Conversion | 99 |
| 4.6.1 Functionality | 99 |
| 4.6.2 Features..... | 99 |

| | |
|--|-----|
| 4.6.3 Block Interface..... | 99 |
| 4.6.4 I/O Pin Description | 100 |
| 4.6.5 Internal operation | 101 |
| 4.6.6 Timing Requirement | 103 |
| 4.6.7 Schematic..... | 103 |
| 4.6.8 Vivado Model | 103 |
| 4.6.9 Test Plan | 106 |
| 4.6.10 TestBench | 108 |
| 4.6.11 Test Result Timing Diagram..... | 110 |

1.Architecture Specification: Written Spec

1.1 Functionality / Feature

Input Management:

- Uses hex keypad code generator and synchronizer to capture numeric digits and operation commands.
- Converts multi-digit hexadecimal inputs into an 8-bit binary number for processing.
- Support up to 255 digits.

8-Bit Integer Operations:

- Performs arithmetic operations (addition, subtraction, multiplication, division) on 8-bit numbers.
- Supports bitwise logic operations (AND, OR and XOR) on 8-bit operands.

Barrel Shifting:

- Implements left/right shift operations using a barrel shifter based on combinational logic

Output Conversion & Display:


- Converts computed binary results back into decimal digits for user display.
- Drives 7-segment displays to show both the input numbers and the results.

System Integration & Control:

- Coordinates the operation sequence among input, computation, and display modules.
- Provides clear and reset functions to start new calculations as needed.

1.2 Operating Procedures and Application

1.2.1 Examples of Application

 

1.2.2 Operating Procedures (External Operations)

1. A system clock, a system reset, a power line, and a ground line are supplied to the 8bit Integer Calculator.
2. The input devices including 2 hex keypad which are number buttons (for entering numbers) and system buttons (for Clear, Enter, and operation commands) as well as the output devices which is 7 segment displays.
3. To start the calculator, first power up the system by turning on the power switch.
4. If any previous input exists, press the Clear button to reset the calculator.
5. Key in the desired numeric values using the hex keypad and press the Enter button. The system captures these keycodes and converts the multi-digit number into an 8bit binary value.
6. Select the desired computation (addition, subtraction, multiplication, division, or bitwise/shift operations) by pressing the corresponding operation button and press the Enter button.

7. Key in the second desired numeric values using the hex keypad. Press the Enter button to initiate the computation. The operation will process the entered operands.
8. The computed binary result is then converted back into decimal digits and displayed on the 7segment display.
9. If a new calculation is desired, reset the system (using the Clear button) and repeat the input and operation selection process.
10. To continue with the result value, Press the enter Button and select the desired computation again.
11. To reinitialize the system at any point, press the Clear button; when finished, power off the system by turning off the power switch.

1.3 Naming Convention

<direction>_<level>_<module name>_<function><port size>

direction

| Name | <u>description</u> |
|------|--------------------|
| i | input |
| o | output |

level


| Name | description |
|--------|-------------|
| b | block |
| c | chip |
| system | system |

Module name

| Name | description |
|--------|---------------------------------------|
| SYN | synchronizer |
| hexpad | Hexadecimal keypad |
| CON | Data Flow Control and input Converter |
| ALU | arithmetic logic unit |
| BS | Barrier shifter |
| IOD | Input/output display |

1.4 Calculator Chip Interface and I/O Pin Description

1.4.1 Calculator Interface

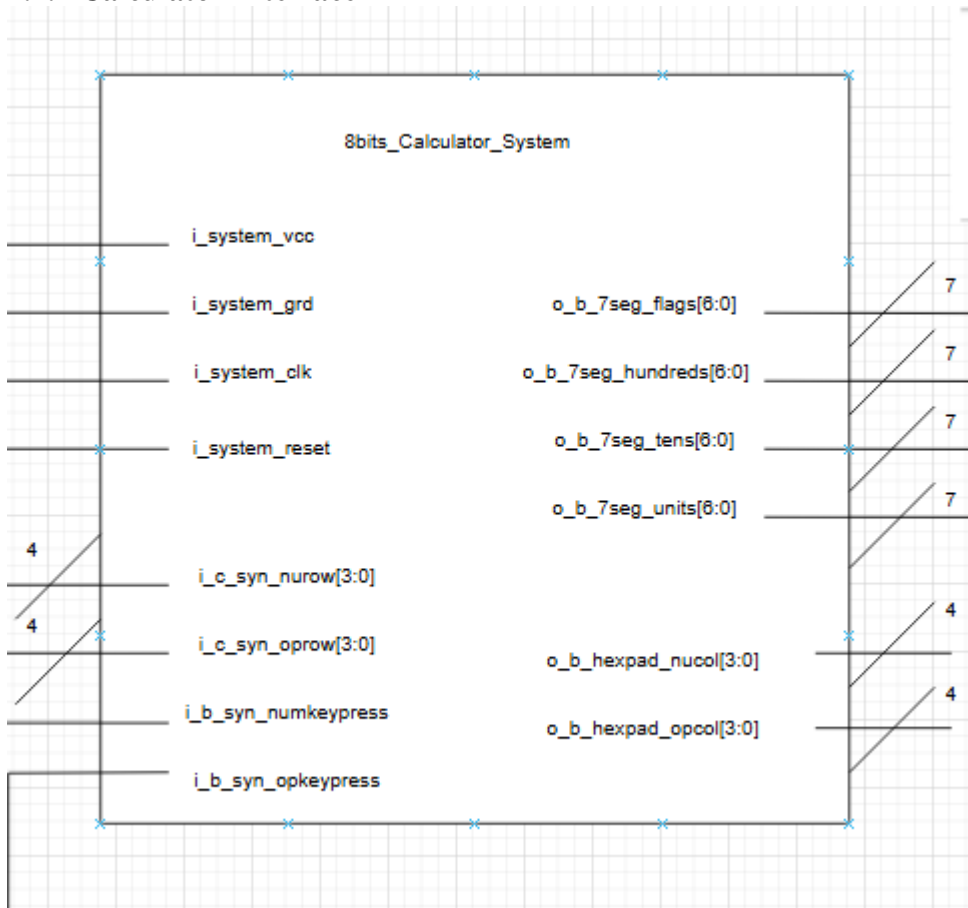


1.4.2 I/O Pin Description

Input Pins


| Pin Name | Pin Class | Pin direction | Source to direction | Pin Function |
|---------------------|-----------|---------------|----------------------------|---|
| i_system_reset | Global | input | Reset button to calculator | System reset signal to initialize the keypad interface. |
| i_system_clk | Global | input | System clock to calculator | Synchronize system with clock system |
| i_c_syn_nurow[3:0] | data | input | Keypad to calculator | Determine number's row number |
| i_c_syn_oprow[3:0] | data | input | Keypad to Calculator | Determine opcode's row number |
| i_b_syn_numkeypress | data | input | Keypad to Calculator | Record clock cycle of |

| | | | | |
|-----------------------------|------|--------|---------------------------------|---|
| | | | | opcode's row number |
| i_b_syn_opkeypress | data | input | Keypad to Calculator | Record clock cycle of opcode's row number |
| o_b_iod_7seg_flags [6:0] | data | output | Calculator to 7-segment display | Display the flags digit of 7-segment |
| o_b_iod_7Seg_hundreds [6:0] | data | output | Calculator to 7-segment display | Display the hundreds digit of 7-segment |
| o_b_iod_7Seg_tens [6:0] | data | output | Calculator to 7-segment display | Display the tens digit of 7-segment |
| o_b_iod_7Seg_units [6:0] | data | output | Calculator to 7-segment display | Display the units digit of 7-segment |
| o_b_hexpad_nucol [3:0] | data | output | Calculator to keypad | Scan number's row number |
| o_b_hexpad_nucol [3:0] | data | output | Calculator to keypad | Scan opcode's row number |

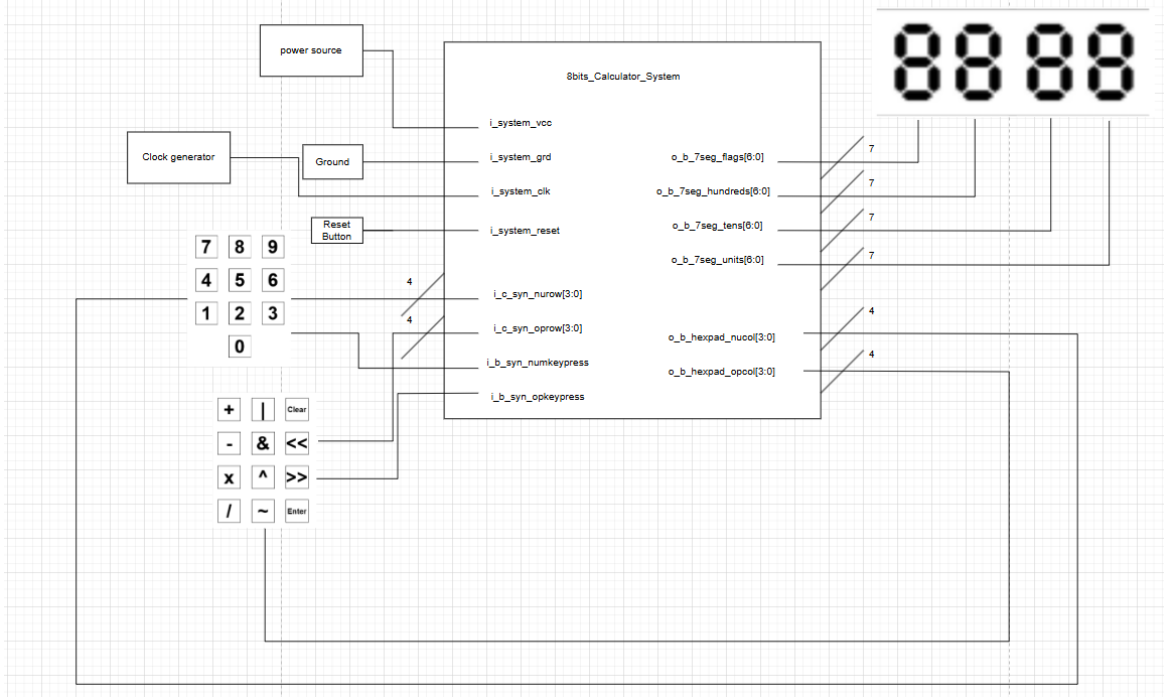1.4.3 Examples of Application (Include I/O Devices) in Block Diagram




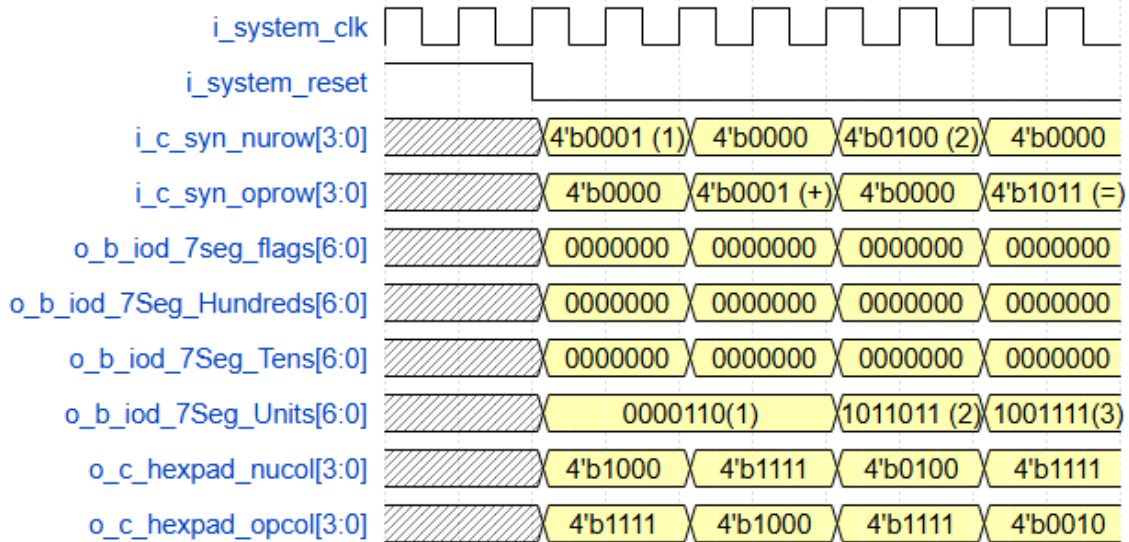1.4.4 Timing Diagram for Handshaking / Communication with External Device



1.5 Internal Operation

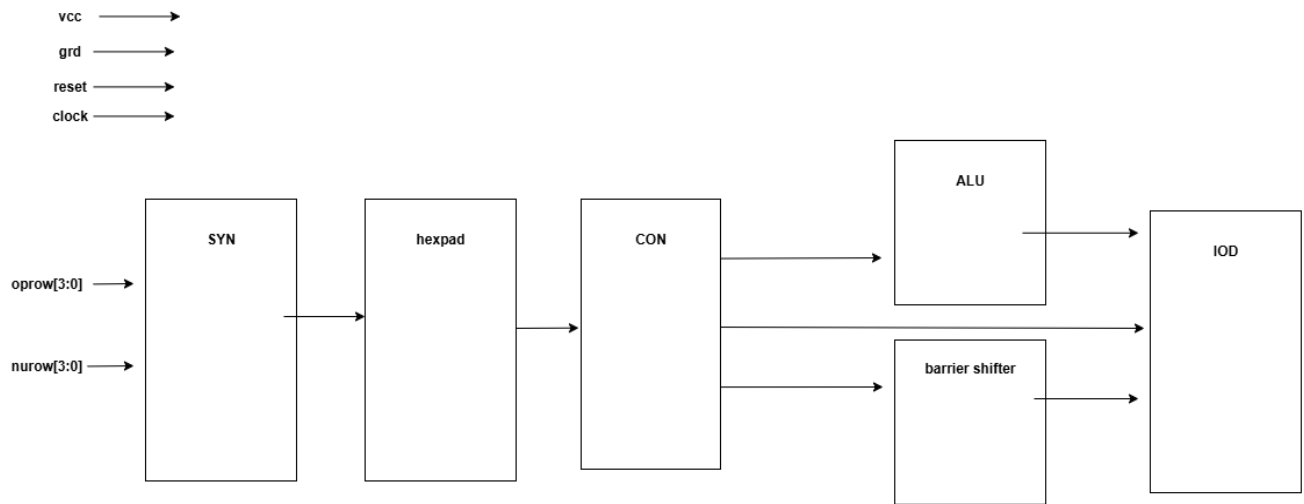1.5.1 Block Diagram with Information Flow



1.5.2 Flowchart



1.6 System Register


| Register | Width | Reset Value | Function |
|-----------------|--------|------------------|---|
| bcd_input_reg | 12-bit | 12'b000000000000 | Temporarily stores BCD digits entered via hexpad. bcd_input_reg[11:8]: 4'b0000 Hundreds place (Digit 2) bcd_input_reg[7:4]: 4'b0000 Tens place (Digit 1) bcd_input_reg[3:0]: 4'b0000 Units place (Digit 0) |
| operand_reg_a | 8-bit | 8'b00000000 | Stores the first 8-bit binary operand converted from bcd_input_reg. |
| operand_reg_b | 8-bit | 8'b00000000 | Stores the second 8-bit binary operand converted from bcd_input_reg. |
| opcode_reg | 4-bit | 4'b0000 | Stores the operation code |
| bcd_display_reg | 12-bit | 12'b000000000000 | Holds the BCD representation of result_reg for seven-segment display bcd_display_reg[11:8]: 4'b0000 Hundreds place (Digit 2) bcd_display_reg[7:4]: 4'b0000 Tens place (Digit 1) bcd_display_reg[3:0]: 4'b0000 Units place (Digit 0) |
| overflow_flag | 1-bit | 1'b0 | Indicates overflow input when operand >255 |

2. Micro-Architecture Specification

2.1 Design Hierarchy

| Chip Partitioning (Top Level) at System Level | Block and Sub-block Partitioning at MicroArchitecture Level |
|---|---|
| Calculator | Block Partitioning |
| | b_syn (for synchronization) |
| | b_hexpad (for get value and sent to next block) |
| | b_con (for convert the value form bcd to binary and sent to next block) |
| | b_ALU (for athematic computation) |
| | b_BS (for barrel shift computation) |
| | b_IOD (for display) |

2.2 Block-level Functioning Partitioning

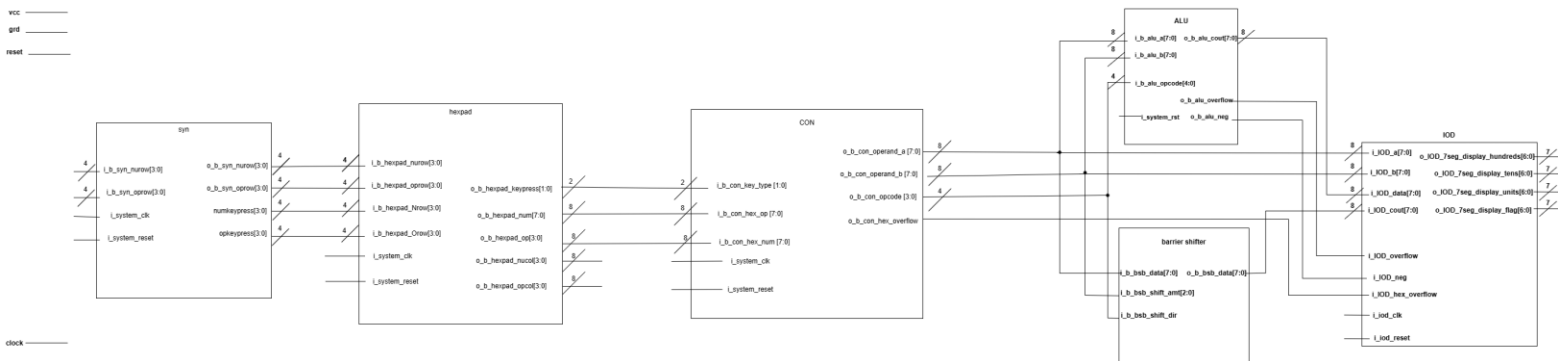

2.3 Full chip verilog model

```
module calculator;
// Clock and reset
logic clk;
logic reset;

// Inputs to syn module
logic [3:0] i_b_syn_nurow;
logic [3:0] i_b_syn_oprow;
logic i_b_syn_numkeypress;
logic i_b_syn_opkeypress;

// Outputs from syn module
logic [3:0] o_b_syn_nurow;
logic [3:0] o_b_syn_oprow;
logic o_b_syn_numkeypress;
logic o_b_syn_opkeypress;

// Outputs from hexpad module
logic [7:0] o_b_hexpad_num;
logic [3:0] o_b_hexpad_op;
logic [3:0] o_b_hexpad_nucol;
logic [3:0] o_b_hexpad_opCol;
logic [1:0] o_b_hexpad_keypress;

// Outputs from cub module
logic [3:0] o_b_con_opcode;
logic [7:0] o_b_con_a;
logic [7:0] o_b_con_b;
logic o_b_con_hex_overflow;

//Outputs from ALU
    logic [7:0] o_alu_out;
    logic o_neg;
    logic o_overflow;

//Outputs from BS
    logic[7:0] o_b_bs_data;

//Outputs from IOD

logic[6:0] o_b_iod_7seg_hundreds; logic[6:0] o_b_iod_7seg_tens; logic[6:0]
o_b_iod_7seg_units; logic[6:0] o_b_iod_7seg_flags;
// Instantiate syn module
syn u_syn (
    .i_system_clk(clk),
    .i_system_reset(reset),
    .i_b_syn_nurow(i_b_syn_nurow),
    .i_b_syn_oprow(i_b_syn_oprow),
    .i_b_syn_numkeypress(i_b_syn_numkeypress),
    .i_b_syn_opkeypress(i_b_syn_opkeypress),
```



```

.o_b_syn_nurow(o_b_syn_nurow),
.o_b_syn_oprow(o_b_syn_oprow),
.o_b_syn_numkeypress(o_b_syn_numkeypress),
.o_b_syn_opkeypress(o_b_syn_opkeypress)
);

```

// Instantiate hexpad module

```

hexpad u_hexpad (
.o_b_hexpad_num(o_b_hexpad_num),
.o_b_hexpad_op(o_b_hexpad_op),
.o_b_hexpad_nucol(o_b_hexpad_nucol),
.o_b_hexpad_opCol(o_b_hexpad_opCol),
.o_b_hexpad_keypress(o_b_hexpad_keypress),
.i_b_hexpad_nurow(o_b_syn_nurow),
.i_b_hexpad_oprow(o_b_syn_oprow),
.i_b_hexpad_Nrow(o_b_syn_numkeypress),
.i_b_hexpad_Orow(o_b_syn_opkeypress),
.i_system_clk(clk),
.i_system_reset(reset)
);

```

// Instantiate con module

```

con u_con (
.i_system_clock(clk),
.i_system_reset(reset),
.i_b_con_key_type(o_b_hexpad_keypress),
.i_b_con_hex_num(o_b_hexpad_num),
.i_b_con_hex_op(o_b_hexpad_op),
.o_b_con_opcode(o_b_con_opcode),
.o_b_con_a(o_b_con_a),
.o_b_con_b(o_b_con_b),
.o_b_con_hex_overflow(o_b_con_hex_overflow)
);

```

// Instantiate ALU module

```

ALU u_alu(
.i_operand_a(o_b_con_a),
.i_operand_b(o_b_con_b),
.i_opcode(o_b_con_opcode),
.i_system_rst(reset),
.o_alu_out(o_alu_out),
.o_neg(o_neg),
.o_overflow(o_overflow)
);

```

// Instantiate BS module

```

BS u_bs(
.i_b_bs_data(o_b_con_a),
.i_b_bs_shift_amt(o_b_con_b),
.i_b_bs_shift_dir(o_b_con_opcode),
.o_b_bs_data(o_b_bs_data)
);

```

// Instantiate IOD module

```

iod u_iod(
.i_system_clk(clk),
.i_system_reset(reset),
.i_b_iod_overflow(o_overflow),
.i_b_iod_neg(o_neg),
.i_b_iod_hex_overflow(o_b_con_hex_overflow),
.i_b_iod_a(o_b_con_a),
.i_b_iod_b(o_b_con_b),
.i_b_iod_data(o_b_bs_data),
.i_b_iod_cout(o_alu_out),
.i_b_iod_opcode(o_b_con_opcode),
.o_b_iod_7seg_hundreds(o_b_iod_7seg_hundreds), .o_b_iod_7seg_tens(o_b_iod_7s
eg_tens),
.o_b_iod_7seg_units(o_b_iod_7seg_units),
.o_b_iod_7seg_flags(o_b_iod_7seg_flags)
);

endmodule

```

3. Architecture Specification: Verification Specification

3.1 Test Plan

| No | Test Feature / Functionality | Test Vector Generator | Expected Outputs | Pass/ Fail |
|----|---------------------------------|---|---|---------------|
| 1 | Reset | <pre> clk = 0; reset = 1; i_b_syn_nurow = 4'b0000; i_b_syn_oprow = 4'b0000; i_b_syn_numkeypress = 0; i_b_syn_opkeypress = 0; #20; reset = 0; #20; </pre> | <pre> //Display '000' o_b_iod_7seg_hundreds[6:0]=0111111 o_b_iod_7seg_tens[6:0]=0111111 o_b_iod_7seg_units[6:0]= 0111111 o_b_iod_7seg_flags[6:0]=0000000 </pre> | Pass |
| 2 | Addition (63 + 36) | <pre> // Press '6' i_b_syn_numkeypress = 1; #20; i_b_syn_nurow = 4'b0010; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; // Press '3' i_b_syn_numkeypress = 1; #20; i_b_syn_nurow = 4'b0100; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; // Press '+' i_b_syn_opkeypress = 1; #40; i_b_syn_oprow = 4'b0001; #20; i_b_syn_oprow = 4'b0000; i_b_syn_opkeypress = 0; #20; // Press '3' i_b_syn_numkeypress = 1; #20; i_b_syn_nurow = 4'b0100; </pre> | <pre> //Display '099' o_b_iod_7seg_hundreds[6:0]=0111111 o_b_iod_7seg_tens[6:0]=1101111 o_b_iod_7seg_units[6:0]= 1101111 o_b_iod_7seg_flags[6:0]=0000000 </pre> | Pass |

| | | | | |
|---|--------------------------------------|---|---|------|
| | | <pre> #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; // Press '6' i_b_syn_numkeypress = 1; #20; i_b_syn_nurow = 4'b0010; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; //press '=' i_b_syn_opkeypress = 1; #20; i_b_syn_oprow = 4'b1000; #20; i_b_syn_oprow = 4'b0000; i_b_syn_opkeypress = 0; #20; </pre> | | |
| 3 | Barrel Shift (6<<3) | <pre> // Press '6' i_b_syn_numkeypress = 1; #20; i_b_syn_nurow = 4'b0010; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; // Press '<<' i_b_syn_opkeypress = 1; #20; i_b_syn_oprow = 4'b0010; #20; i_b_syn_oprow = 4'b0000; i_b_syn_opkeypress = 0; #20; // Press '3' i_b_syn_numkeypress = 1; #20; i_b_syn_nurow = 4'b0100; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; </pre> | <pre> //Display '048' o_b_iod_7seg_hundreds[6:0]=0111111 o_b_iod_7seg_tens[6:0]=1100110 o_b_iod_7seg_units[6:0]= 1111111 o_b_iod_7seg_flags[6:0]=0000000 </pre> | pass |

| | | | | |
|---|--|---|--|------|
| | | <pre>//press '=' i_b_syn_opkeypress = 1; #20; i_b_syn_oprow = 4'b1000; #20; i_b_syn_oprow = 4'b0000; i_b_syn_opkeypress = 0; #20;</pre> | | |
| 4 | Multiplication (105 * 3) Overflow | <pre>// Press '1' i_b_syn_numkeypress = 1; #40; i_b_syn_nurow = 4'b0100; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; //Press '0' i_b_syn_numkeypress = 1; #30; i_b_syn_nurow = 4'b1000; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; // Press '5' i_b_syn_numkeypress = 1; #30; i_b_syn_nurow = 4'b0010; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; // Press '*' i_b_syn_opkeypress = 1; #40; i_b_syn_oprow = 4'b0100; #20; i_b_syn_oprow = 4'b0000; i_b_syn_opkeypress = 0; #20; // Press '3' i_b_syn_numkeypress = 1; #20; i_b_syn_nurow = 4'b0100;</pre> | <p>Display 'E' at the Last Digit of 7 Segment</p> <p>o_b_iod_7seg_flags[6:0]=1111001</p> | pass |

| | | | | |
|---|---|--|--|------|
| | | <pre> #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; // Press '=' i_b_syn_opkeypress = 1; #20; i_b_syn_oprow = 4'b1000; #20; i_b_syn_oprow = 4'b0000; i_b_syn_opkeypress = 0; #20; </pre> | | |
| 5 | Substraction (15-30) Negative Flag | <pre> // Press '1' i_b_syn_numkeypress = 1; #40; i_b_syn_nurow = 4'b0100; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; // Press '5' i_b_syn_numkeypress = 1; #30; i_b_syn_nurow = 4'b0010; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; // Press '-' i_b_syn_opkeypress = 1; #40; i_b_syn_oprow = 4'b0010; #20; i_b_syn_oprow = 4'b0000; i_b_syn_opkeypress = 0; #20; // Press '3' i_b_syn_numkeypress = 1; #20; i_b_syn_nurow = 4'b0100; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; //Press '0' </pre> | Display '-' at the Last Digit of 7 Segment o_b_iod_7seg_flags[6: 0]=1000000 | pass |

| | | | | |
|--|--|--|--|--|
| | | <pre> i_b_syn_numkeypress = 1; #30; i_b_syn_nurow = 4'b1000; #20; i_b_syn_nurow = 4'b0000; i_b_syn_numkeypress = 0; #20; // Press '=' i_b_syn_opkeypress = 1; #20; i_b_syn_oprow = 4'b1000; #20; i_b_syn_oprow = 4'b0000; i_b_syn_opkeypress = 0; #20; </pre> | | |
|--|--|--|--|--|

3.2 Testbench

```
`timescale 1ns / 1ps

module calculator;

// Clock and reset
logic clk;
logic reset;

// Inputs to syn module
logic [3:0] i_b_syn_nurow;
logic [3:0] i_b_syn_oprow;
logic i_b_syn_numkeypress;
logic i_b_syn_opkeypress;

// Outputs from syn module
logic [3:0] o_b_syn_nurow;
logic [3:0] o_b_syn_oprow;
logic o_b_syn_numkeypress;
logic o_b_syn_opkeypress;

// Outputs from hexpad module
logic [7:0] o_b_hexpad_num;
logic [3:0] o_b_hexpad_op;
logic [3:0] o_b_hexpad_nucol;
logic [3:0] o_b_hexpad_opCol;
logic [1:0] o_b_hexpad_keypress;

// Outputs from con module
logic [3:0] o_b_con_opcode;
logic [7:0] o_b_con_a;
logic [7:0] o_b_con_b;
logic o_b_con_hex_overflow;

//Outputs from ALU
    logic [7:0] o_alu_out;
    logic o_neg;
    logic o_overflow;

//Outputs from BS
    logic[7:0] o_b_bs_data;

//Outputs from IOD

logic[6:0] o_b_iod_7seg_hundreds;

logic[6:0] o_b_iod_7seg_tens;

logic[6:0] o_b_iod_7seg_units;

logic[6:0] o_b_iod_7seg_flags;
```



```
// Instantiate syn module
syn u_syn (
    .i_system_clk(clk),
    .i_system_reset(reset),
    .i_b_syn_nurow(i_b_syn_nurow),
    .i_b_syn_oprow(i_b_syn_oprow),
    .i_b_syn_numkeypress(i_b_syn_numkeypress),
    .i_b_syn_opkeypress(i_b_syn_opkeypress),
    .o_b_syn_nurow(o_b_syn_nurow),
    .o_b_syn_oprow(o_b_syn_oprow),
    .o_b_syn_numkeypress(o_b_syn_numkeypress),
    .o_b_syn_opkeypress(o_b_syn_opkeypress)
);
```

```
// Instantiate hexpad module
hexpad u_hexpad (
    .o_b_hexpad_num(o_b_hexpad_num),
    .o_b_hexpad_op(o_b_hexpad_op),
    .o_b_hexpad_nucol(o_b_hexpad_nucol),
    .o_b_hexpad_opCol(o_b_hexpad_opCol),
    .o_b_hexpad_keypress(o_b_hexpad_keypress),
    .i_b_hexpad_nurow(o_b_syn_nurow),
    .i_b_hexpad_oprow(o_b_syn_oprow),
    .i_b_hexpad_Nrow(o_b_syn_numkeypress),
    .i_b_hexpad_Orow(o_b_syn_opkeypress),
    .i_system_clk(clk),
    .i_system_reset(reset)
);
```

```
// Instantiate con module
con u_con (
    .i_system_clock(clk),
    .i_system_reset(reset),
    .i_b_con_key_type(o_b_hexpad_keypress),
    .i_b_con_hex_num(o_b_hexpad_num),
    .i_b_con_hex_op(o_b_hexpad_op),
    .o_b_con_opcode(o_b_con_opcode),
    .o_b_con_a(o_b_con_a),
    .o_b_con_b(o_b_con_b),
    .o_b_con_hex_overflow(o_b_con_hex_overflow)
);
```

```
// Instantiate ALU module
ALU u_alu(
    .i_operand_a(o_b_con_a),
    .i_operand_b(o_b_con_b),
    .i_opcode(o_b_con_opcode),
    .i_system_rst(reset),
    .o_alu_out(o_alu_out),
    .o_neg(o_neg),
    .o_overflow(o_overflow)
);
```

```
// Instantiate BS module
```

```
BS u_bs(
```

```

.i_b_bs_data(o_b_con_a),
.i_b_bs_shift_amt(o_b_con_b),
.i_b_bs_shift_dir(o_b_con_opcode),
.o_b_bs_data(o_b_bs_data)
);
// Instantiate IOD module
iod u_iod(
.i_system_clk(clk),
.i_system_reset(reset),
.i_b_iod_overflow(o_overflow),
.i_b_iod_neg(o_neg),
.i_b_iod_hex_overflow(o_b_con_hex_overflow),
.i_b_iod_a(o_b_con_a),
.i_b_iod_b(o_b_con_b),
.i_b_iod_data(o_b_bs_data),
.i_b_iod_cout(o_alu_out),
.i_b_iod_opcode(o_b_con_opcode),
.o_b_iod_7seg_hundreds(o_b_iod_7seg_hundreds),
.o_b_iod_7seg_tens(o_b_iod_7seg_tens), .o_b_iod_7seg_units(o_b_iod_7seg_units)
, .o_b_iod_7seg_flags(o_b_iod_7seg_flags)
);
// Clock generation
always begin #5 clk = ~clk;
end
// Test 1 sequence
initial begin
clk = 0;
reset = 1;
i_b_syn_nurow = 4'b0000;
i_b_syn_oprow = 4'b0000;
i_b_syn_numkeypress = 0;
i_b_syn_opkeypress = 0;
#20;
reset = 0;

```

```

#20;

//Test 2 (63+36)=99
// Simulate number key press
i_b_syn_numkeypress = 1;
// activate number scanning
#20;
i_b_syn_nurow = 4'b0010;
// simulate key press (e.g., '6')
#20; i_b_syn_nurow = 4'b0000;
i_b_syn_numkeypress = 0;
// release key
#20;
// Simulate number key press
i_b_syn_numkeypress = 1;
// activate number scanning
#20; i_b_syn_nurow = 4'b0100;
// simulate key press (e.g., '3')
#20;
i_b_syn_nurow = 4'b0000;
i_b_syn_numkeypress = 0;
// release key
#20;

// Simulate operator '+' press
i_b_syn_opkeypress = 1;
#40;
i_b_syn_oprow = 4'b0001; // simulate '+' press
#20;
i_b_syn_oprow = 4'b0000;
i_b_syn_opkeypress = 0;
#20;

// Simulate number key press
i_b_syn_numkeypress = 1; // activate number scanning
#20;

```

```

i_b_syn_nurow = 4'b0100; // simulate key press (e.g., '3')
#20;
i_b_syn_nurow = 4'b0000;
i_b_syn_numkeypress = 0; // release key
#20;
// Simulate number key press
i_b_syn_numkeypress = 1; // activate number scanning
#20;
i_b_syn_nurow = 4'b0010; // simulate key press (e.g., '6')
#20;
i_b_syn_nurow = 4'b0000;
i_b_syn_numkeypress = 0; // release key
#20;

// Simulate another operator press (e.g., '=')
i_b_syn_opkeypress = 1;
#20;
i_b_syn_oprow = 4'b1000; // simulate '=' press
#20;
i_b_syn_oprow = 4'b0000;
i_b_syn_opkeypress = 0;
#20;

//test 3 (6<<3=48)

// Simulate number key press
i_b_syn_numkeypress = 1;

// activate number scanning
#20;

i_b_syn_nurow = 4'b0010;

// simulate key press (e.g., '6')
#20;

i_b_syn_nurow = 4'b0000;

i_b_syn_numkeypress = 0;

// release key
#20;

// Simulate operator press (e.g., '<<')
i_b_syn_opkeypress = 1;
#20;
i_b_syn_oprow = 4'b0010; // simulate '<<' press
#20;
i_b_syn_oprow = 4'b0000;
i_b_syn_opkeypress = 0;
#20;

```

```

// Simulate number key press
i_b_syn_numkeypress = 1; // activate number scanning
#20;
i_b_syn_nurow = 4'b0100; // simulate key press (e.g., '3')
#20;
i_b_syn_nurow = 4'b0000;
i_b_syn_numkeypress = 0; // release key
#20;

// Simulate another operator press (e.g., '=')
i_b_syn_opkeypress = 1;
#20;
i_b_syn_oprow = 4'b1000; // simulate '=' press
#20;
i_b_syn_oprow = 4'b0000;
i_b_syn_opkeypress = 0;
#20;

//test 4 (105*3=315,overflow)

// Simulate number key press

i_b_syn_numkeypress = 1; // activate number scanning

#40;

i_b_syn_nurow = 4'b0100;

// simulate key press (e.g., '1')

#20;

i_b_syn_nurow = 4'b0000;

i_b_syn_numkeypress = 0; // release key #20;

// Simulate number key press
i_b_syn_numkeypress = 1; // activate number scanning
#30;
i_b_syn_nurow = 4'b1000; // simulate key press (e.g., '0')
#20;
i_b_syn_nurow = 4'b0000;
i_b_syn_numkeypress = 0; // release key
#20;
// Simulate number key press
i_b_syn_numkeypress = 1; // activate number scanning
#30;
i_b_syn_nurow = 4'b0010; // simulate key press (e.g., '5')
#20;
i_b_syn_nurow = 4'b0000;
i_b_syn_numkeypress = 0; // release key
#20;

```

```

// Simulate operator press (e.g., '*')
i_b_syn_opkeypress = 1;
#40;
i_b_syn_oprow = 4'b0100; // simulate '*' press
#20;
i_b_syn_oprow = 4'b0000;
i_b_syn_opkeypress = 0;
#20;

// Simulate number key press
i_b_syn_numkeypress = 1; // activate number scanning
#20;
i_b_syn_nurow = 4'b0100; // simulate key press (e.g., '3')
#20;
i_b_syn_nurow = 4'b0000;
i_b_syn_numkeypress = 0; // release key
#20;

// Simulate another operator press (e.g., '=')
i_b_syn_opkeypress = 1;
#20;
i_b_syn_oprow = 4'b1000; // simulate '=' press
#20;
i_b_syn_oprow = 4'b0000;
i_b_syn_opkeypress = 0;
#20;
// End simulation
#100;

//test 5 (15-30=-15,negative flag) // Simulate number key press
i_b_syn_numkeypress = 1; // activate number scanning

#40;

i_b_syn_nurow = 4'b0100; // simulate key press (e.g., '1')

#20;

i_b_syn_nurow = 4'b0000;

i_b_syn_numkeypress = 0; // release key

#20;

// Simulate number key press
i_b_syn_numkeypress = 1; // activate number scanning
#30;
i_b_syn_nurow = 4'b0010; // simulate key press (e.g., '5')
#20;
i_b_syn_nurow = 4'b0000;
i_b_syn_numkeypress = 0; // release key
#20;

// Simulate another operator press (e.g., '-')

```

```

i_b_syn_opkeypress = 1;
#40;
i_b_syn_oprow = 4'b0010; // simulate '*' press
#20;
i_b_syn_oprow = 4'b0000;
i_b_syn_opkeypress = 0;
#20;

// Simulate number key press
i_b_syn_numkeypress = 1; // activate number scanning
#20;
i_b_syn_nurow = 4'b0100; // simulate key press (e.g., '3')
#20;
i_b_syn_nurow = 4'b0000;
i_b_syn_numkeypress = 0; // release key
#20;

// Simulate number key press
i_b_syn_numkeypress = 1; // activate number scanning
#30;
i_b_syn_nurow = 4'b1000; // simulate key press (e.g., '0')
#20;
i_b_syn_nurow = 4'b0000;
i_b_syn_numkeypress = 0; // release key
#20;


// Simulate another operator press (e.g., '=')
i_b_syn_opkeypress = 1;
#20;
i_b_syn_oprow = 4'b1000; // simulate '=' press
#20;
i_b_syn_oprow = 4'b0000;
i_b_syn_opkeypress = 0;
#20;
// End simulation
#100;
$finish;
end

endmodule


```

3.3 Test Simulation


// Test 1 sequence

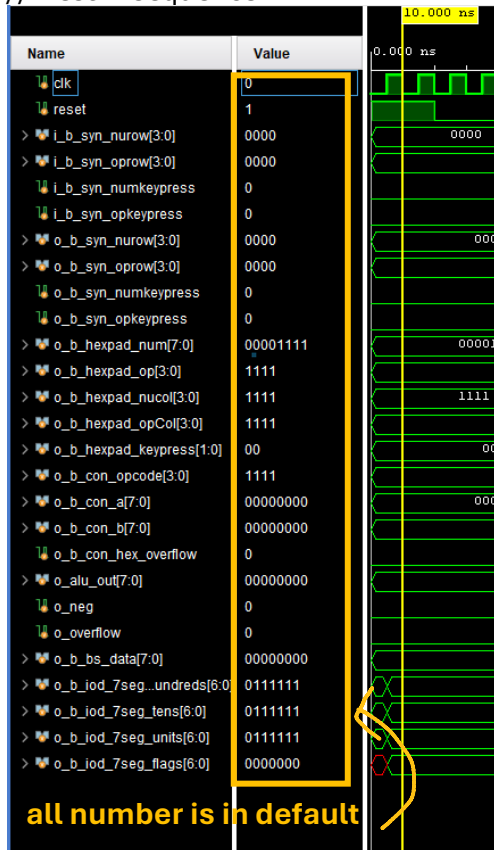


//Test 2 (63+36)=99

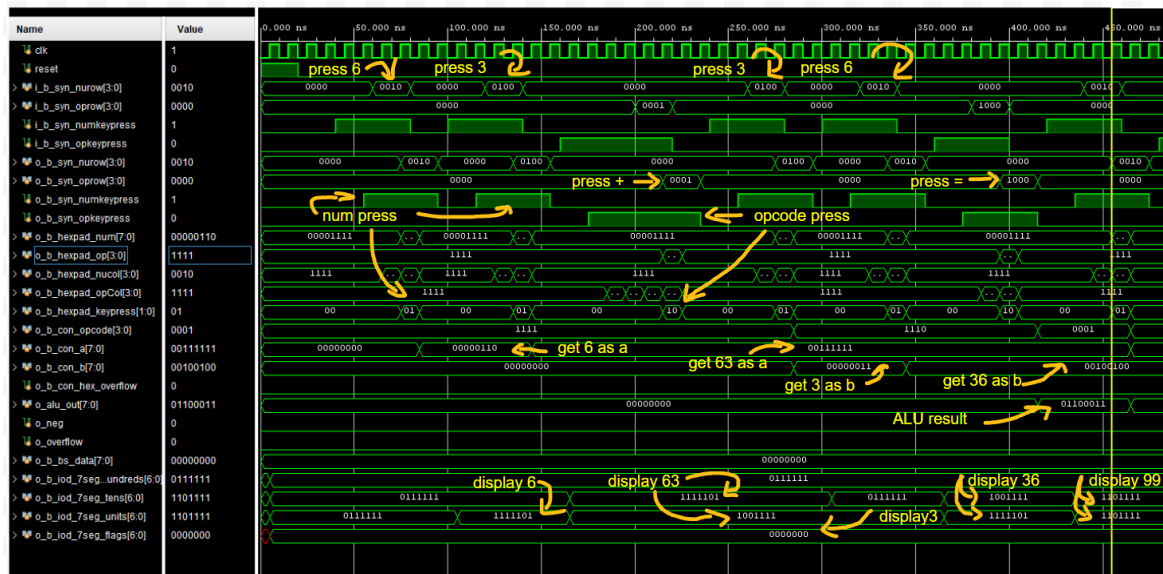


//test 3 ($6 < 3 = 48$)

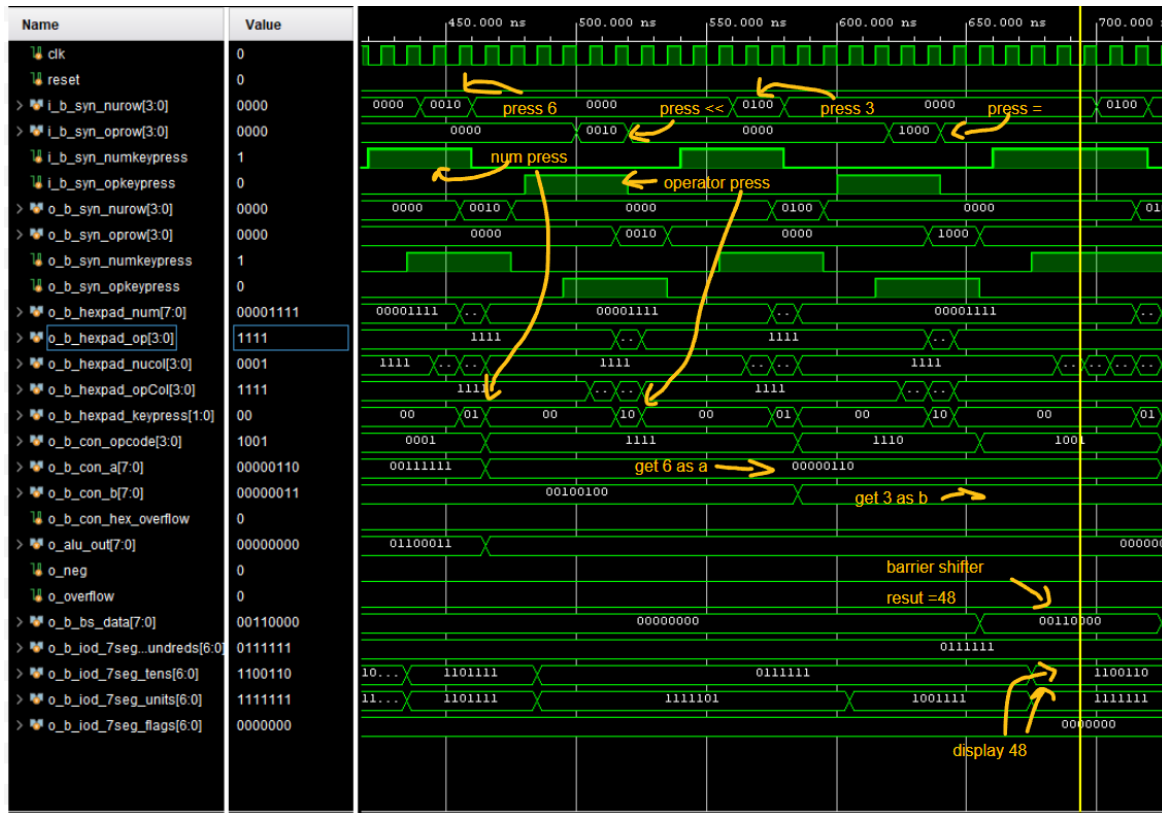

//test 4 ($105 * 3 = 315$, overflow)

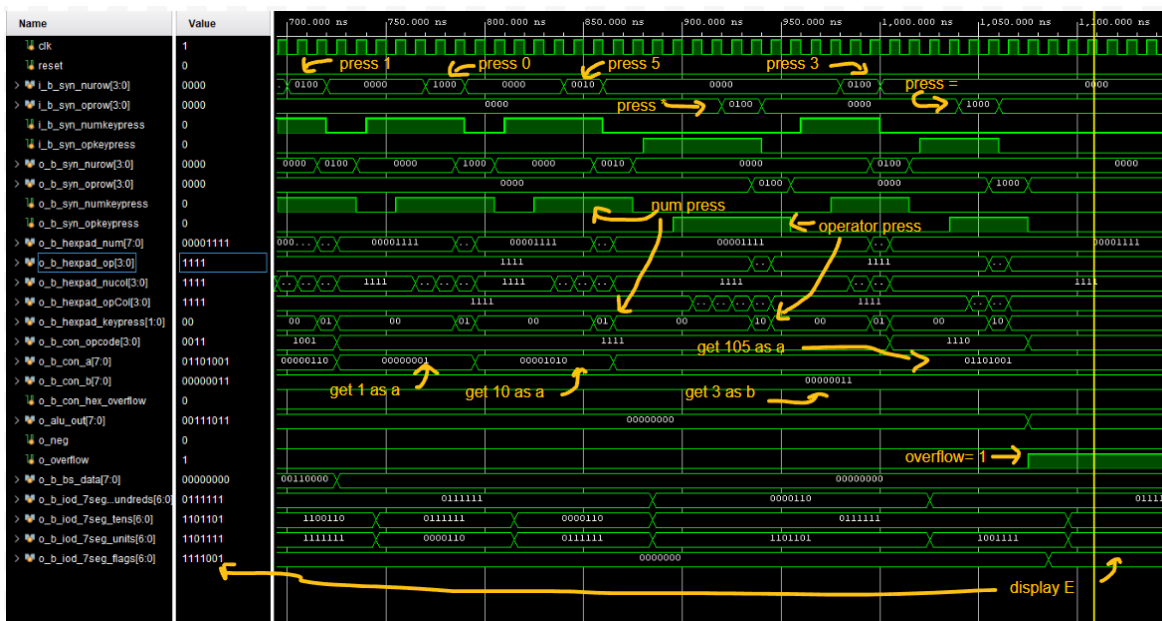

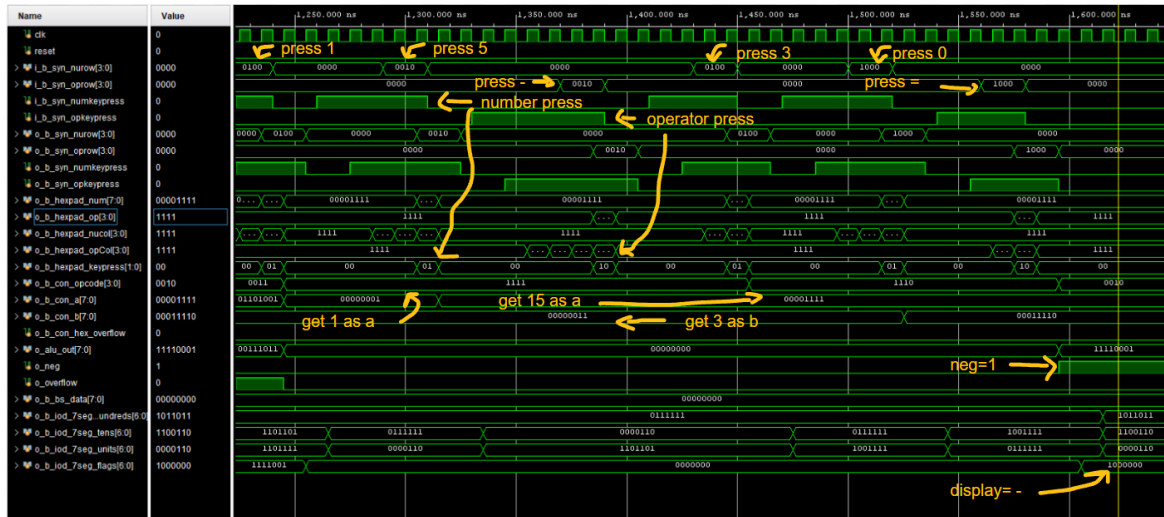//test 5 ($15 - 30 = -15$, negative flag) // Simulate number key press



4 Micro-Architecture Specification (Block level)

4.1 Synchronizer

4.1.1 Functionality

- The **SYN Module** is designed to synchronize asynchronous row signals from a keypad matrix to the system clock domain. The module uses multiple flip-flops to sample and stabilize the asynchronous input signals. It prevents metastability by ensuring that only stable signals are passed to the system, providing reliable data synchronization for key scanning operations.
- The **i_b_syn_nurow[3:0]** , **i_b_syn_oprow[3:0]** ,**i_b_syn_numkeypress** and **i_b_syn_opkeypress** signals are used to input the row signals of the keypad matrix during the scanning process. These signals are active when scanning different rows of the matrix.
- The **i_system_reset** signal initializes the synchronization process, ensuring that all internal states are cleared before synchronization begins. This helps prevent erroneous data during the initial stage of synchronization.
- The **i_b_syn_nurow[3:0]** , **i_b_syn_oprow[3:0]** ,**i_b_syn_numkeypress** and **i_b_syn_opkeypress** are the synchronized row signals that represent the stabilized rows of the keypad matrix, ensuring that the matrix rows are correctly identified and processed by the system clock.
- The **i_system_clk** signal is used as the system clock to synchronize the asynchronous input signals. All synchronization actions are aligned to the rising edge of this clock signal.

4.1.2 Features

Asynchronous Signal Synchronization:

The **SYN Module** synchronizes asynchronous row signals from the keypad matrix (**o_b_syn_nurow[3:0]**, **o_b_syn_oprow[3:0]**) to the system clock (**i_system_clk**), ensuring that all key scanning operations are synchronized.

Keypad Scanning Support:

The module supports keypad scanning by taking input row signals (**o_b_syn_nurow[3:0]**, **o_b_syn_oprow[3:0]**, **i_b_syn_numkeypress**, **i_b_syn_opkeypress**) from the keypad matrix. It processes these signals and outputs synchronized row signals (**o_b_syn_nurow[3:0]**, **o_b_syn_oprow[3:0]**, **i_b_syn_numkeypress**, **i_b_syn_opkeypress**).

Metastability Prevention:

The module prevents metastability by synchronizing the incoming asynchronous signals and ensuring that only stable signals are passed to the output. The **i_reset** signal clears the synchronization process if needed to maintain reliability.


System Clock Synchronization:

The **i_system_clk** system clock ensures that the synchronization process occurs at the correct time, with all asynchronous inputs being synchronized to this clock domain.

Initialization with Reset:

The **i_system_reset** signal ensures that the synchronization process is initialized correctly, clearing any previous states and avoiding spurious data.

4.1.3 Block Interface

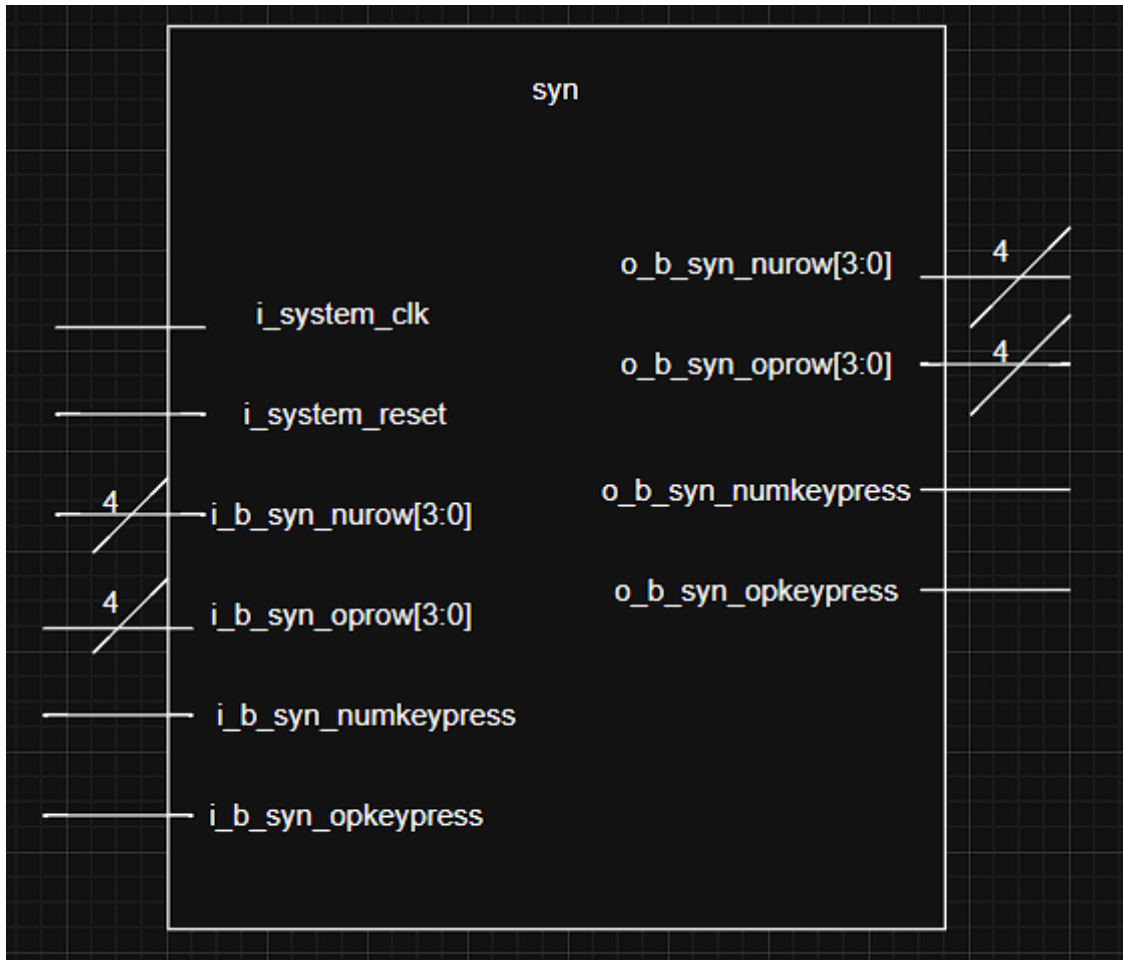

4.1.4 I/O Pin Description

| Pin Name | Pin Class | Pin Direction | Source to direction | Pin Function |
|-----------------------------------|----------------|---------------|------------------------------|---|
| <code>i_system_clock</code> | Control | Input | System Clock to syn | Clock signal to synchronize input signals |
| <code>i_system_reset</code> | Control | Input | Reser b button to SYN | Asynchronous reset for internal registers |
| <code>i_b_syn_nurow [3:0]</code> | Data | Input | Keypad (number row) to SYN | Raw row data from numeric keypad |
| <code>i_b_syn_oprow [3:0]</code> | Data | Input | Keypad (operator row) to SYN | Raw row data from operator keypad |
| <code>i_b_syn_numkeypr ess</code> | Status/Control | Input | hexpad module to SYN | Signal indicating numeric key was pressed |

| | | | | |
|-------------------------|--------------------|--------|-------------------------|---|
| i_b_syn_opkeypres | Status/ Control | Input | hexpad module to SYN | Signal indicating opcode key was pressed |
| o_b_syn_nurow [3:0] | Data | Output | SYN to hexpad | Synchronized numeric keypad row output |
| o_b_syn_oprow [3:0] | Data | Output | SYN to hexpad | Synchronized operator keypad row output |
| o_b_syn_numkeypr ess | Status/ Control | Output | SYN to cub or FSM | Synchronized numeric key press status |
| o_b_syn_opkeypres | Status/ Control | Output | SYN → cub or FSM | Synchronized operator key press status |


4.1.5 Internal operational

| Clock signal (ip_sys_clk) | Input | Output | Synchronizer Function Description |
|------------------------------|-------|--------|--|
| 0 → 1 (↑ rising edge) | 0 | 0 | Latches active-low key input as ‘pressed’ without uncertain state |
| 0 → 1 (↑ rising edge) | 1 | 1 | Latches active-low key input as ‘not pressed’ without issues |
| 0 → 1 (↑ rising edge) | X | X | Maintains undefined input if unstable |
| 0 → 1 (↑ rising edge) | Z | Z | Handles high-impedance state as-is |
| 1 → 0 (↓ falling edge) | Qn | Qn-1 | No operation; output remains latched on rising edge only |

| Clock Signal (i_clk) | Input stable for 8 Cycle | Output (o_b_syn_*) |
|---------------------------|-----------------------------------|---------------------------|
| 0 → 1 (↑ rising edge) | Yes | Updated with new value |
| 0 → 1 (↑ rising edge) | No | Previous value held |
| 1 → 0 (↓ falling edge) | N/A | No change |


4.1.6 Timing Requirement

Synchronizer timing diagram

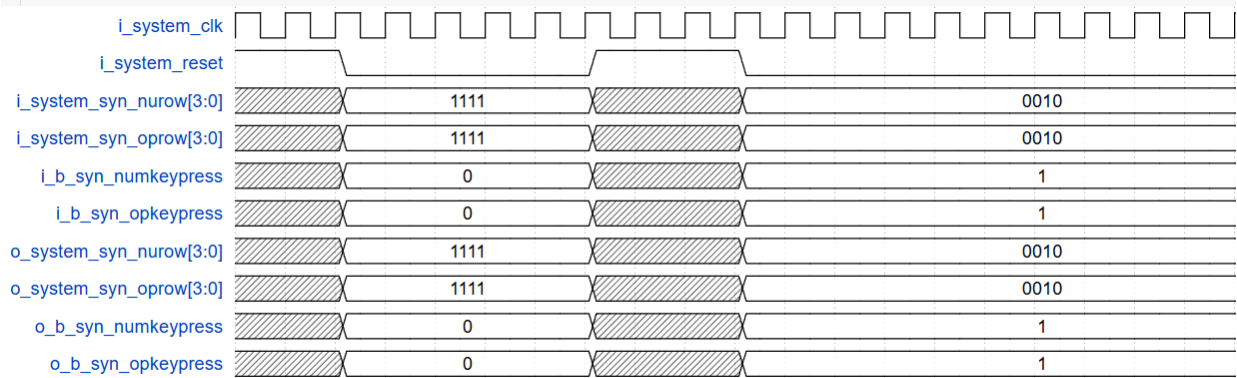


4.1.7 Schematic

Predesign

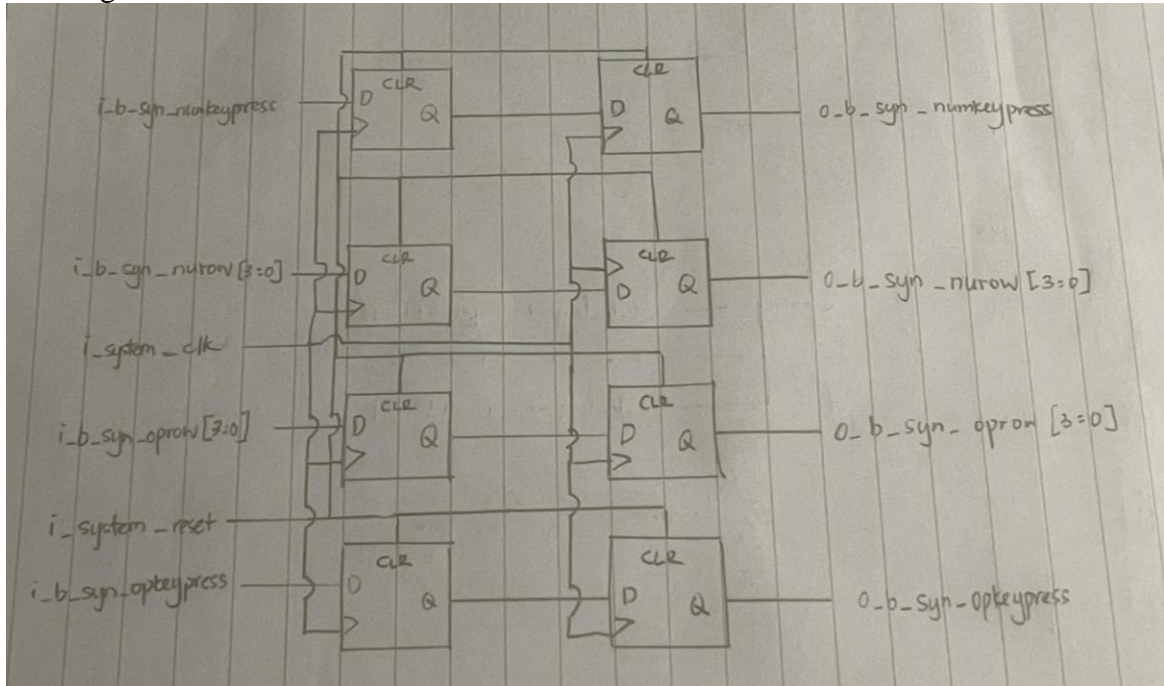

Postdesign

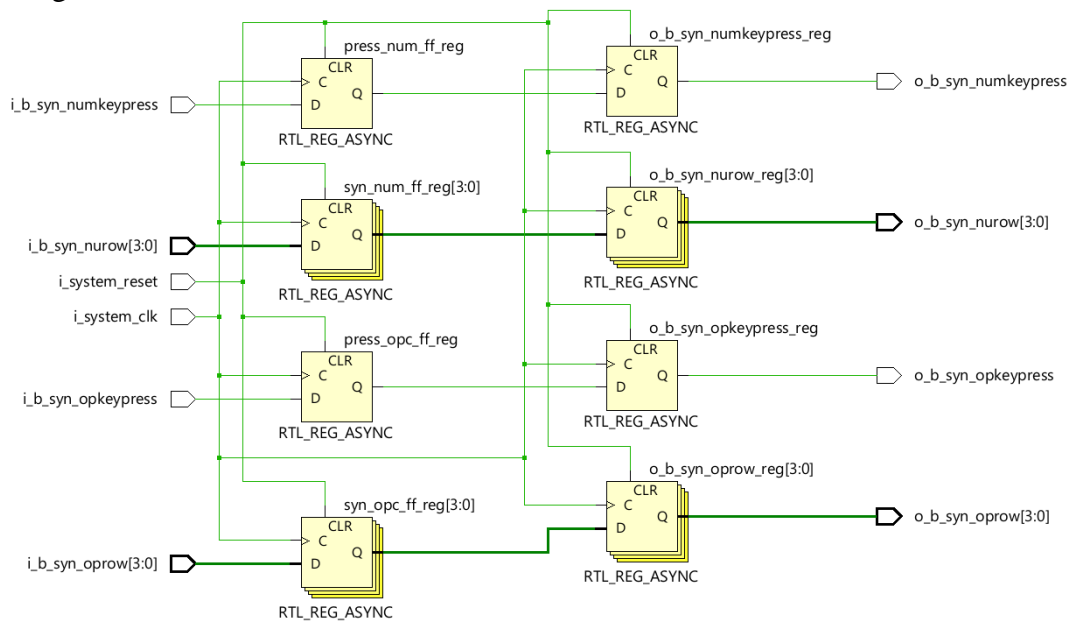

4.1.8 Vivado Model

```
/////////////////////////////////////////////////////////////////
// Company: UTAR
// Engineer: Cheah Lik Ding
// Create Date: 05/05/2025
// Module Name: syn
// Project Name: syn
/////////////////////////////////////////////////////////////////

module SYN(
input i_system_clk,
input i_system_reset,
input [3:0] i_b_syn_nurow,
input [3:0] i_b_syn_oprow,
input logic i_b_syn_numkeypress,
input logic i_b_syn_opkeypress,
output logic [3:0] o_b_syn_nurow,
output logic [3:0] o_b_syn_oprow,
output logic o_b_syn_numkeypress,
output logic o_b_syn_opkeypress

);

logic [3:0] syn_num_ff;
logic [3:0] syn_opc_ff;
logic press_num_ff;
logic press_opc_ff;

always_ff @(posedge i_system_clk or posedge i_system_reset) begin
    if (i_system_reset) begin
        syn_num_ff <= 4'b0000;
        syn_opc_ff <= 4'b0000;
        press_num_ff <= 0;
        press_opc_ff <= 0;
        o_b_syn_nurow <= 4'b0000;
        o_b_syn_oprow <= 4'b0000;
        o_b_syn_numkeypress <=0;
        o_b_syn_opkeypress <=0;

    end else begin
        syn_num_ff <= i_b_syn_nurow;
        syn_opc_ff <= i_b_syn_oprow;
        o_b_syn_nurow <= syn_num_ff;
        o_b_syn_oprow <= syn_opc_ff;
        press_num_ff<=i_b_syn_numkeypress;
        press_opc_ff<=i_b_syn_opkeypress;
        o_b_syn_numkeypress<= press_num_ff;
        o_b_syn_opkeypress<= press_opc_ff;
    end
end

endmodule
```


4.1.9 Test Plan

| No. | Test Feature | Test Vector | Expected Outputs | Pass / Fail |
|-----|------------------------------------|---|---|-------------|
| 1 | System Reset | reset= 1 | o_b_syn_nurow = 4'b0000 o_b_syn_oprow = 4'b0000 o_b_syn_numkeypress = 1'b0 o_b_syn_opkeypress = 1'b0 | pass |
| 2 | Valid Key Press (Debounced) | i_b_syn_nurow = 4'b1010; i_b_syn_oprow = 4'b1010; #100; | o_b_syn_nurow = 4'b1010 o_b_syn_oprow = 4'b1010 o_b_syn_numkeypress = 1'b1 o_b_syn_opkeypress = 1'b1 | pass |
| 3 | Unstable Input (Debounced Fail) | i_b_syn_nurow = 4'b1100; #5; | o_b_syn_nurow = 4'b1111; o_b_syn_oprow = 4'b1111; | pass |

4.1.10 TestBench

```

////////////////////////////////////
// Company: UTAR
// Engineer: Cheah Lik Ding
// Create Date: 05/05/2025
// Module Name: tb_syn
// Project Name: tb_syn
////////////////////////////////////
module tb_syn;
// Inputs
logic clk;
logic rst;
logic [3:0] i_b_syn_nurow;
logic [3:0] i_b_syn_oprow;
logic i_b_syn_numkeypress;
logic i_b_syn_opkeypress;

// Outputs
logic [3:0] o_b_syn_nurow;
logic [3:0] o_b_syn_oprow;
logic o_b_syn_numkeypress;
logic o_b_syn_opkeypress;

// Instantiate DUT
syn uut (
    .i_system_clk(clk),
    .i_system_reset(rst),
    .i_b_syn_nurow(i_b_syn_nurow),
    .i_b_syn_oprow(i_b_syn_oprow),
    .i_b_syn_numkeypress(i_b_syn_numkeypress),

```

```

.i_b_syn_opkeypress(i_b_syn_opkeypress),
.o_b_syn_nurow(o_b_syn_nurow),
.o_b_syn_oprow(o_b_syn_oprow),
.o_b_syn_numkeypress(o_b_syn_numkeypress),
.o_b_syn_opkeypress(o_b_syn_opkeypress)
);

// Clock generation
always #5 clk = ~clk;

// Stimulus
initial begin
$display("==== Start syn_tb simulation ====");
clk = 0;
rst = 1;
i_b_syn_nurow = 4'b0000;
i_b_syn_oprow = 4'b0000;
i_b_syn_numkeypress = 0;
i_b_syn_opkeypress = 0;

// Test 1: System Reset
$display("Test 1: System Reset");
#60;
rst = 0;

// Test 2: Valid Key Press (Debounced)
$display("Test 2: Valid Key Press (Debounced)");
#10;
i_b_syn_nurow = 4'b1010;
i_b_syn_oprow = 4'b1010;
i_b_syn_numkeypress = 1;
i_b_syn_opkeypress = 1;
#100;
i_b_syn_nurow = 4'b1111;
i_b_syn_oprow = 4'b1111;
i_b_syn_numkeypress = 0;
i_b_syn_opkeypress = 0;

// Test 3: Unstable Input (Debounce Fail)
$display("Test 3: Unstable Input (Debounce Fail)");
#10;
i_b_syn_nurow = 4'b1100;
i_b_syn_numkeypress = 1;
#5;
i_b_syn_nurow = 4'b1111;
i_b_syn_oprow = 4'b1111;
i_b_syn_numkeypress = 0;
i_b_syn_opkeypress = 0;

// Observe Outputs
#20;
$display("Output NuRow: %b", o_b_syn_nurow);
$display("Output OpRow: %b", o_b_syn_oprow);
$display("Output NumPress: %b", o_b_syn_numkeypress);
$display("Output OpPress: %b", o_b_syn_opkeypress);

```

```

    $display("==== End syn_tb simulation ====");
    $stop;
end

endmodule

```

4.1.11 Test Result Timing Diagram


//Test 1: System reset

```

reset= 1
o_b_syn_nurow = 4'b0000
o_b_syn_oprow = 4'b0000
o_b_syn_numkeypress = 1'b0
o_b_syn_opkeypress = 1'b0

```

#60 i_system_reset = 0;

 


// Test 2: Valid Key Press (Debounced)

```

#10
i_b_syn_nurow = 4'b1010;
i_b_syn_oprow = 4'b1010;
#100;
o_b_syn_nurow = 4'b1010
o_b_syn_oprow = 4'b1010
o_b_syn_numkeypress = 1'b1
o_b_syn_opkeypress = 1'b1

```

 


// Test 3: Unstable Input (Debounce Fail)

```

i_b_syn_nurow = 4'b1100;
#5;
o_b_syn_nurow = 4'b1111;
o_b_syn_oprow = 4'b1111;

```

 

4.2 hex keypad code generator

4.2.1 Functionality

- Number Keys From 0 to 9
- Operation Keys of Addition, Subtraction, Multiplication, Division, Bitwise AND, OR , XOR, NOT, Barrel Shift Left and Right. The Enter Button for Continue the operation.
- Accepts 8-bit results from previous computations (e.g., ALU/shifter outputs).
- Uses system clock to synchronize keypad inputs and avoid metastability.
- System reset initializes registers and outputs to default states.
- Flags overflow if the operand exceeds 8 bits.
- Binary Output:
 - Based on the scanned keys, the module outputs the corresponding binary values.
- Data Routing:
 - Directs operands to the ALU or Barrel Shifter based on the opcode
 - Routes computation results to the I/O conversion block for display.
- Finite State Machine (FSM) with 4 States:
 - State 00 (Value a): Stores value of a
 - State 01 (Operators): stores operator used
 - State 10 (Value b): Stores value of b
 - State 11 (Computation): Calculates the result

4.2.2 Features

Dual Keypad Sections:

- Numeric Section: Inputs values (0-9) via dedicated rows/columns.
- Operation Section: Inputs arithmetic/logic operations. via separate rows/columns.

Output Interfaces:

- 8-bit Operands: Send numeric inputs to ALU, Barrel Shifter, and IOD.
- 4-bit Opcode: Specifies operations

Compatibility

- Integrates with ALU, Barrel Shifter, and IOD for arithmetic operations, shifts, and display updates.


Low-Latency Design

- Processes inputs within 1 clock cycle for real-time responsiveness.

Synchronization:

- The clock signal is used to synchronize the keypad input signals with the system's clock, ensuring that the outputs are stable and reliable.

4.2.3 Block Interface

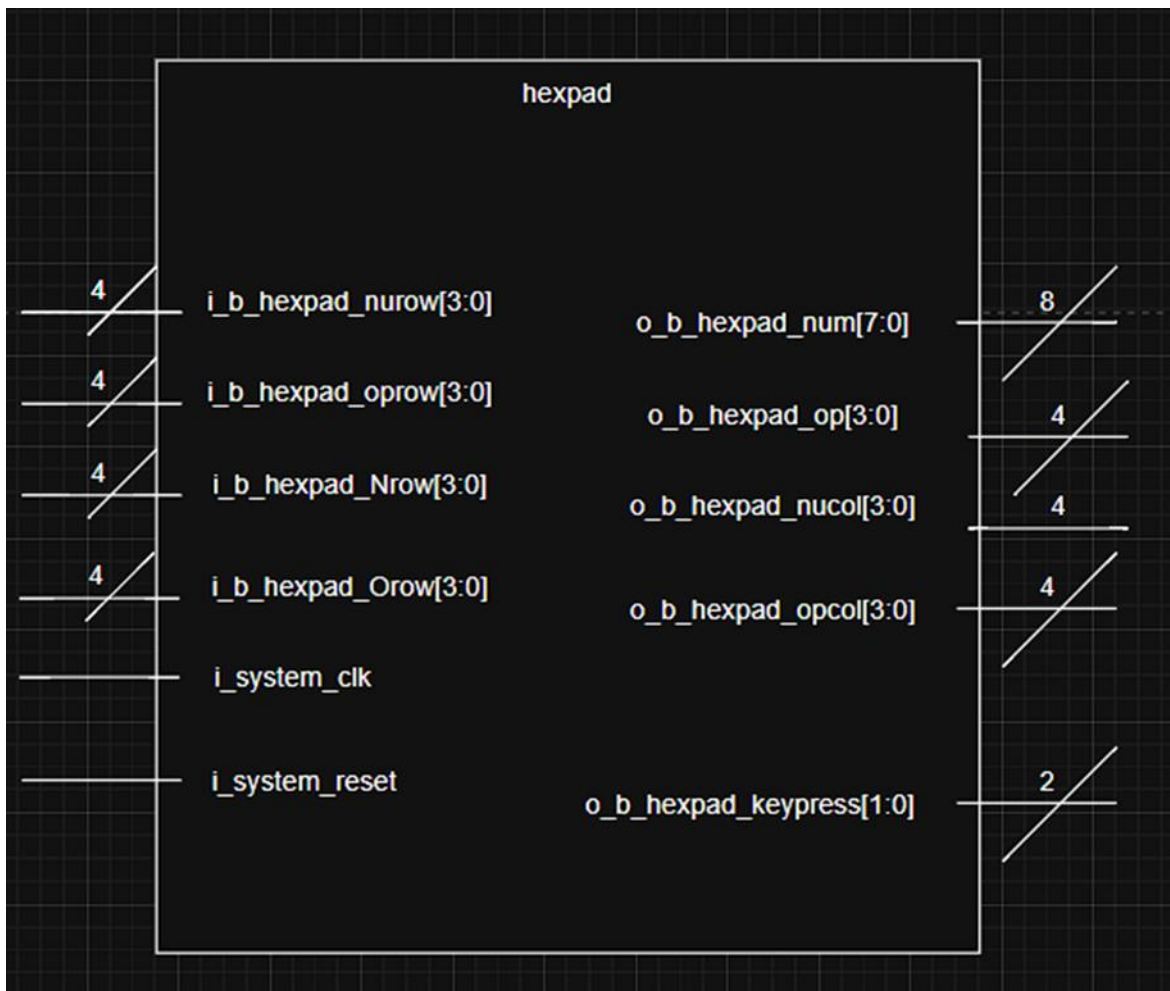

4.2.4 I/O Pin Description

| Pin Name | Pin Class | Pin Direction | Source to direction | Pin Function |
|-----------------------------|-----------------|---------------|------------------------|--|
| <code>i_system_reset</code> | Global, control | Input | Reset button to hexpad | Asynchronous reset to initialize state machine and outputs |
| <code>i_system_clk</code> | Global, control | Input | Clock to hexpad | System clock for FSM timing and sequential logic |

| | | | | |
|-----------------------------------|---------|--------|------------------------------------|--|
| i_b_hexpad_nurow [3:0] | data | Input | keypad to hexpad | Active-low row signal from number keypad (detect key press) |
| i_b_hexpad_oprow [3:0] | data | Input | keypad to hexpad | Active-low row signal from operator keypad |
| i_b_hexpad_Nrow[3:0] | Control | input | keypad scan enable to hexpad | Enable signal for number keypad row scanning |
| i_b_hexpad_Orow[3:0] | Control | input | keypad scan enable to hexpad | Enable signal for operator keypad row scanning |
| o_b_hexpad_num[7:0] | data | Output | Hexpad to CON | Outputs decoded number key value (0–9) |
| o_b_hexpad_op[3:0] | data | output | Hexpad to CON | Outputs decoded operator key value (e.g., +, -, *, etc.) |
| o_b_hexpad_nucol[3:0] | control | Output | Hexpad to keypad matrix | Active-low column scan signal for number keypad |
| o_b_hexpad_opCol [3:0] | control | Output | Hexpad to keypad matrix | Active-low column scan signal for operator keypad |
| o_b_hexpad_keypress [1:0] | Status | Output | Hexpad to controller | Indicates if a key is pressed: 01 = number, 10 = operator |

4.2.5 Internal operation

Number key

| Column (o_b_hexpad_nurow) | Row (i_b_hexpad_nucol) | Key | binary code |
|------------------------------|------------------------|-----|-------------|
| 4'b0001 | 4'b0010 | 9 | 4'b1001 |
| 4'b0001 | 4'b0100 | 8 | 4'b1000 |
| 4'b0001 | 4'b1000 | 7 | 4'b0111 |
| 4'b0010 | 4'b0010 | 6 | 4'b0110 |
| 4'b0010 | 4'b0100 | 5 | 4'b0101 |
| 4'b0010 | 4'b1000 | 4 | 4'b0100 |
| 4'b0100 | 4'b0010 | 3 | 4'b0011 |
| 4'b0100 | 4'b0100 | 2 | 4'b0010 |
| 4'b0100 | 4'b1000 | 1 | 4'b0001 |
| 4'b1000 | 4'b0100 | 0 | 4'b0000 |


| | | | |
|-----------------|---|---|---|
| Default/Invalid | - | - | - |
|-----------------|---|---|---|

| Column (o_b_hexpad_opcol) | Row (i_b_hexpad_oprow) | Operator | binary code |
|------------------------------|---------------------------|----------|-------------|
| 4'b0001 | 4'b0100 | | 4'b0101 |
| 4'b0001 | 4'b1000 | + | 4'b0001 |
| 4'b0010 | 4'b0010 | << | 4'b1001 |
| 4'b0010 | 4'b0100 | & | 4'b0110 |
| 4'b0010 | 4'b1000 | - | 4'b0010 |
| 4'b0100 | 4'b0010 | >> | 4'b1010 |
| 4'b0100 | 4'b0100 | ^ | 4'b0111 |
| 4'b0100 | 4'b1000 | * | 4'b0011 |
| 4'b1000 | 4'b0010 | = | 4'b1011 |
| 4'b1000 | 4'b0100 | ~ | 4'b1000 |
| 4'b1000 | 4'b1000 | / | 4'b0100 |
| Default/Invalid | - | - | - |


8bit result to binary

| Result(i_b_hexpad_result) | binary code |
|---------------------------|-------------|
| 8b'00000001 | 4'b0001 |
| 8b'00000010 | 4'b0010 |
| 8b'00000011 | 4'b0011 |
| 8b'00000100 | 4'b0100 |
| 8b'00000101 | 4'b0101 |
| 8b'00000110 | 4'b0110 |
| 8b'00000111 | 4'b0111 |
| 8b'00001000 | 4'b1000 |
| 8b'00001001 | 4'b1001 |
| 8b'00001010 | 4'b1010 |
| 8b'00001011 | 4'b1011 |
| No key | 4'b0000 |

4.2.6 Timing Requirement

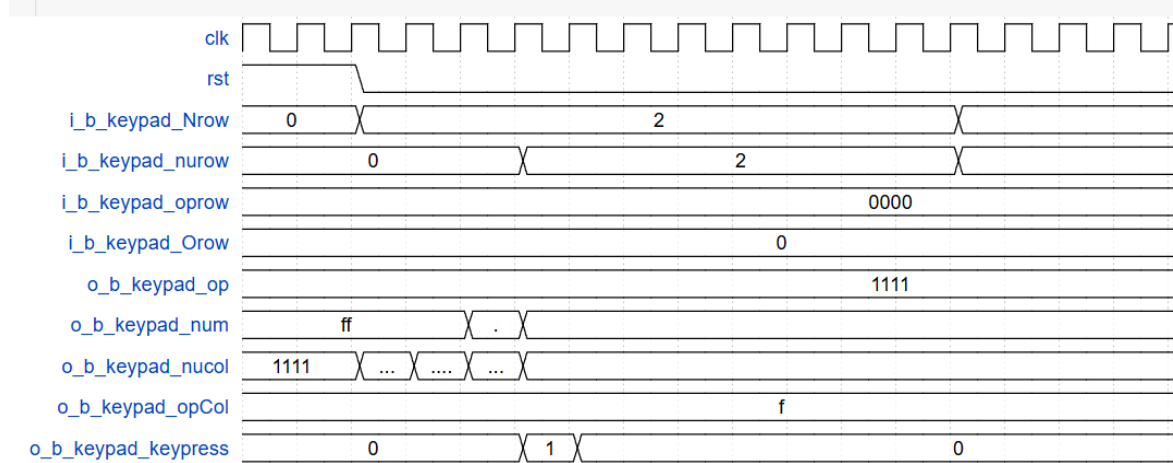

4.2.7 Schematic Predesign

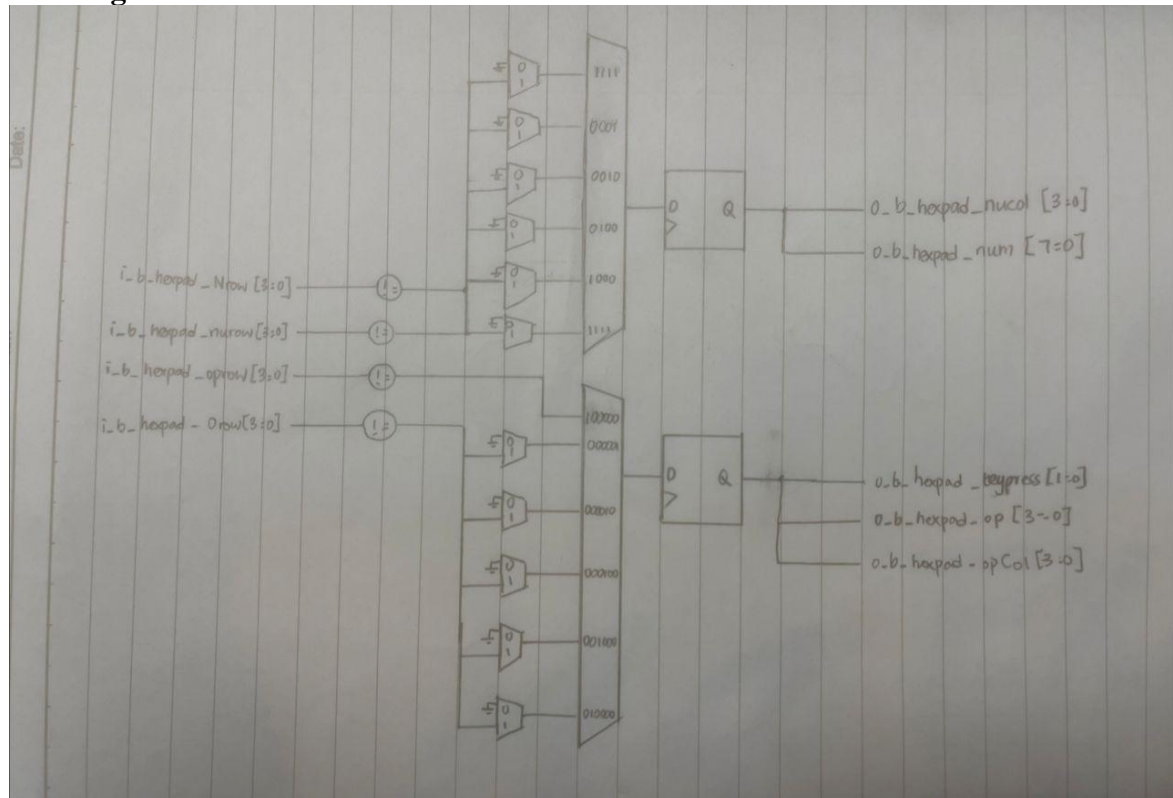

4.2.8 Vivado Model

```
////////////////////////////////////  
// Company: UTAR  
// Engineer: Cheah Lik Ding  
// Create Date: 05/05/2025  
// Module Name: hexpad  
// Project Name: hexpad  
////////////////////////////////////
```

```
module hexpad (  
  
    output logic [7:0] o_b_hexpad_num,  
  
    output logic [3:0] o_b_hexpad_op,  
  
    output logic [3:0] o_b_hexpad_nucol,  
  
    output logic [3:0] o_b_hexpad_opCol,  
  
    output logic [1:0] o_b_hexpad_keypress,  
  
    input logic [3:0] i_b_hexpad_nurow,  
  
    input logic [3:0] i_b_hexpad_oprow,  
  
    input logic i_b_hexpad_Nrow,  
  
    input logic i_b_hexpad_Orow,  
  
    input logic i_system_clk,  
  
    input logic i_system_reset  
  
);  
  
// ----- Number FSM -----  
  
typedef enum  
  
    logic [5:0] { S_0 = 6'b000001, S_1 = 6'b000010, S_2 = 6'b000100, S_3 =  
    6'b001000, S_4 = 6'b010000, S_5 = 6'b100000 } state_t;  
  
    state_t state, next_state;  
  
    always_ff @(posedge i_system_clk or posedge i_system_reset) begin  
  
        if (i_system_reset) state <= S_0;  
  
        else state <= next_state;  
  
    end  
  
    always_comb begin
```

```

next_state = S_0;

o_b_hexpad_nucol = 4'b0000;

case (state)
  S_0: begin
    o_b_hexpad_nucol = 4'b1111;
    if (i_b_hexpad_Nrow != 0)
      next_state = S_1;
    else
      next_state = S_0;
  end
  S_1: begin
    o_b_hexpad_nucol = 4'b0001;
    if (i_b_hexpad_nurow != 4'b0000)
      next_state = S_5;
    else
      next_state = S_2;
  end
  S_2: begin
    o_b_hexpad_nucol = 4'b0010;
    if (i_b_hexpad_nurow != 4'b0000)
      next_state = S_5;
    else
      next_state = S_3;
  end
  S_3: begin
    o_b_hexpad_nucol = 4'b0100;
    if (i_b_hexpad_nurow != 4'b0000)
      next_state = S_5;
    else
      next_state = S_4;
  end
  S_4: begin
    o_b_hexpad_nucol = 4'b1000;
    if (i_b_hexpad_nurow != 4'b0000)
      next_state = S_5;
    else
      next_state = S_0;
  end
  S_5: begin
    o_b_hexpad_nucol = 4'b1111;
    if (i_b_hexpad_Nrow == 4'b0000)
      next_state = S_0;
    else
      next_state = S_5;
  end
  default: next_state = S_0;
endcase

end

// ----- Operator FSM -----

typedef enum

```

```

logic [5:0] { S0_OP = 6'b000001, S1_OP = 6'b000010, S2_OP = 6'b000100, S3_OP
= 6'b001000, S4_OP = 6'b010000, S5_OP = 6'b100000 } state_op_t;

state_op_t state_op, next_state_op;

always_ff @(posedge i_system_clk or posedge i_system_reset) begin

if (i_system_reset) state_op <= S0_OP;

else state_op <= next_state_op;

end

always_comb begin

next_state_op = S0_OP;

o_b_hexpad_opCol = 4'b0000;

case (state_op)
    S0_OP: begin
        o_b_hexpad_opCol = 4'b1111;
        if (i_b_hexpad_Orow != 0)
            next_state_op = S1_OP;
        else
            next_state_op = S0_OP;
    end
    S1_OP: begin
        o_b_hexpad_opCol = 4'b0001;
        if (i_b_hexpad_oprow != 4'b0000)
            next_state_op = S5_OP;
        else
            next_state_op = S2_OP;
    end
    S2_OP: begin
        o_b_hexpad_opCol = 4'b0010;
        if (i_b_hexpad_oprow != 4'b0000)
            next_state_op = S5_OP;
        else
            next_state_op = S3_OP;
    end
    S3_OP: begin
        o_b_hexpad_opCol = 4'b0100;
        if (i_b_hexpad_oprow != 4'b0000)
            next_state_op = S5_OP;
        else
            next_state_op = S4_OP;
    end
    S4_OP: begin
        o_b_hexpad_opCol = 4'b1000;
        if (i_b_hexpad_oprow != 4'b0000)
            next_state_op = S5_OP;
        else
            next_state_op = S0_OP;
    end
    S5_OP: begin
        o_b_hexpad_opCol = 4'b1111;

```

```

        if (i_b_hexpad_Orow == 4'b0000)
            next_state_op = S0_OP;
        else
            next_state_op = S5_OP;
        end
        default: next_state_op = S0_OP;
    endcase

end

always_comb begin

    o_b_hexpad_keypress = 2'b00; // default: no key pressed
    if (((state==S_1)||((state==S_2)||((state==S_3)||((state==S_4))&&
    i_b_hexpad_nurow)
        //if (numRow != 4'b0000)
            o_b_hexpad_keypress = 2'b01; // Number key pressed
    else if
        (((state_op==S1_OP)||((state_op==S2_OP)||((state_op==S3_OP)||((state_op==S4_O
        P))&& i_b_hexpad_oprow)

        //else if (opRow != 4'b0000)
            o_b_hexpad_keypress = 2'b10; // Operator key pressed
    end

    // ----- Decoder Logic -----
    always_comb begin
        case ({i_b_hexpad_nurow, o_b_hexpad_nuCol})
            8'b0001_0010: o_b_hexpad_num = 8'd9;
            8'b0001_0100: o_b_hexpad_num = 8'd8;
            8'b0001_1000: o_b_hexpad_num = 8'd7;
            8'b0010_0010: o_b_hexpad_num = 8'd6;
            8'b0010_0100: o_b_hexpad_num = 8'd5;
            8'b0010_1000: o_b_hexpad_num = 8'd4;
            8'b0100_0010: o_b_hexpad_num = 8'd3;
            8'b0100_0100: o_b_hexpad_num = 8'd2;
            8'b0100_1000: o_b_hexpad_num = 8'd1;
            8'b1000_0100: o_b_hexpad_num = 8'd0;
            default: o_b_hexpad_num = 8'b1111;
        endcase
    end

    always_comb begin
        case ({i_b_hexpad_oprow, o_b_hexpad_opCol})
            8'b0001_0100: o_b_hexpad_op = 4'd5; // |
            8'b0001_1000: o_b_hexpad_op = 4'd1; // +
            8'b0010_0010: o_b_hexpad_op = 4'd9; // <<
            8'b0010_0100: o_b_hexpad_op = 4'd6; // &
            8'b0010_1000: o_b_hexpad_op = 4'd2; // -
            8'b0100_0010: o_b_hexpad_op = 4'd10; // >>
            8'b0100_0100: o_b_hexpad_op = 4'd7; // ^
            8'b0100_1000: o_b_hexpad_op = 4'd3; // *
            8'b1000_0010: o_b_hexpad_op = 4'd11; // =
            8'b1000_0100: o_b_hexpad_op = 4'd8; // ~
            8'b1000_1000: o_b_hexpad_op = 4'd4; // /
            default: o_b_hexpad_op = 4'b1111;
        endcase
    end
end

```

```

endcase
end

endmodule

```

4.2.9 Test Plan

| No. | Test Case | Description of Test Vector Generation | Expected Operation | Pass/fail |
|-----|--------------------|---|---|-----------|
| 1 | Reset | reset = 1 | o_b_hexpad_nucol = 4'b1111 o_b_hexpad_opCol = 4'b1111 o_b_hexpad_num = 8'hFF o_b_hexpad_op = 4'hF o_b_hexpad_keypress = 2'b00 | Pass |
| 2 | Press key 5 | i_b_hexpad_Nrow = 1; wait for 3 clock cycle i_b_hexpad_nurow = 4'b0010; | o_b_hexpad_nucol = 4'b0100; o_b_hexpad_num = 8'd5; o_b_hexpad_keypress = 2'b01; | Pass |
| 3 | Press operator '+' | i_b_hexpad_Orow =1; Wait for 4 clock cycle i_b_hexpad_nurow = 4'b0010; | o_b_hexpad_opCol = 4'b1000; o_b_hexpad_op = 4'd1; o_b_hexpad_keypress = 2'b10; | Pass |

4.2.10 TestBench

```
////////////////////////////////////
// Company: UTAR
// Engineer: Cheah Lik Ding
// Create Date: 05/05/2025
// Module Name: tb_hexpad
// Project Name: tb_hexpad
////////////////////////////////////

module tb_hexpad;

logic [7:0] o_b_hexpad_num;
logic [3:0] o_b_hexpad_op;
logic [3:0] o_b_hexpad_nucol, o_b_hexpad_opCol;
logic [1:0] o_b_hexpad_keypress;

logic [3:0] i_b_hexpad_nurow, i_b_hexpad_oprow;
logic i_b_hexpad_Nrow, i_b_hexpad_Orow;
logic i_system_clk, i_system_reset;

// Instantiate DUT
hexpad dut (
    .o_b_hexpad_num(o_b_hexpad_num),
    .o_b_hexpad_op(o_b_hexpad_op),
    .o_b_hexpad_nucol(o_b_hexpad_nucol),
    .o_b_hexpad_opCol(o_b_hexpad_opCol),
    .o_b_hexpad_keypress(o_b_hexpad_keypress),
    .i_b_hexpad_nurow(i_b_hexpad_nurow),
    .i_b_hexpad_oprow(i_b_hexpad_oprow),
    .i_b_hexpad_Nrow(i_b_hexpad_Nrow),
    .i_b_hexpad_Orow(i_b_hexpad_Orow),
    .i_system_clk(i_system_clk),
    .i_system_reset(i_system_reset)
);

// Clock generation: 10ns period
initial i_system_clk = 0;
always #5 i_system_clk = ~i_system_clk;

initial begin
    // Test 1 Rest
    i_system_reset = 1;
    i_b_hexpad_nurow = 4'b0000;
    i_b_hexpad_oprow = 4'b0000;
    i_b_hexpad_Nrow = 0;
    i_b_hexpad_Orow = 0;

    #20;
    i_system_reset = 0;

    // Test 2 === Press key 5 ===
    i_b_hexpad_Nrow = 1;
    #30;
    i_b_hexpad_nurow = 4'b0010;
    #80;
    i_b_hexpad_nurow = 4'b0000;
```

```

i_b_hexpad_Nrow = 0;

// Test 3 === Press operator '+' ===
#50;
i_b_hexpad_Orow = 1;
#40;
i_b_hexpad_oprow = 4'b0001;
#80;
i_b_hexpad_oprow = 4'b0000;
i_b_hexpad_Orow = 0;

// === End simulation ===
#100;
$finish;
end

initial begin
  $display("Time\t NuRow NuCol Num OpRow OpCol Op KeyPress");
  $monitor("%0t\t %b %b %0d %b %b %0d %b",
    $time,
    i_b_hexpad_nurow,
    o_b_hexpad_nucol,
    o_b_hexpad_num,
    i_b_hexpad_oprow,
    o_b_hexpad_opCol,
    o_b_hexpad_op,
    o_b_hexpad_keypress);
end

endmodule

```

 

4.2.11 Test Result Timing Diagram

// Test 1: Reset test

reset = 1

All outputs should be at default values:

- o_b_hexpad_nucol = 4'b1111
- o_b_hexpad_opCol = 4'b1111
- o_b_hexpad_num = 8'hFF
- o_b_hexpad_op = 4'hF
- o_b_hexpad_keypress = 2'b00



//Test 2: Press key 5

i_b_hexpad_Nrow = 1;

Wait for 3 clock cycle


i_b_hexpad_nurow = 4'b0010;

Expected output

o_b_hexpad_nucol = 4'b0100;

o_b_hexpad_num = 8'd5;

o_b_hexpad_keypress = 2'b01;

 

//Test 3: Press operator '+'

i_b_hexpad_Orow = 1;

Wait for 4 clock cycle


i_b_hexpad_nurow = 4'b0010;

Expected Output:

o_b_hexpad_opCol = 4'b1000;

o_b_hexpad_op = 4'd1;

o_b_hexpad_keypress = 2'b10;

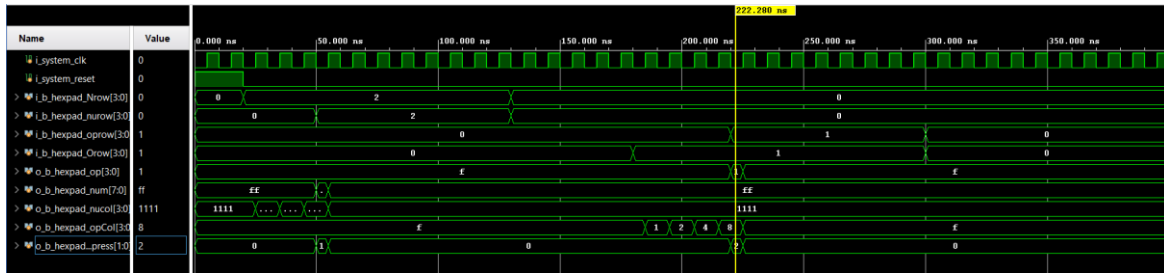

4.3 Control Unit Block

4.3.1 Functionality

The cub module serves as the control unit that manages user input from a keypad for a simple calculator system. It interprets numeric and operator key inputs, organizes operand data, decodes operations, and prepares the appropriate output signals for arithmetic or logic computation.

1. Operand Capture:

- Accepts numeric key inputs and constructs multi-digit operands A and B.
- Supports up to 3-digit input for each operand using decimal entry logic ($\times 10$ accumulation).

2. Operator Decoding:

- Receives an operator key and decodes it into a 4-bit opcode.
- Recognizes arithmetic (+, -, *, /) and bitwise (&, |, ^, ~, <<, >>) operations.

3. State Management:

- Uses a finite state machine (FSM) to control input sequencing:
IDLE \rightarrow LOAD_A \rightarrow LOAD_OP \rightarrow LOAD_B \rightarrow (optional COMPUTE) \rightarrow RESET
- Prevents accidental multiple registrations using key debounce logic (prev_key latch).


4. Overflow Detection:

- Monitors operand values and sets an overflow flag if they exceed 255 (8-bit limit).

4.3.2 Features

- Support for Two Operands:** Handles two separate 8-bit operands.
- Multi-Digit Entry:** Allows users to input numbers digit by digit (e.g., pressing '1', then '2' results in 12).
- Operator Mapping:** Decodes specific hex values to standard operations (+, -, etc.).
- Shift Operation Detection:** Flags if the selected operation is a shift (<< or >>).
- Overflow Flag:** Signals when an operand exceeds 8-bit capacity.
- Reset Handling:** Fully resets all internal registers and state on reset.

4.3.3 Block Interface

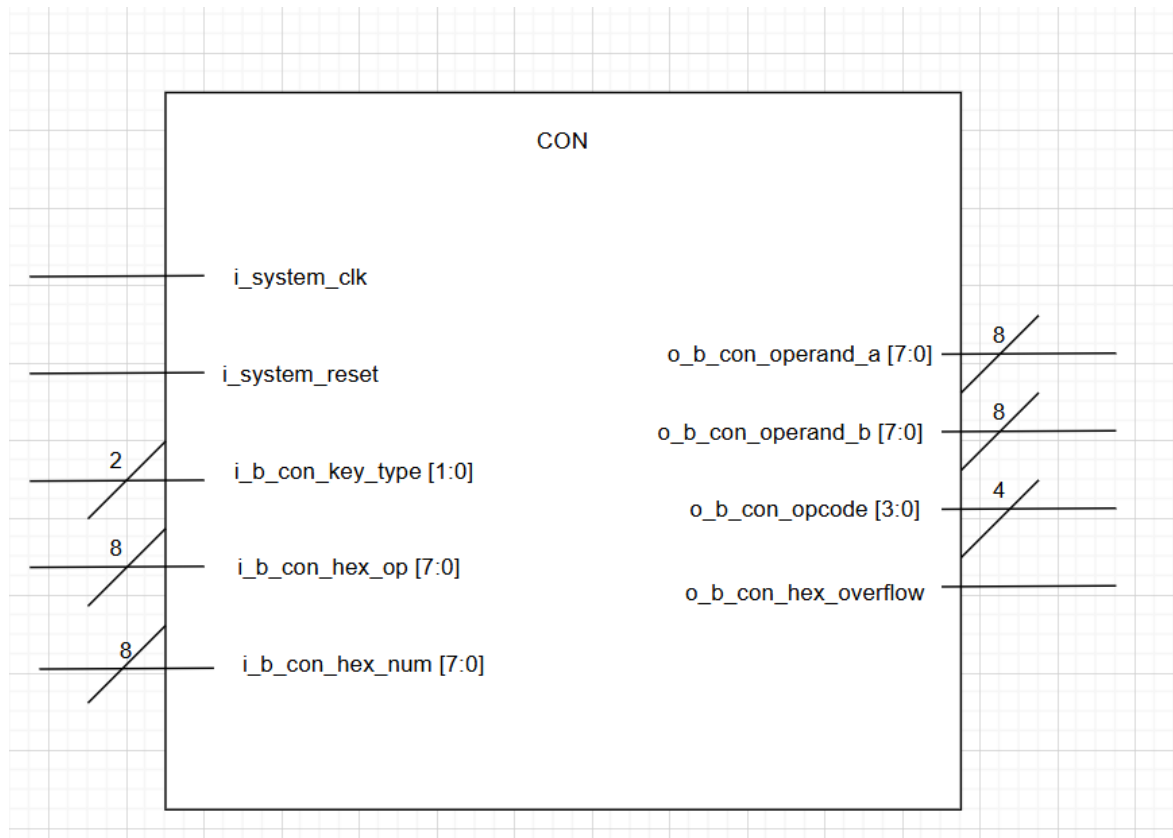

4.3.4 I/O Pin Description


| Pin Name | Source To Destination | Pin Direction | Pin Class | Pin Function |
|-------------------------------------|-----------------------|---------------|-----------|--|
| <code>i_system_clk</code> | Global Clock to CON | input | control | System clock used for synchronous logic |
| <code>i_system_reset</code> | Reset Button to CON | input | control | Active-high system reset that initializes the module |
| <code>i_b_con_hex_num[7:0]</code> | Keypad Decoder to CON | input | data | 8-bit value representing the pressed number key |
| <code>i_b_con_hex_opc[7:0]</code> | Keypad Decoder to CON | input | data | 8-bit value representing the pressed operator key |
| <code>i_b_con_key_type [1:0]</code> | Keypad Decoder to CON | input | data | Indicates the type of key pressed: number |

| | | | | |
|------------------------|--------------------|--------|--------|---|
| | | | | or operator |
| o_b_con_operand_a[7:0] | CON to ALU/Display | output | data | 8-bit output of the first operand (A) |
| o_b_con_operand_b[7:0] | CON to ALU/Display | output | data | 8-bit output of the second operand (B) |
| o_b_con_hex_overflow | CON to Display | output | status | High if operand A or B exceeds 8-bit (overflow) |
| o_b_con_opcode[3:0] | CON to ALU | output | data | 4-bit decoded opcode based on the operator key |


4.3.5 Internal operation

| | reset | A=1 | B=2 | Opcode='+' | Opcode='=' | B=256 |
|------------------------|-------|---------|---------|---|--|-------------------------|
| i_system_reset | 1 | 0 | 0 | 0 | 0 | 0 |
| i_b_con_hex_num[7:0] | 8'h0 | 8'h1 | 8'h2 | 8'h0 | 8'h0 | 8'd2, 8'd5, 8'd6 |
| i_b_con_hex_opc[7:0] | 8'h0 | 8'h0 | 8'h0 | 8'h3 | 8'h5 | 8'h4 |
| i_b_con_key_type [1:0] | 2'b00 | 2'b01 | 2'b01 | 2'b10 | 2'b10 | 2'b01 |
| o_b_con_operand_a[7:0] | 8'h0 | 8'h1 | 8'h0 | 8'h0 | 8'h0 | 8'h0 |
| o_b_con_operand_b[7:0] | 8'h0 | 8'h0 | 8'h2 | 8'h0 | 8'h0 | 8'h2 8'h25 8'h256 |
| o_b_con_hex_overflow | 0 | 0 | 0 | 0 | 0 | 1 |
| o_b_con_opcode[3:0] | 4'h0 | 4'b1111 | 4'b1110 | stored 4'b0001 and release after press(=) | 4'b1011 opcode that stored before | 4'b1110 |


4.3.6 Timing Requirement

 

4.3.7 Schematic Predesign

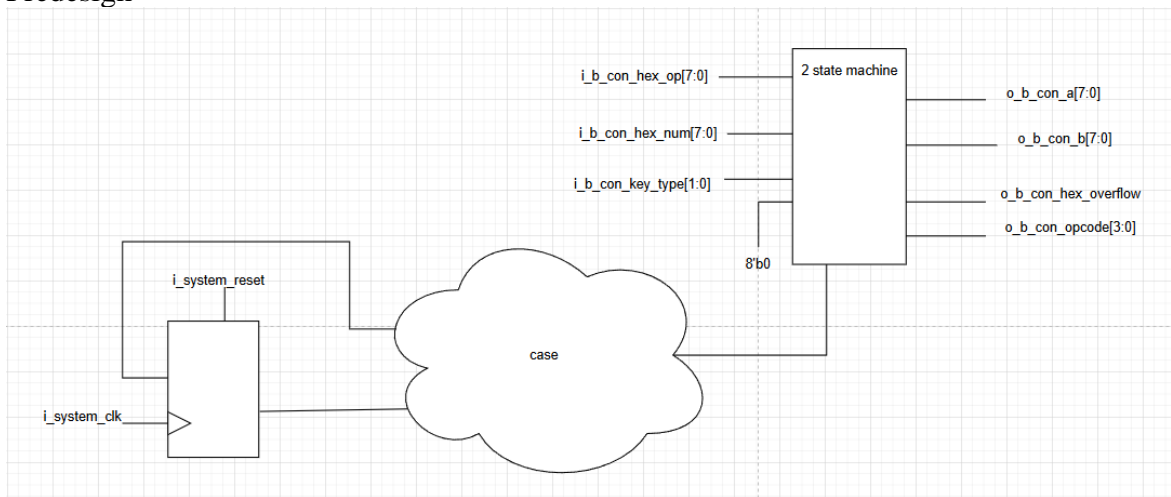

Postdesign

 

4.3.8 Vivado Model

```

////////////////////////////////////
// Company: UTAR
// Engineer: CHONG BING HONG
// Create Date: 07/05/2025

```

```

// Module Name: CON
// Project Name: CON
/////////////////////////////////////////////////////////////////

module con (
input i_system_clock,
input i_system_reset,
input [1:0] i_b_con_key_type,
input [7:0] i_b_con_hex_num,
input [7:0] i_b_con_hex_op,

output logic [3:0] o_b_con_opcode,
output logic [7:0] o_b_con_a,
output logic [7:0] o_b_con_b,
output logic o_b_con_hex_overflow );

logic [8:0] reg_a, reg_b;
logic opc_load = 1'b0;
logic [2:0] state = 3'b000;
logic [7:0] str_key_op;

always_ff @(posedge i_system_clock, posedge i_system_reset) begin
    if (i_system_reset) begin
        o_b_con_opcode    <= 4'hF;
        o_b_con_a         <= 8'h00;
        o_b_con_b         <= 8'h00;
        reg_a              <=0;
        reg_b              <=0;
        o_b_con_hex_overflow <= 1'b0;
        opc_load           <= 1'b0;
        state              <= 3'b000;
    end
    else begin
        case (state)
            3'b000: begin
                if ((i_b_con_key_type == 2'b10) && (i_b_con_hex_op != 4'hF)&&
(i_b_con_hex_op != 4'hB)) begin
                    str_key_op <= i_b_con_hex_op;
                    opc_load    <= 1'b1;
                end
                else if ((i_b_con_key_type == 2'b10)&&(i_b_con_hex_op != 4'hF)) begin
                    state    <= 3'b100;
                end
                else if ((!opc_load) && (i_b_con_key_type == 2'b01) && (i_b_con_hex_num
<= 8'h09)) begin
                    reg_a<=reg_a*10+i_b_con_hex_num;
                    o_b_con_opcode <= 4'hF;
                    o_b_con_a <= reg_a*10+i_b_con_hex_num;
                    o_b_con_hex_overflow <= ((reg_a*10+i_b_con_hex_num) > 255);
                end
            end
        endcase
    end
end

```

```

        end
        else if (opc_load && (i_b_con_key_type == 2'b01) && (i_b_con_hex_num <=
8'h09)) begin
            reg_b<=reg_b*10+i_b_con_hex_num;
            o_b_con_opcode <= 4'hE;
            o_b_con_b <= reg_b*10+i_b_con_hex_num;
            o_b_con_hex_overflow <= ((reg_b*10+i_b_con_hex_num) > 255);
        end
    end
end

3'b100: begin
    o_b_con_opcode <= str_key_op;
    opc_load<=0;
    state    <= 3'b000;
end
default: state <= 3'b000;
endcase
end
end
endmodule

```

4.3.9 Test Plan

| No. | Test Case | Description of Test Vector Generation | Expected Operation | Pass/fail |
|-----|----------------------|--|---|-----------|
| 1 | System Reset | //Wait for 10 clock cycle, tb_system_reset = 1; //wait for 10 clock cycle, tb_system_reset = 0; //wait for 10 clock cycle | i_b_con_hex_num=11111111 i_b_con_hex_op=11111111 o_b_con_a=00000000 o_b_con_b=00000000 o_b_con_opcode=1111 o_b_con_hex_overflow=0 | pass |
| 2 | Load Operand A (135) | //A=1 i_b_con_key_type = 2'b01; i_b_con_hex_num = 8'h01; //Wait for10 clock cycle, i_b_con_key_type = 2'b00; // release i_b_con_hex_num = 8'hFF; //Wait for10 clock cycle, //A=3 i_b_con_key_type = | i_b_con_key_type=2'b01 o_b_con_a=8'd1 o_b_con_opcode=4'b1111 After 10 clock cycle, i_b_con_key_type=2'b01 I_b_con_a=8'd13 o_b_con_opcode=4'b1111 After 10 clock cycle, i_b_con_key_type=2'b01 I_b_con_a=8'd135 o_b_con_opcode=4'b1111 | pass |

| | | | | |
|---|----------------------|--|--|------|
| | | <pre> 2'b01; i_b_con_hex_num =8'h03; //Wait for10 clock cycle, i_b_con_key_type = 2'b00; // release i_b_con_hex_num =8'hFF; //Wait for10 clock cycle, //A=5 i_b_con_key_type = 2'b01; i_b_con_hex_num =8'h05; //Wait for10 clock cycle, i_b_con_key_type = 2'b00; // release i_b_con_hex_num =8'hFF; //Wait for10 clock cycle, </pre> | | |
| 3 | Load Operator (+) | <pre> i_b_con_key_type = 2'b10; i_b_con_hex_op = 8'h01; // + //Wait for10 clock cycle, i_b_con_key_type = 2'b00; i_b_con_hex_op = 8'hFF; //Wait for10 clock cycle, </pre> | <pre> i_b_con_key_type = 2'b10 i_b_con_hex_op = 8'h01 </pre> | pass |
| 4 | Load Operand B(4) | <pre> //B=4 i_b_con_key_type = 2'b01; i_b_con_hex_num = 8'h04; //Wait for10 clock cycle, i_b_con_key_type = </pre> | <pre> i_b_con_key_type = 2'b01 o_b_con_b= 8'h4 o_b_con_opcode=4'b1110 </pre> | pass |

| | | | | |
|---|----------------------|--|---|------|
| | | 2'b00; i_b_con_hex_num = 8'hFF; //Wait for10 clock cycle, | | |
| 5 | Load (=) | //hex_op =(= i_b_con_key_type = 2'b10; i_b_con_hex_op = 8'h0B; //Wait for10 clock cycle, i_b_con_key_type = 2'b00; i_b_con_hex_op = 8'hFF; //Wait for20 clock cycle, | i_b_con_key_type = 2'b10 i_b_con_hex_op = 8'hB o_b_con_opcode=4'0001 | pass |
| 6 | Load operator(>>) | // operator =>> i_b_con_key_type = 2'b10; i_b_con_hex_op = 8'h10; //Wait for10 clock cycle, i_b_con_key_type = 2'b00; i_b_con_hex_op = 8'hFF; //Wait for10 clock cycle, | i_b_con_key_type = 2'b10 i_b_con_hex_op = 8'h10 | pass |
| 7 | Overflow(256) | //reset previous result //Wait for10 clock cycle, i_system_reset = 1; //Wait for10 clock cycle, i_system_reset = 0; //Wait for10 clock cycle, //A=2 i_b_con_key_type = 2'b01; i_b_con_hex_num =8'h02; //Wait for10 clock | i_b_con_key_type=2'b01 o_b_con_a=8'd2 o_b_con_opcode=4'b1111 After 10 clock cycle, i_b_con_key_type=2'b01 I_b_con_a=8'd25 o_b_con_opcode=4'b1111 After 10 clock cycle, i_b_con_key_type=2'b01 I_b_con_a=8'd0 o_b_con_opcode=4'b1111 o_b_con_overflow=1 | pass |

| | | | | |
|--|--|---|--|--|
| | | cycle, i_b_con_key_type = 2'b00; // release i_b_con_hex_num =8'hFF; //Wait for10 clock cycle, //A=5 i_b_con_key_type = 2'b01; i_b_con_hex_num =8'h05; //Wait for10 clock cycle, i_b_con_key_type = 2'b00; // release i_b_con_hex_num =8'hFF; //Wait for10 clock cycle, //A=6 i_b_con_key_type = 2'b01; i_b_con_hex_num =8'h06; //Wait for10 clock cycle, i_b_con_key_type = 2'b00; // release i_b_con_hex_num =8'hFF; //Wait for10 clock cycle, | | |
|--|--|---|--|--|

4.3.10 TestBench

```

////////////////////////////////////
// Company: UTAR
// Engineer: CHONG BING HONG
// Create Date: 07/05/2025
// Module Name: tb_con
// Project Name: tb_con
////////////////////////////////////

```

` timescale 1ns / 1ps

```

`define PERIOD_CLK 5

module tb_con();

// Inputs
logic      tb_system_clock;
logic      tb_system_reset;
logic [1:0] tb_b_con_key_type;
logic [7:0] tb_b_con_hex_num;
logic [7:0] tb_b_con_hex_op;

// Outputs
logic [7:0] tb_b_con_operand_a;
logic [7:0] tb_b_con_operand_b;
logic [3:0] tb_b_con_opcode;
logic      tb_b_con_hex_overflow;

// DUT
con dut (
    .i_system_clock(tb_system_clock),
    .i_system_reset(tb_system_reset),
    .i_b_con_key_type(tb_b_con_key_type),
    .i_b_con_hex_num(tb_b_con_hex_num),
    .i_b_con_hex_op(tb_b_con_hex_op),
    .o_b_con_operand_a(tb_b_con_operand_a),
    .o_b_con_operand_b(tb_b_con_operand_b),
    .o_b_con_opcode(tb_b_con_opcode),
    .o_b_con_hex_overflow(tb_b_con_hex_overflow)
);

// Clock generation
initial tb_system_clock = 0;
always #(`PERIOD_CLK) tb_system_clock = ~tb_system_clock;

initial begin
    $display("--- Start tb_cub ---");

// Default init
    tb_system_reset = 0;
    tb_b_con_key_type = 2'b00;
    tb_b_con_hex_num = 8'hFF;
    tb_b_con_hex_op = 8'hFF;

//Test Case 1: System Reset
    #10; tb_system_reset = 1;
    #10; tb_system_reset = 0;
    #10;

//Test Case 2: Load Operand A (1?3?5)
    tb_b_con_key_type = 2'b01;
    tb_b_con_hex_num = 8'h01;
    #10;
    tb_b_con_key_type = 2'b00; // release
    tb_b_con_hex_num = 8'hFF;
    #10;

```

```

tb_b_con_key_type = 2'b01;
tb_b_con_hex_num = 8'h03;
#10;
tb_b_con_key_type = 2'b00; // release
tb_b_con_hex_num = 8'hFF;
#10;

tb_b_con_key_type = 2'b01;
tb_b_con_hex_num = 8'h05;
#10;
tb_b_con_key_type = 2'b00; // release
tb_b_con_hex_num = 8'hFF;
#10;

//Test Case 3: Load Operator (+)
tb_b_con_key_type = 2'b10;
tb_b_con_hex_op = 8'h01; // +
#10;
tb_b_con_key_type = 2'b00;
tb_b_con_hex_op = 8'hFF;
#10;

//Test Case 4: Load Operand B (4)
tb_b_con_key_type = 2'b01;
tb_b_con_hex_num = 8'h04;
#10;
tb_b_con_key_type = 2'b00;
tb_b_con_hex_num = 8'hFF;
#10;

//Test Case 5: Trigger Compute by Loading ("=")
tb_b_con_key_type = 2'b10;
tb_b_con_hex_op = 8'h0B;
#10;
tb_b_con_key_type = 2'b00;
tb_b_con_hex_op = 8'hFF;
#20;

//Test Case 6: Trigger Barrel Shifter by Loading (">>")
tb_b_con_key_type = 2'b10;
tb_b_con_hex_op = 8'h10; // >>
#10;
tb_b_con_key_type = 2'b00;
tb_b_con_hex_op = 8'hFF;
#10;

//Test Case 7: overflow (2, 5, 6)
//reset
#10; tb_system_reset = 1;
#10; tb_system_reset = 0;
#10;

tb_b_con_key_type = 2'b01;
tb_b_con_hex_num = 8'h02;
#10;
tb_b_con_key_type = 2'b00; // release

```

```

tb_b_con_hex_num = 8'hFF;
#10;

tb_b_con_key_type = 2'b01;
tb_b_con_hex_num = 8'h05;
#10;
tb_b_con_key_type = 2'b00; // release
tb_b_con_hex_num = 8'hFF;
#10;


tb_b_con_key_type = 2'b01;
tb_b_con_hex_num = 8'h06;
#10;
tb_b_con_key_type = 2'b00; // release
tb_b_con_hex_num = 8'hFF;
#10;
// End simulation
#(`PERIOD_CLK * 5);
$display("--- End tb_con ---");
$finish;
end

endmodule

```

4.3.11 Result Simulation

//Test Case 1: System Reset

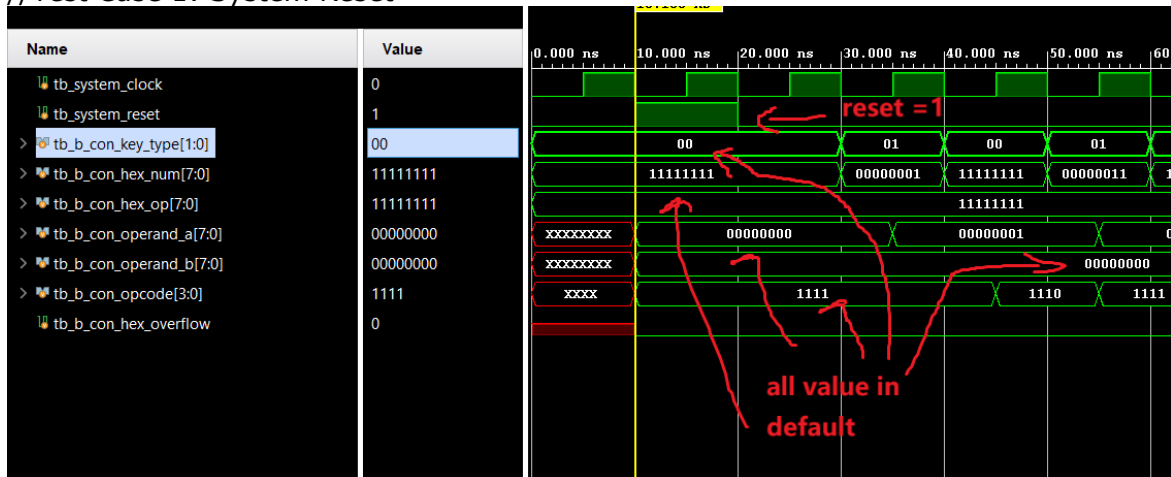


//Test Case 2: Load Operand A (1,3,5)



//Test Case 3: Load Operator (+)


//Test Case 4: Load Operand B

(4)

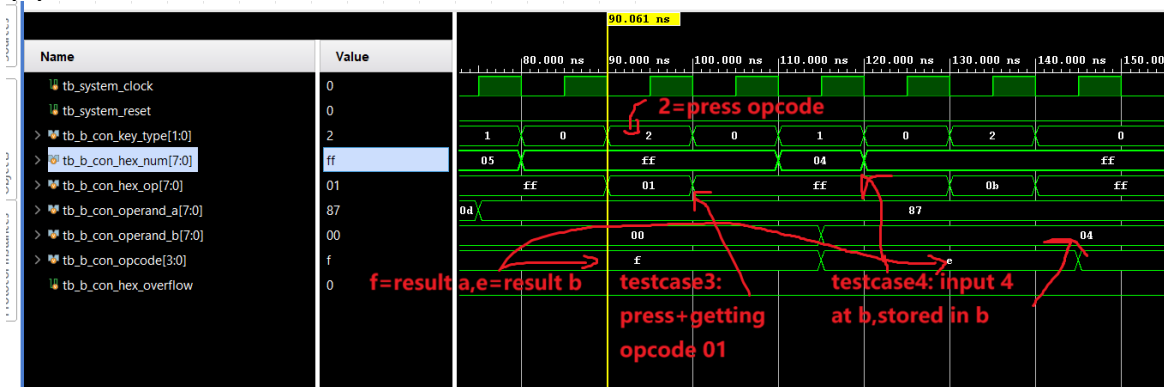


//Test Case 5: Trigger Compute by Loading ("=")

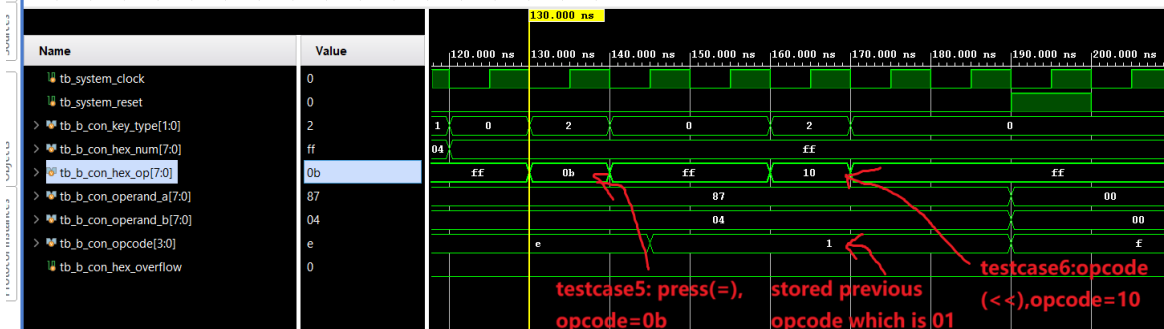//Test Case 6: Trigger Barrel Shifter by Loading (">>")



//Test Case 7: overflow (2, 5, 6)

 

4.4 ALU

4.4.1 Functionality

- Addition of two 8-bit integers
- Subtraction of two 8-bit integers


- Multiplication of two 8-bit integers
- Division of two 8-bit integers
- Bitwise AND of two 8-bit integers
- Bitwise OR of two 8-bit integers
- Bitwise XOR of two 8-bit integers
- Bitwise NOT of an 8-bit integer

4.4.2 Features

- Detects overflow for Addition, Multiplication and Division
- Detects negative of Subtraction

4.4.3 Block Interface

ALU Block Interface:

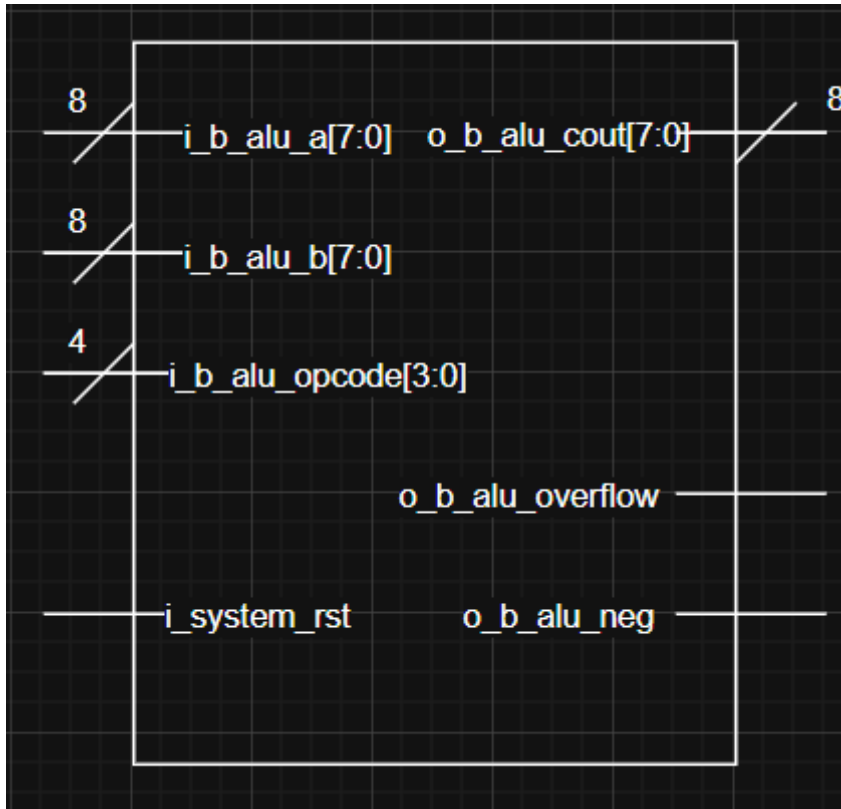

4.4.4 I/O Pin Description


| Pin Name | Source To Destination | Pin Direction | Pin Class | Pin Function |
|----------------------|-----------------------|---------------|-----------|--|
| i_b_alu_a[7:0] | CON to ALU | Input | data | Transmit the first 8-bit data to ALU |
| i_b_alu_b [7:0] | CON to ALU | Input | data | Transmit the second 8-bit data to ALU |
| i_b_alu_opcode [3:0] | CON to ALU | Input | data | Transmit the operation code to the ALU for determine the operation |

| | | | | |
|--------------------|---------------------|--------|-----------------|---------------------------------------|
| i_system_rst | RESET button to ALU | Input | Global, control | To reset system |
| o_b_alu_cout [7:0] | ALU to IOD | Output | data | Transmit the 8-bit result to Display |
| o_b_alu_overflow | ALU to IOD | Output | data | Transmit the Overflow flag to Display |
| o_b_alu_neg | ALU to IOD | Output | data | Transmit the Negative flag to Display |


4.4.5 Internal operation

| i_b_alu_opcode [3:0] | ALU Function | ALU Implication | Notes |
|----------------------|----------------|-----------------|-----------------------------|
| 0001 | Addition | $A + B$ | If result > 255, overflow=1 |
| 0010 | Subtraction | $A - B$ | if $A < B$, neg = 1 |
| 0011 | Multiplication | $A * B$ | If result > 255, overflow=1 |
| 0100 | Division | A / B | If $B == 0$, overflow =1 |
| 0101 | Bitwise AND | $A \& B$ | |
| 0110 | Bitwise OR | $A B$ | |
| 0111 | Bitwise XOR | $A \wedge B$ | |
| 1000 | Bitwise NOT | $\sim A$ | |


4.4.6 Timing Requirement

 

4.4.7 Schematic predesign

 

postdesign

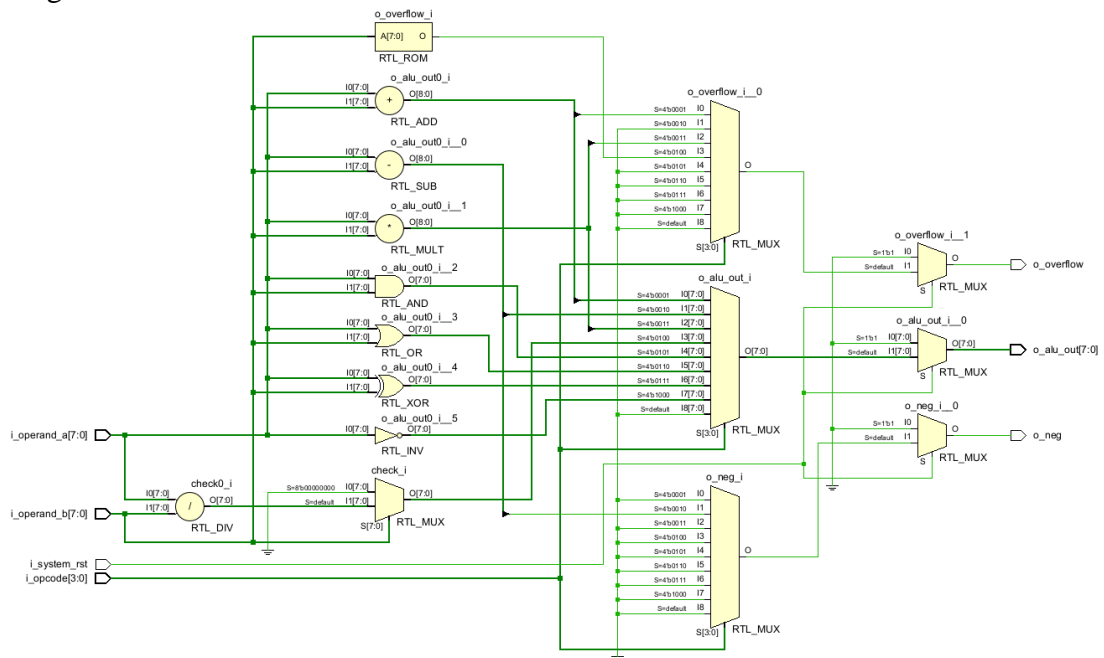

4.4.8 Vivado Model

```
/////////////////////////////////////////////////////////////////
// Company: UTAR
// Engineer: SHU MEE ANG
// Create Date: 05/05/2025
// Module Name: ALU
// Project Name: ALU
/////////////////////////////////////////////////////////////////
module ALU (
output logic [7:0] o_alu_out,
output logic o_neg,
output logic o_overflow,
input logic [7:0] i_operand_a,
input logic [7:0] i_operand_b,
input logic [3:0] i_opcode,
input logic i_system_rst
);

logic [7:0] bitwise;
logic [8:0] check;

always_comb begin
    if (i_system_rst) begin
        o_alu_out = 8'b0;
        o_neg = 1'b0;
        o_overflow = 1'b0;
    end else begin
        case (i_opcode)
            4'b0001: begin // A + B
                check = i_operand_a + i_operand_b;
                {o_overflow, o_alu_out} = check;
                o_neg = 1'b0;
            end
            4'b0010: begin // A - B
                check = i_operand_a - i_operand_b;
                {o_neg, o_alu_out} = check;
                o_overflow = 1'b0;
            end
            4'b0011: begin // A * B
                check = i_operand_a * i_operand_b;
                {o_overflow, o_alu_out} = check;
                o_neg = 1'b0;
            end
            4'b0100: begin // A / B
                if (i_operand_b == 0) begin
                    check = 9'b0;
                    o_overflow = 1'b1;
                end else begin
                    check = i_operand_a / i_operand_b;
                    o_overflow = 1'b0;
                end
                o_alu_out = check;
                o_neg = 1'b0;
            end
        end case
    end
end
```

```

4'b0101: begin // A & B
    bitwise = i_operand_a & i_operand_b;
    o_alu_out = bitwise;
    o_neg = 1'b0;
    o_overflow = 1'b0;
end
4'b0110: begin // A | B
    bitwise = i_operand_a | i_operand_b;
    o_alu_out = bitwise;
    o_neg = 1'b0;
    o_overflow = 1'b0;
end
4'b0111: begin // A ^ B
    bitwise = i_operand_a ^ i_operand_b;
    o_alu_out = bitwise;
    o_neg = 1'b0;
    o_overflow = 1'b0;
end
4'b1000: begin // ~A
    bitwise = ~i_operand_a;
    o_alu_out = bitwise;
    o_neg = 1'b0;
    o_overflow = 1'b0;
end
default: begin
    o_alu_out = 8'b0;
    o_neg = 1'b0;
    o_overflow = 1'b0;
end
endcase
end
end

endmodule

```

4.4.9 Test Plan

| No. | Test Feature / Functionality | Test Vector Generator | Expected Outputs | Pass/Fail |
|-----|---------------------------------------|---|---|-----------|
| 1 | Addition (Normal: 10 + 20) | i_b_alu_a[7:0] = 8'd10, i_b_alu_b[7:0] = 8'd20, i_b_alu_opcode[3:0] = 4'b0001, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'd30, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |
| 2 | Addition (Overflow: 200 + 100) | i_b_alu_a[7:0] = 8'd200, i_b_alu_b[7:0] = 8'd100, i_b_alu_opcode[3:0] = 4'b0001, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'd44, o_b_alu_overflow = 1, o_b_alu_neg = 0 | pass |
| 3 | Subtraction (Normal: 50 - 30) | i_b_alu_a[7:0] = 8'd50, i_b_alu_b[7:0] = 8'd30, i_b_alu_opcode[3:0] = 4'b0010, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'd20, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |
| 4 | Subtraction (Negative: 30 - 50) | i_b_alu_a[7:0] = 8'd30, i_b_alu_b[7:0] = 8'd50, i_b_alu_opcode[3:0] = 4'b0010, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'd236, o_b_alu_overflow = 0, o_b_alu_neg = 1 | pass |
| 5 | Multiplication (Normal: 10 * 20) | i_b_alu_a[7:0] = 8'd10, i_b_alu_b[7:0] = 8'd20, i_b_alu_opcode[3:0] = 4'b0011, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'd200, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |
| 6 | Multiplication (Overflow: 16 * 16) | i_b_alu_a[7:0] = 8'd16, i_b_alu_b[7:0] = 8'd16, i_b_alu_opcode[3:0] = 4'b0011, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'd0, o_b_alu_overflow = 1, o_b_alu_neg = 0 | pass |
| 7 | Division (Normal: 100 / | i_b_alu_a[7:0] = 8'd100, i_b_alu_b[7:0] = 8'd5, i_b_alu_opcode[3:0] = | o_b_alu_cout[7:0] = 8'd20, o_b_alu_overflow = 0, | pass |

| | | | | |
|----|-------------------------------|---|--|------|
| | 5) | 4'b0100, Wait for 1 clock cycle | o_b_alu_neg = 0 | |
| 8 | Division (By Zero: 100 / 0) | i_b_alu_a[7:0] = 8'd100, i_b_alu_b[7:0] = 8'd0, i_b_alu_opcode[3:0] = 4'b0100, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'd0, o_b_alu_overflow = 1, o_b_alu_neg = 0 | pass |
| 9 | Bitwise AND | i_b_alu_a[7:0] = 8'b10101010, i_b_alu_b[7:0] = 8'b01010101, i_b_alu_opcode[3:0] = 4'b0101, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'b00000000, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |
| 10 | Bitwise OR | i_b_alu_a[7:0] = 8'b10101010, i_b_alu_b[7:0] = 8'b01010101, i_b_alu_opcode[3:0] = 4'b0110, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'b11111111, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |
| 11 | Bitwise XOR | i_b_alu_a[7:0] = 8'b10101010, i_b_alu_b[7:0] = 8'b01010101, i_b_alu_opcode[3:0] = 4'b0111, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'b11111111, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |
| 12 | Bitwise NOT | i_b_alu_a[7:0] = 8'b10101010, i_b_alu_b[7:0] = 8'd0, i_b_alu_opcode[3:0] = 4'b1000, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'b01010101, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |
| 13 | Addition (Max Value: 255 + 0) | i_b_alu_a[7:0] = 8'd255, i_b_alu_b[7:0] = 8'd0, i_b_alu_opcode[3:0] = 4'b0001, Wait for 1 clock | o_b_alu_cout[7:0] = 8'd255, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |

| | | | | |
|----|-----------------------------------|---|---|------|
| | | cycle | | |
| 14 | Subtraction (Min Value: 0 - 0) | i_b_alu_a[7:0] = 8'd0, i_b_alu_b[7:0] = 8'd0, i_b_alu_opcode[3:0] = 4'b0010, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'd0, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |
| 15 | Multiplication (Zero: 0 * 100) | i_b_alu_a[7:0] = 8'd0, i_b_alu_b[7:0] = 8'd100, i_b_alu_opcode[3:0] = 4'b0011, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'd0, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |
| 16 | Division (Zero Num: 0 / 5) | i_b_alu_a[7:0] = 8'd0, i_b_alu_b[7:0] = 8'd5, i_b_alu_opcode[3:0] = 4'b0100, Wait for 1 clock cycle | o_b_alu_cout[7:0] = 8'd0, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |
| 17 | Reset Test | i_system_rst = 1, Hold for 1 clock cycle | o_b_alu_cout[7:0] = 8'd0, o_b_alu_overflow = 0, o_b_alu_neg = 0 | pass |

4.4.10 TestBench

```
/////////////////////////////////////////////////////////////////
// Company: UTAR
// Engineer: SHU MEE ANG
// Create Date: 05/07/2025
// Module Name: tbALU
// Project Name: tbALU
/////////////////////////////////////////////////////////////////

module tb_alu8 ();
wire [7:0] tb_alu_out;
wire tb_neg;
wire tb_overflow;

logic [7:0] tb_operand_a;
logic [7:0] tb_operand_b;
logic [3:0] tb_opcode;
logic tb_system_rst;

ALU
dut_alu
(.o_alu_out (tb_alu_out),
.o_neg (tb_neg),
.o_overflow (tb_overflow),
.i_operand_a (tb_operand_a),
.i_operand_b (tb_operand_b),
.i_opcode (tb_opcode),
.i_system_rst (tb_system_rst));

bit tb_clk = 0;
initial tb_clk <= 1;
always #10 tb_clk = ~tb_clk;

initial begin
// Initialize inputs
tb_operand_a <= 8'b0;
tb_operand_b <= 8'b0;
tb_opcode <= 4'b0;
tb_system_rst <= 1'b0;

// Test 1: Addition (Normal: 10 + 20)
@(posedge tb_clk);
tb_operand_a <= 8'd10;
tb_operand_b <= 8'd20;
tb_opcode <= 4'b0001;
repeat(2) @(posedge tb_clk);

// Test 2: Addition (Overflow: 200 + 100)
@(posedge tb_clk);
tb_operand_a <= 8'd200;
tb_operand_b <= 8'd100;
tb_opcode <= 4'b0001;
repeat(2) @(posedge tb_clk);
```



```

// Test 3: Subtraction (Normal: 50 - 30)
@(posedge tb_clk);
tb_operand_a <= 8'd50;
tb_operand_b <= 8'd30;
tb_opcode <= 4'b0010;
repeat(2) @(posedge tb_clk);

// Test 4: Subtraction (Negative: 30 - 50)
@(posedge tb_clk);
tb_operand_a <= 8'd30;
tb_operand_b <= 8'd50;
tb_opcode <= 4'b0010;
repeat(2) @(posedge tb_clk);

// Test 5: Multiplication (Normal: 10 * 20)
@(posedge tb_clk);
tb_operand_a <= 8'd10;
tb_operand_b <= 8'd20;
tb_opcode <= 4'b0011;
repeat(2) @(posedge tb_clk);

// Test 6: Multiplication (Overflow: 16 * 16)
@(posedge tb_clk);
tb_operand_a <= 8'd16;
tb_operand_b <= 8'd16;
tb_opcode <= 4'b0011;
repeat(2) @(posedge tb_clk);

// Test 7: Division (Normal: 100 / 5)
@(posedge tb_clk);
tb_operand_a <= 8'd100;
tb_operand_b <= 8'd5;
tb_opcode <= 4'b0100;
repeat(2) @(posedge tb_clk);

// Test 8: Division (By Zero: 100 / 0)
@(posedge tb_clk);
tb_operand_a <= 8'd100;
tb_operand_b <= 8'd0;
tb_opcode <= 4'b0100;
repeat(2) @(posedge tb_clk);

// Test 9: Bitwise AND
@(posedge tb_clk);
tb_operand_a <= 8'b10101010;
tb_operand_b <= 8'b01010101;
tb_opcode <= 4'b0101;
repeat(2) @(posedge tb_clk);

// Test 10: Bitwise OR
@(posedge tb_clk);
tb_operand_a <= 8'b10101010;
tb_operand_b <= 8'b01010101;
tb_opcode <= 4'b0110;
repeat(2) @(posedge tb_clk);

```

```

// Test 11: Bitwise XOR
@(posedge tb_clk);
tb_operand_a <= 8'b10101010;
tb_operand_b <= 8'b01010101;
tb_opcode <= 4'b0111;
repeat(2) @(posedge tb_clk);

// Test 12: Bitwise NOT
@(posedge tb_clk);
tb_operand_a <= 8'b10101010;
tb_operand_b <= 8'd0;
tb_opcode <= 4'b1000;
repeat(2) @(posedge tb_clk);

// Test 13: Addition (Max Value: 255 + 0)
@(posedge tb_clk);
tb_operand_a <= 8'd255;
tb_operand_b <= 8'd0;
tb_opcode <= 4'b0001;
repeat(2) @(posedge tb_clk);

// Test 14: Subtraction (Min Value: 0 - 0)
@(posedge tb_clk);
tb_operand_a <= 8'd0;
tb_operand_b <= 8'd0;
tb_opcode <= 4'b0010;
repeat(2) @(posedge tb_clk);

// Test 15: Multiplication (Zero: 0 * 100)
@(posedge tb_clk);
tb_operand_a <= 8'd0;
tb_operand_b <= 8'd100;
tb_opcode <= 4'b0011;
repeat(2) @(posedge tb_clk);

// Test 16: Division (Zero Num: 0 / 5)
@(posedge tb_clk);
tb_operand_a <= 8'd0;
tb_operand_b <= 8'd5;
tb_opcode <= 4'b0100;
repeat(2) @(posedge tb_clk);

// Test 17: Reset Test
@(posedge tb_clk);
tb_system_rst <= 1'b1;
repeat(2) @(posedge tb_clk);
tb_system_rst <= 1'b0;


// Delay to settle outputs
repeat(10) @(posedge tb_clk);
$stop;
end

endmodule


```

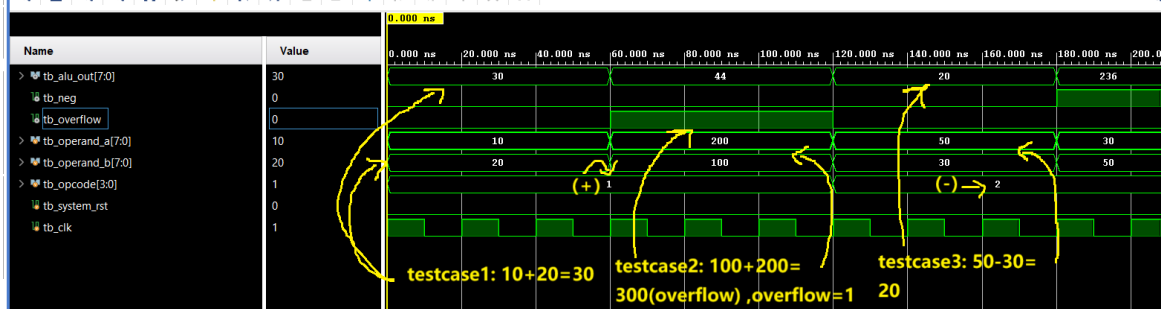4.4.11 Result Simulation


// Test 1: Addition (Normal: $10 + 20$)
 // Test 2: Addition (Overflow: $200 + 100$)
 // Test 3: Subtraction (Normal: $50 - 30$)



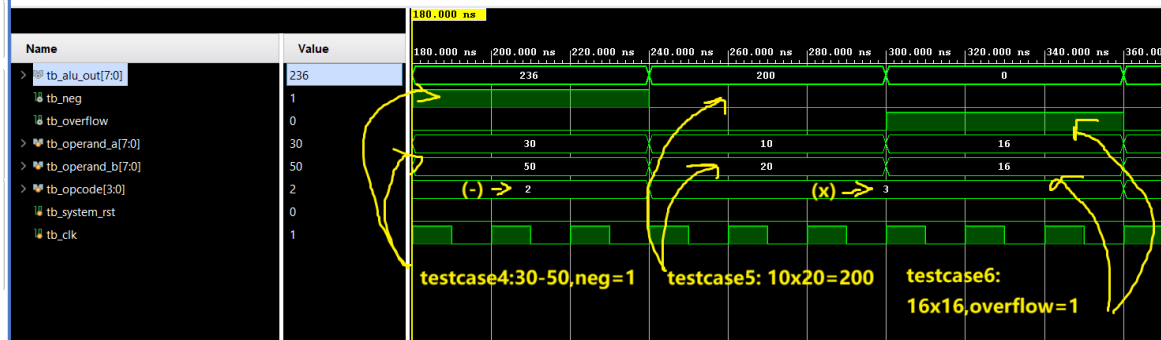
// Test 4: Subtraction (Negative: $30 - 50$)
 // Test 5: Multiplication (Normal: $10 * 20$)
 // Test 6: Multiplication (Overflow: $16 * 16$)



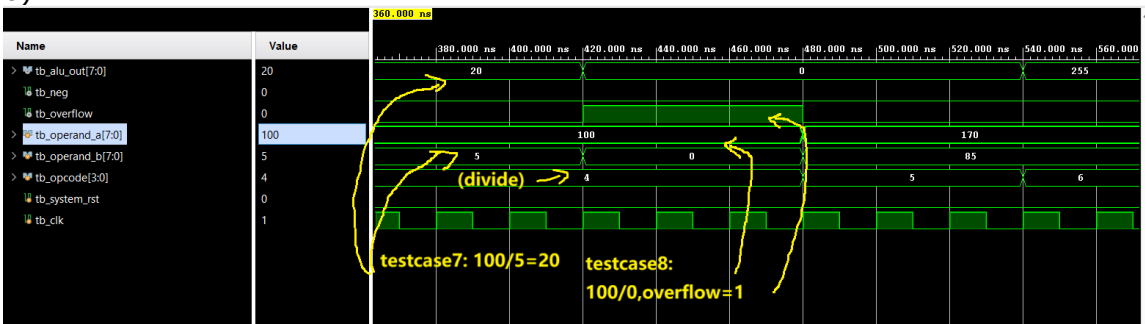// Test 7: Division (Normal: $100 / 5$)
 // Test 8: Division (By Zero: $100 / 0$)



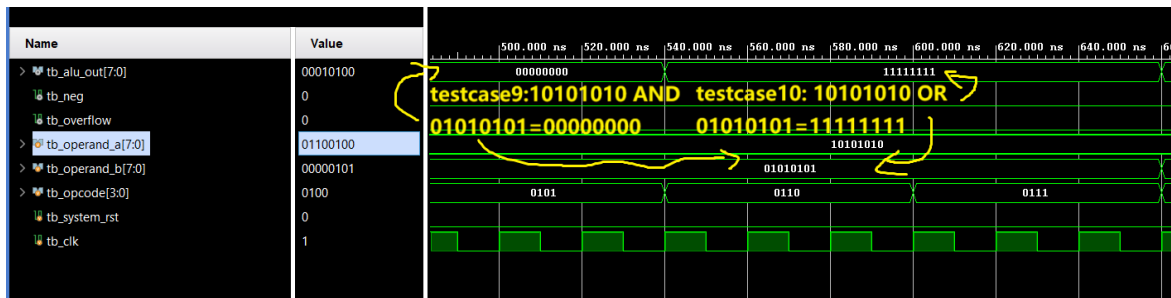
// Test 9: Bitwise AND
 // Test 10: Bitwise OR



// Test 11: Bitwise XOR

// Test 12: Bitwise

NOT

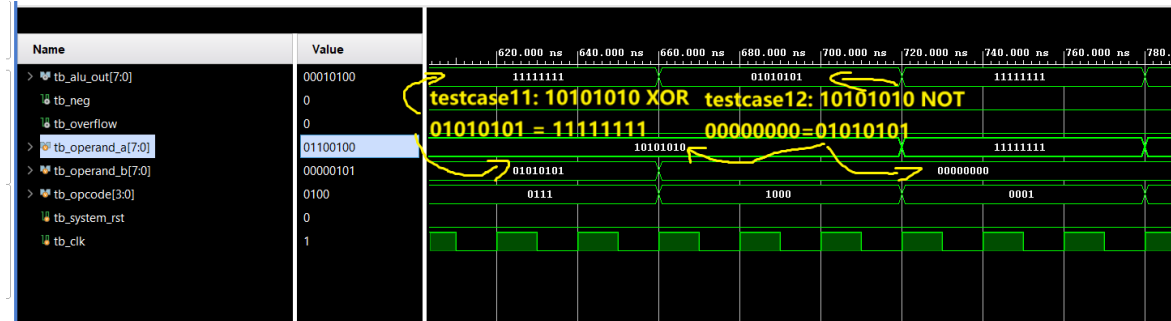


// Test 13: Addition (Max Value: 255 + 0)

// Test 14: Subtraction (Min Value: 0 - 0)

// Test 15: Multiplication (Zero: 0 *


100)

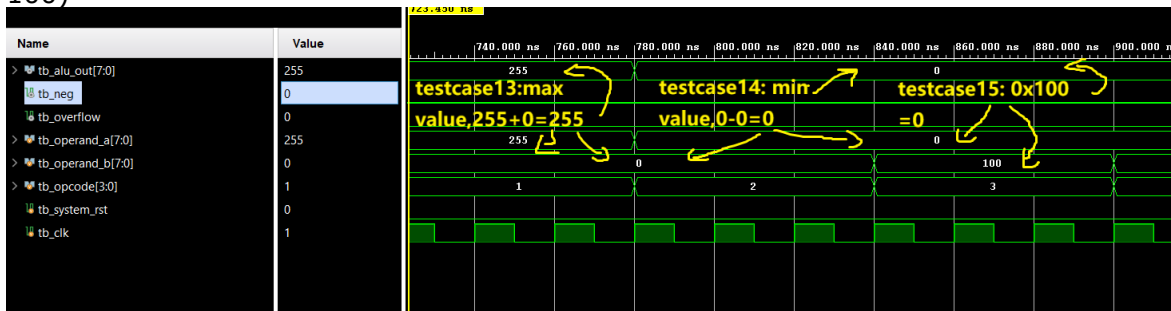

// Test 16: Division (Zero Num: 0 / 5)

// Test 17: Reset

Test

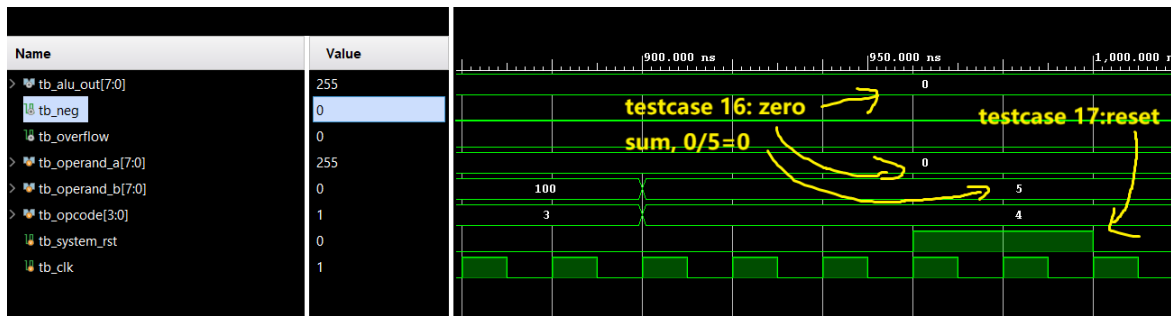

4.5 Barrel Shifter


4.5.1 Functionality

- Accepts an 8-bit input word and a 3-bit shift amount.
- Uses a single combinational pass (one “cycle” of logic) to produce the result.
- When shift to the left, moves each bit toward the MSB and fills vacated LSB positions with 0.
- When shift to the right, moves each bit toward the LSB and fills vacated MSB positions with 0.
- Does not use any built-in shift operators
- Implements shifts via a tree of multiplexers.

4.5.2 Features

- Bidirectional: supports both logical left and logical right shifts.
- Variable amount: shift distance from 0 to 7 via a 3-bit control.
- Zero-fill: always inserts zeros into the newly vacated bit positions.
- Purely combinational: no flip-flops or latches—outputs change immediately with inputs.
- Single-cycle latency: the entire shift completes in one layer of logic.
- Mux-tree implementation: uniform, predictable delay across shifting stages.

4.5.3 Block Interface

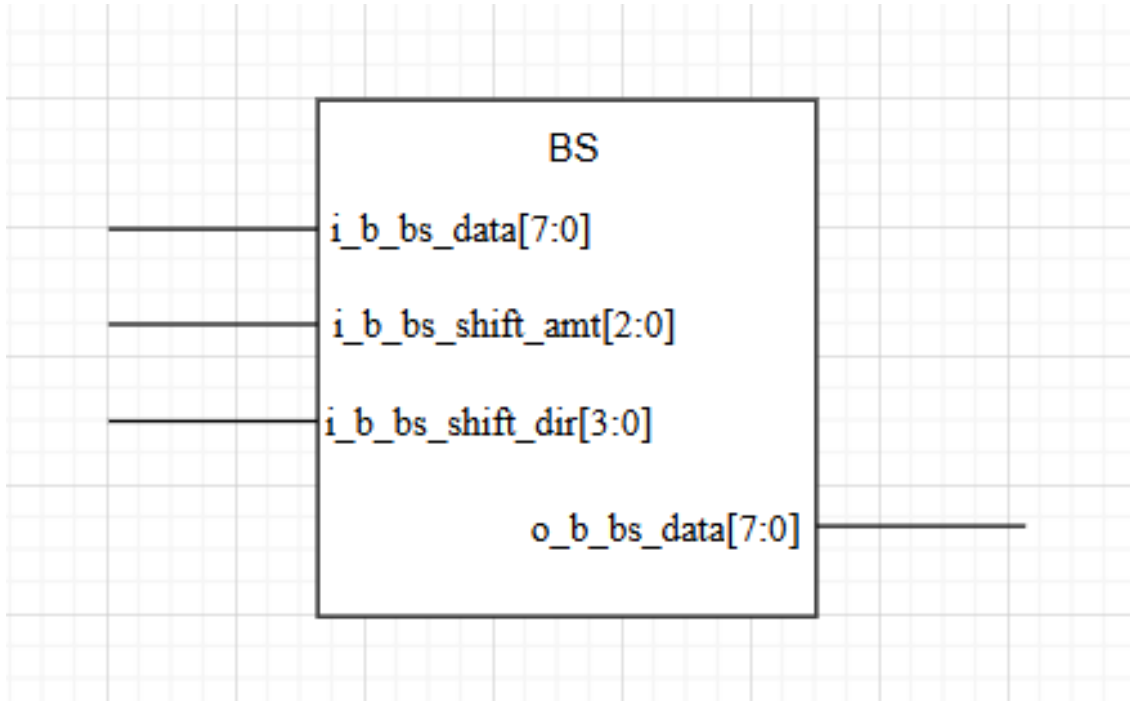

4.5.4 I/O Pin Description

| Pin Name | Pin Class | Pin Direction | Source to Destination | Pin Function |
|-----------------------|-----------|---------------|-----------------------|--------------------------------|
| i_b_bs_data[7:0] | data | input | CON to BS | 8-bit input data to be shifted |
| i_b_bs_shift_amt[2:0] | data | input | CON to BS | Shift amount of input data |
| i_b_bs_shift_dir[3:0] | control | input | CON to BS | Shift direction of input data |
| o_b_bs_data[7:0] | data | output | BS to IOD | 8-bit shifted output data |


4.4.5 Internal Operation

| i_b_bs_data[7:0] | i_b_bs_shift_amt[2:0] | i_b_bs_shift_dir[3:0] | o_b_bs_data[7:0] | Function Description |
|------------------|-----------------------|-----------------------|------------------|-------------------------------------|
| 8'b00011111 | 3'b000 (0 bit) | 4'b1001 (left) | 8'b00011111 | Logical left shift by 0 (No Shift) |
| 8'b00011111 | 3'b001 (1 bit) | 4'b1001 | 8'b00111110 | Logical left shift by 1 |
| 8'b00011111 | 3'b011 (3 bit) | 4'b1001 | 8'b11111000 | Logical left shift by 3 |
| 8'b00011111 | 3'b111 (7 bit) | 4'b1001 | 8'b10000000 | Logical left shift by 7 |
| 8'b11111000 | 3'b000 (0 bit) | 4'b1010 (right) | 8'b11111000 | Logical right shift by 0 (No Shift) |
| 8'b11111000 | 3'b001 (1 bit) | 4'b1010 | 8'b01111100 | Logical right shift by 1 |
| 8'b11111000 | 3'b011 (3 bit) | 4'b1010 | 8'b00011111 | Logical right shift by 3 |

| | | | | |
|-------------|-------------------|---------|-------------|--------------------------|
| 8'b11111000 | 3'b111 (7 bit) | 4'b1010 | 8'b00000001 | Logical right shift by 7 |
|-------------|-------------------|---------|-------------|--------------------------|

4.5.6 Timing Requirement

Barrel Shifter

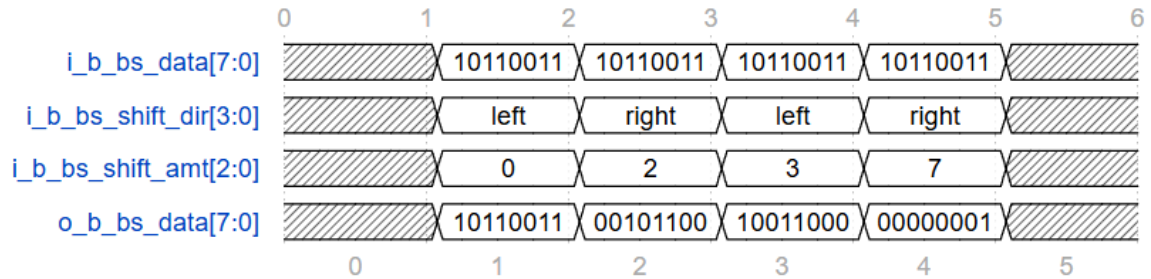

Timing Diagram

Predesign



4.5.8 Vivado Model

```
////////////////////////////////////  
  
//company : UTAR  
  
//Engineer: JAYSON CHEN MIN XIANG  
  
// CREATE DATE :07/05/2025  
  
//MODULE NAME: BS  
  
//PROJECT NAME :BS  
  
////////////////////////////////////  
module BS  
(  
    input logic[7:0]  i_b_bs_data,  
    input logic[2:0]  i_b_bs_shift_amt,  
    input logic[3:0]  i_b_bs_shift_dir,  
    output logic[7:0] o_b_bs_data  
);  
  
localparam left = 4'b1001; //the opcode for logical left shift  
localparam right = 4'b1010; //the opcode for logical left shift  
  
logic [7:0] temp_left [0:3];  
logic [7:0] temp_right [0:3];  
  
// Left shift logic  
assign temp_left[0] = i_b_bs_data;  
always_comb begin
```

```

    for (int col = 0; col < 3; col++) begin
        for (int row = 0; row < 8; row++) begin
            if (row < (2 ** col)) begin
                temp_left[col+1][row] = i_b_bs_shift_amt[col] ? 1'b0 :
temp_left[col][row];
            end else begin
                temp_left[col+1][row] = i_b_bs_shift_amt[col] ? temp_left[col][row - (2
** col)] : temp_left[col][row];
            end
        end
    end
end

// Right shift logic
assign temp_right[0] = i_b_bs_data;
always_comb begin
    for (int col = 0; col < 3; col++) begin
        for (int row = 0; row < 8; row++) begin
            if (row >= 8 - (2 ** col)) begin
                temp_right[col+1][row] = i_b_bs_shift_amt[col] ? 1'b0 :
temp_right[col][row];
            end else begin
                temp_right[col+1][row] = i_b_bs_shift_amt[col] ? temp_right[col][row
+ (2 ** col)] : temp_right[col][row];
            end
        end
    end
end

always_comb begin
    case (i_b_bs_shift_dir)

```

```

left: o_b_bs_data = temp_left[3];

right: o_b_bs_data = temp_right[3];

default: o_b_bs_data = 8'b0; // for invalid direction

endcase

end

endmodule

```

4.5.9 Test Plan

| No | Test Case | Description of Test Vector Generation | Expected Operation | Status |
|----|--------------------------|---|-----------------------------------|--------|
| 1 | System initialization | i_b_bs_data[7:0]: 4'b00000000 i_b_bs_shift_amt[2:0]: 3'b000 i_b_bs_shift_dir[3:0]: 4'b0000 | -o_b_bs_data[7:0]: 8'b00000000 | pass |
| 2 | Left shift by 1 | i_b_bs_data[7:0]: 4'b00000001 i_b_bs_shift_amt[2:0]: 3'b001 i_b_bs_shift_dir[3:0]: 4'b1001 (left) | o_b_bs_data[7:0]: 8'b00000010 | pass |
| 3 | Left shift by 7 | i_b_bs_data[7:0]: 8'b00000001 i_b_bs_shift_amt[2:0]: 3'b111 i_b_bs_shift_dir[3:0]: 4'b1001 (left) | o_b_bs_data[7:0]: 8'b10000000 | pass |
| 4 | Right shift by 1 | i_b_bs_data[7:0]: 8'b10000000 i_b_bs_shift_amt[2:0]: 3'b111 i_b_bs_shift_dir[3:0]: 4'b1010(right) | o_b_bs_data[7:0]: 8'b01000000 | pass |
| 5 | Right shift by 7 | i_b_bs_data[7:0]: 8'b10000000 i_b_bs_shift_amt[2:0]: 3'b111 i_b_bs_shift_dir[3:0]: 4'b1010(right) | o_b_bs_data[7:0]: 8'b00000001 | pass |
| 6 | Pattern left shift by 2 | i_b_bs_data[7:0]: 8'b10101010 i_b_bs_shift_amt[2:0]: 3'b010 i_b_bs_shift_dir[3:0]: 4'b1001(left) | o_b_bs_data[7:0]: 8'b10101000 | pass |
| 7 | Pattern right shift by 3 | i_b_bs_data[7:0]: 8'b10101010 i_b_bs_shift_amt[2:0]: 3'b011 i_b_bs_shift_dir[3:0]: 4'b1010(right) | o_b_bs_data[7:0]: 8'b00010101 | pass |
| 8 | No shift | i_b_bs_data[7:0]: 8'b11111111 i_b_bs_shift_amt[2:0]: 3'b000 | o_b_bs_data[7:0]: 8'b11111111 | pass |

| | | | | |
|----|--------------------------------|---|----------------------------------|------|
| | | i_b_bs_shift_dir[3:0]:4'b1001(right) //wait for 1 clock cycle | | |
| 9 | Invalid shift direction | i_b_bs_data[7:0]:8'b10101010 i_b_bs_shift_amt[2:0]: 3'b010 i_b_bs_shift_dir[3:0]:4'b1000 | o_b_bs_data[7:0]: 8'b00000000 | pass |
| 10 | No shift and invalid direction | i_b_bs_data[7:0]:8'b10101010 i_b_bs_shift_amt[2:0]: 3'b000 i_b_bs_shift_dir[3:0]:4'b1000 | o_b_bs_data[7:0]: 8'b00000000 | pass |
| 11 | Maximum left shift test | i_b_bs_data[7:0]:8'b11111111 i_b_bs_shift_amt[2:0]: 3'b111 i_b_bs_shift_dir[3:0]:4'b1001(left) | o_b_bs_data[7:0]: 8'b10000000 | pass |
| 12 | Maximum right shift test | i_b_bs_data[7:0]:8'b11111111 i_b_bs_shift_amt[2:0]: 3'b111 i_b_bs_shift_dir[3:0]:4'b1010(right) | o_b_bs_data[7:0]: 8'b00000001 | pass |

4.5.10 TestBench

```
////////////////////////////////////
```

```
//company : UTAR
```

```
//Engineer: JAYSON CHEN MIN XIANG
```

```
// CREATE DATE :07/05/2025
```

```
//MODULE NAME: tb_BS
```

```
//PROJECT NAME :tb_BS
```

```
////////////////////////////////////
```

```
`define PERIOD_CLK 10
```

```
module BS_tb;
```

```

// Inputs
logic [3:0] i_b_bs_shift_dir;
logic [7:0] i_b_bs_data;
logic [2:0] i_b_bs_shift_amt;

// Outputs
wire [7:0] o_b_bs_data;

// Instantiate DUT
BS dut (
    .i_b_bs_shift_dir (i_b_bs_shift_dir),
    .i_b_bs_data      (i_b_bs_data),
    .i_b_bs_shift_amt (i_b_bs_shift_amt),
    .o_b_bs_data      (o_b_bs_data)
);

// Test stimulus

initial begin

// Default inputs

i_b_bs_shift_dir = 4'b0000;

i_b_bs_data = 8'h00;

i_b_bs_shift_amt = 3'b000;

// Wait out reset

```

```

#(`PERIOD_CLK * 5);

// 2) Left shift by 1
i_b_bs_shift_dir = 4'b1001;
i_b_bs_data      = 8'b00000001;
i_b_bs_shift_amt = 3'b001;
#(`PERIOD_CLK * 2);

// 3) Left shift by 7
i_b_bs_data      = 8'b00000001;
i_b_bs_shift_amt = 3'b111;
#(`PERIOD_CLK * 2);

// 4) Right shift by 1
i_b_bs_shift_dir = 4'b1010;
i_b_bs_data      = 8'b10000000;
i_b_bs_shift_amt = 3'b001;
#(`PERIOD_CLK * 2);

// 5) Right shift by 7
i_b_bs_data      = 8'b10000000;
i_b_bs_shift_amt = 3'b111;
#(`PERIOD_CLK * 2);

// 6) Pattern left shift by 2
i_b_bs_shift_dir = 4'b1001;
i_b_bs_data      = 8'b10101010;
i_b_bs_shift_amt = 3'b010;
#(`PERIOD_CLK * 2);

// 7) Pattern right shift by 3

```

```

i_b_bs_shift_dir = 4'b1010;
i_b_bs_shift_amt = 3'b011;
#(`PERIOD_CLK * 2);

// 8) No shift
i_b_bs_shift_dir = 4'b1001;
i_b_bs_shift_amt = 3'b000;
i_b_bs_data      = 8'hFF;
#(`PERIOD_CLK * 2);

// 9) invalid shift direction
i_b_bs_shift_dir = 4'b1000;
i_b_bs_data      = 8'b10101010;
i_b_bs_shift_amt = 3'b010;
#(`PERIOD_CLK * 2);

// 10) no shift and invalid direction
i_b_bs_shift_dir = 4'b1000;
i_b_bs_data      = 8'b10101010;
i_b_bs_shift_amt = 3'b000;
#(`PERIOD_CLK * 2);

// 11) Maximum shift test (Left and Right)
i_b_bs_shift_dir = 4'b1001;
i_b_bs_data      = 8'b11111111;
i_b_bs_shift_amt = 3'b111;
#(`PERIOD_CLK * 2);

i_b_bs_shift_dir = 4'b1010;
i_b_bs_data      = 8'b11111111;
i_b_bs_shift_amt = 3'b111;

```

```
#(`PERIOD_CLK * 2);
```

```
$finish;
```

```
end
```

```
endmodule
```

4.5.11 Test Result Timing Diagram

Each figure provided represents a test case that is provided in the **4.4.9 test plan**. The figures provide the name, their values and waveform of the input and output of their respective test case.

 


Figure 4.4.11.1: The Entire overall Timing Diagram

 


Figure 4.4.11.2: System Initialization

 


Figure 4.4.11.3: left shift by 1

 


Figure 4.4.11.4: left shift by 7

 


Figure 4.4.11.5: right shift by 1

 


Figure 4.4.11.6: right shift by 7

 


Figure 4.4.11.7: pattern left shift by 2

 


Figure 4.4.11.8: pattern right shift by 3

 


Figure 4.4.11.9: no shift

 


Figure 4.4.11.10: invalid shift direction

 


Figure 4.4.11.11: no shift and invalid shift direction

 


Figure 4.4.11.12: maximum left shift

 


Figure 4.4.11.13: maximum right shift

4.6 Input / Output Conversion


4.6.1 Functionality

- Display Input Digit by Digit
- convert Binary into BCD
- Convert BCD into 7Segment Display Decoder
- Error Handling for Results
- Real-Time Synchronization
- Reset Mechanism

4.6.2 Features

- Operates with 8-bit Integers
- Supports Input and Output via Hex Keypad and 7-Segment Display
- Binary Conversion Capabilities
- Error Handling
- Sign Handling
- Screen Clear Mechanism

4.6.3 Block Interface

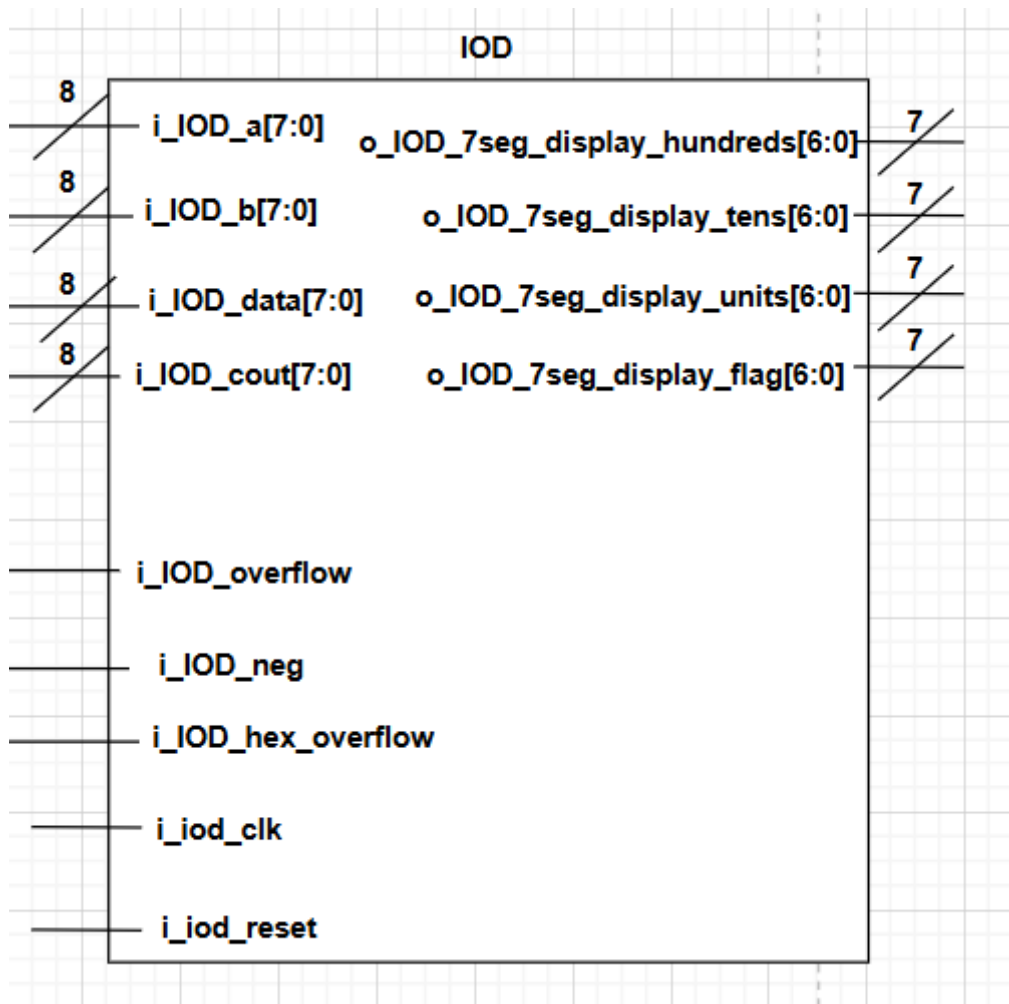

4.6.4 I/O Pin Description

| Pin Name | Pin Class | Pin Direction | Source to direction | Pin Function |
|------------------------------|-----------------|---------------|--------------------------|--|
| i_b_iod_a | data | input | CON to IOD | Carry 8-bit binary input from the hexpad |
| I_b_iod_b | data | input | CON to IOD | Carry 8-bit binary input from hexpad |
| i_b_iod_cout | data | input | ALU to IOD | Computation result from the ALU |
| I_b_iod_data | data | input | BS to IOD | Computation result from the barrier shifter |
| i_b_iod_opcode | data | input | CON to IOD | Determine to display result from ALU or display result from barrier shifter |
| i_b_iod_overflow | data | input | ALU to IOD | Overflow flag from the ALU indicating arithmetic overflow. |
| i_b_iod_neg | data | input | ALU to IOD | Negative result flag from the ALU indicating a subtraction result is negative. |
| i_b_iod_hex_overflow | control | input | CON to IOD | Overflow flag from the hexpad indicating arithmetic overflow. |
| i_system_clk | global, control | input | Clock to IOD | Clock signal for synchronizing operations. |
| i_system_reset | global, control | input | Reset button to IOD | Asynchronous reset signal to clear stored results and reset the system. |
| o_b_iod_7seg_hundreds | data | output | IOD to 7-segment display | Display signal for the hundreds digit on the 7-segment display. |
| o_b_iod_7seg_tens | data | output | IOD to 7-segment display | Display signal for the tens digit on the 7-segment display. |
| o_b_iod_7seg_units | data | output | IOD to 7-segment display | Display signal for the units digit on the 7-segment display. |
| o_b_iod_7seg_flags | data | output | IOD to 7-segment display | Signal to indicate errors (e.g., overflow, negative symbol, etc.). |

4.6.5 Internal operation

Binary code from hexpad

| Key | binary code |
|---------------------|-------------|
| + | 4'b0001 |
| - | 4'b0010 |
| * | 4'b0011 |
| / | 4'b0100 |
| & | 4'b0101 |
| | 4'b0110 |
| ^ | 4'b0111 |
| ~ | 4'b1000 |
| << | 4'b1001 |
| >> | 4'b1010 |
| First key in value | 4'b1111 |
| Second key in value | 4'b1110 |
| No key | 4'b0000 |

7-segment display table

| 7-Segment Output (7-bit) | Display |
|--------------------------|---------|
| 0111111 | 0 |
| 0000110 | 1 |
| 1011011 | 2 |
| 1001111 | 3 |
| 1100110 | 4 |
| 1101101 | 5 |
| 1111101 | 6 |
| 0000111 | 7 |
| 1111111 | 8 |
| 1101111 | 9 |
| 1000000 | - |
| 1111001 | E |
| 0000000 | default |

Example table


| | 22+75 | 2<<4 | Display a(22) | Display b(75) |
|-----------------------|-----------------|-----------------|-----------------|-----------------|
| i_b_iod_a | 8b'00010110(22) | 8b'00000010(2) | 8b'00010110(22) | 8b'00000000 |
| I_b_iod_b | 8b'01001011(75) | 8b'00000100(4) | 8b'00000000 | 8b'01001011(75) |
| i_b_iod_cout | 8b'01100001(97) | 8b'00000000 | 8b'00000000 | 8b'00000000 |
| I_b_iod_data | 8b'00000000 | 8b'00100000(32) | 8b'00000000 | 8b'00000000 |
| i_b_iod_opcode | 4'b0001(+) | 4'b1001(<<) | 4'b1111 | 4'b1110 |

| | | | | |
|------------------------------|----------------|----------------|----------------|----------------|
| i_b_iod_overflow | 0 | 0 | 0 | 0 |
| i_b_iod_neg | 0 | 0 | 0 | 0 |
| i_b_iod_hex_overflow | 0 | 0 | 0 | 0 |
| i_system_reset | 0 | 0 | 0 | 0 |
| o_b_iod_7seg_flags | 0000000 | 0000000 | 0000000 | 0000000 |
| o_b_iod_7seg_hundreds | 0111111(0) | 0111111(0) | 0111111(0) | 0111111(0) |
| o_b_iod_7seg_tens | 1101111 (9) | 1001111 (3) | 1011011 (2) | 0000111 (7) |
| o_b_iod_7seg_units | 0000111(7) | 1011011 (2) | 1011011 (2) | 1101101 (5) |

Example table


| | Hex_overflow | overflow | Neg(22-75) | reset |
|------------------------------|---------------------|-----------------|---------------------|--------------|
| i_b_iod_a | 8b'00000000 | 8b'00000000 | 8b'00010110(22) | 8b'00000000 |
| I_b_iod_b | 8b'00000000 | 8b'00000000 | 8b'01001011(75) | 8b'00000000 |
| i_b_iod_cout | 8b'00000000 | 8b'00000000 | 8b'01100001 (53) | 8b'00000000 |
| I_b_iod_data | 8b'00000000 | 8b'00000000 | 8b'00000000 | 8b'00000000 |
| i_b_iod_opcode | 4'b0000 | 4'b0000 | 4'b 0010(-) | 4'b0000 |
| i_b_iod_overflow | 0 | 1 | 0 | 0 |
| i_b_iod_neg | 0 | 0 | 1 | 0 |
| i_b_iod_hex_overflow | 1 | 0 | 0 | 0 |
| i_system_reset | 0 | 0 | 0 | 1 |
| o_b_iod_7seg_flags | 1111001(E) | 1111001(E) | 1000000(-) | 0000000 |
| o_b_iod_7seg_hundreds | 0111111(0) | 0111111 (0) | 0111111 (0) | 0000000 |
| o_b_iod_7seg_tens | 0111111 (0) | 0111111 (0) | 1101101 (5) | 0000000 |
| o_b_iod_7seg_units | 0111111 (0) | 0111111 (0) | 1001111(3) | 0000000 |

4.6.6 Timing Requirement

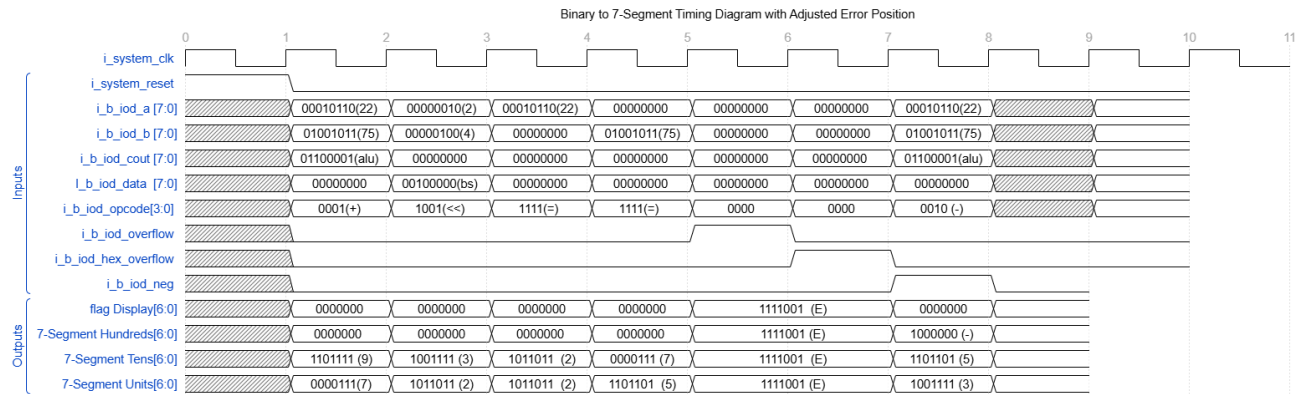


4.6.7 Schematic

Pre schematic

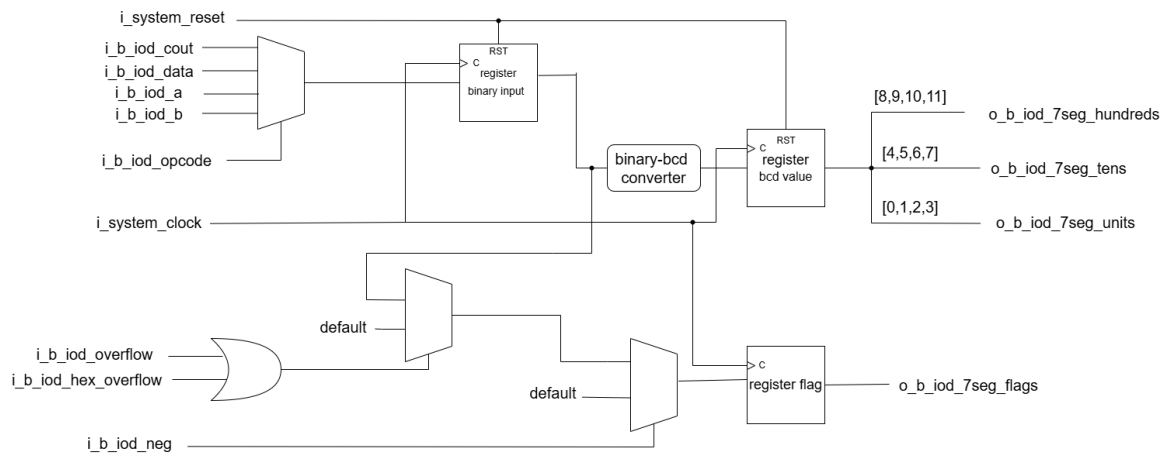

Post schematic

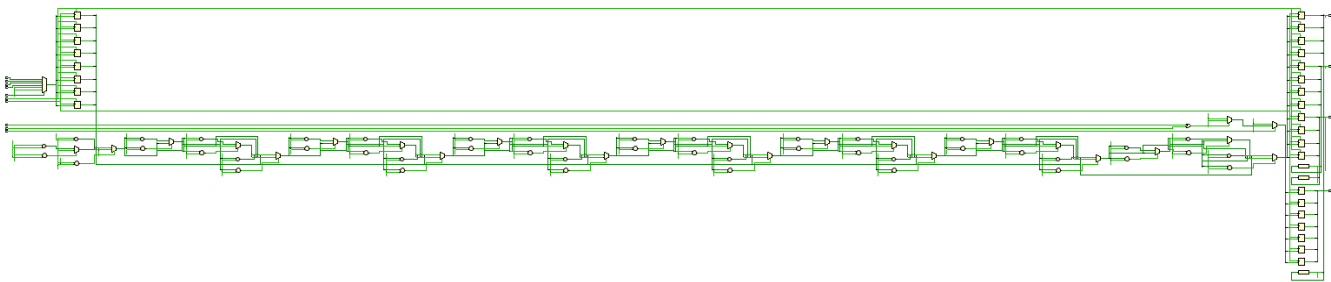

4.6.8 Vivado Model

```

////////////////////////////////////
//company : UTAR
//Engineer: CHONG BING HONG
// CREATE DATE :07/05/2025
//MODULE NAME:IOD
//PROJECT NAME :IOD
////////////////////////////////////

```

```

module iod(

```

```

//input
input i_system_clk,
input i_system_reset,
input i_b_iod_overflow,
input i_b_iod_neg,
input i_b_iod_hex_overflow,
input [7:0] i_b_iod_a,
input [7:0] i_b_iod_b,
input [7:0] i_b_iod_data,
input [7:0] i_b_iod_cout,
input [3:0] i_b_iod_opcode,

//output
output logic[6:0] o_b_iod_7seg_hundreds,
output logic[6:0] o_b_iod_7seg_tens,
output logic[6:0] o_b_iod_7seg_units,
output [6:0] o_b_iod_7seg_flags);

//reg
logic [7:0] binary_input;
logic [19:0] shift_reg;
logic [6:0] flag_display;
logic [11:0] bcd_value;

// select a, b, result ALU, result barrirer
// Select computation result based on opcode

always_ff @(posedge i_system_clk) begin
    if (i_system_reset) binary_input <= 8'h0;
    else begin

        case (i_b_iod_opcode)
            4'b0001, 4'b0010, 4'b0011, 4'b0100, 4'b0101,
            4'b0110, 4'b0111, 4'b1000: binary_input <= i_b_iod_cout;
            4'b1001, 4'b1010: binary_input <= i_b_iod_data;
            4'b1111: binary_input <= i_b_iod_a;
            4'b1110: binary_input <= i_b_iod_b;
            4'b0000: binary_input <= 8'b00000000;
            default: binary_input <= 8'b00000000;
        endcase
    end
end

//binary to bcd
always_ff @(posedge i_system_clk) begin
    if (i_system_reset) begin
        bcd_value <= 12'b00000000000000;
        flag_display <= 7'b00000000;
    end else begin

        // Initialize variables
        integer i;
        shift_reg = {12'b00000000000000, binary_input};

        // Shift & Add-3 algorithm for Binary to BCD conversion
        for (i = 0; i < 8; i = i + 1) begin

```



```

    // Correct BCD digits BEFORE shifting
    if (shift_reg[19:15] >= 5)
        shift_reg[19:15] = shift_reg[19:15] + 3;
    if (shift_reg[15:12] >= 5)
        shift_reg[15:12] = shift_reg[15:12] + 3;
    if (shift_reg[11:8] >= 5)
        shift_reg[11:8] = shift_reg[11:8] + 3;

    // Shift left by 1 bit while retaining the LSB
    shift_reg = {shift_reg[18:0], binary_input[7-i]};
end

// Assign final BCD values
bcd_value <= shift_reg[19:8];

end

// Handling Negative and Overflow
if (i_b_iod_neg)
    flag_display <= 7'b1000000; // "-" sign
else if (i_b_iod_overflow || i_b_iod_hex_overflow)
    flag_display <= 7'b1111001; // "E" error signal
else
    flag_display <= 7'b0000000; // Default no error
end

always_comb begin

//7-seg output
    case (bcd_value[11:8])
        4'b0000: o_b_iod_7seg_hundreds = 7'b0111111; // "0"
        4'b0001: o_b_iod_7seg_hundreds = 7'b0000110; // "1"
        4'b0010: o_b_iod_7seg_hundreds = 7'b1011011; // "2"
        4'b0011: o_b_iod_7seg_hundreds = 7'b1001111; // "3"
        4'b0100: o_b_iod_7seg_hundreds = 7'b1100110; // "4"
        4'b0101: o_b_iod_7seg_hundreds = 7'b1101101; // "5"
        4'b0110: o_b_iod_7seg_hundreds = 7'b1111101; // "6"
        4'b0111: o_b_iod_7seg_hundreds = 7'b0000111; // "7"
        4'b1000: o_b_iod_7seg_hundreds = 7'b1111111; // "8"
        4'b1001: o_b_iod_7seg_hundreds = 7'b1101111; // "9"
        default: o_b_iod_7seg_hundreds = 7'b0000000; // Blank display
    endcase

    case (bcd_value[7:4])
        4'b0000: o_b_iod_7seg_tens = 7'b0111111;
        4'b0001: o_b_iod_7seg_tens = 7'b0000110;
        4'b0010: o_b_iod_7seg_tens = 7'b1011011;
        4'b0011: o_b_iod_7seg_tens = 7'b1001111;
        4'b0100: o_b_iod_7seg_tens = 7'b1100110;
        4'b0101: o_b_iod_7seg_tens = 7'b1101101;
        4'b0110: o_b_iod_7seg_tens = 7'b1111101;
        4'b0111: o_b_iod_7seg_tens = 7'b0000111;
        4'b1000: o_b_iod_7seg_tens = 7'b1111111;
        4'b1001: o_b_iod_7seg_tens = 7'b1101111;
        default: o_b_iod_7seg_tens = 7'b0000000;
    endcase
end

```

```

case (bcd_value[3:0])
  4'b0000: o_b_iod_7seg_units = 7'b0111111;
  4'b0001: o_b_iod_7seg_units = 7'b0000110;
  4'b0010: o_b_iod_7seg_units = 7'b1011011;
  4'b0011: o_b_iod_7seg_units = 7'b1001111;
  4'b0100: o_b_iod_7seg_units = 7'b1100110;
  4'b0101: o_b_iod_7seg_units = 7'b1101101;
  4'b0110: o_b_iod_7seg_units = 7'b1111101;
  4'b0111: o_b_iod_7seg_units = 7'b0000111;
  4'b1000: o_b_iod_7seg_units = 7'b1111111;
  4'b1001: o_b_iod_7seg_units = 7'b1101111;
  default: o_b_iod_7seg_units = 7'b0000000;
endcase

end

//assign value(not necessarily)
assign o_b_iod_7seg_hundreds = bcd_value[11:8];
assign o_b_iod_7seg_tens = bcd_value[7:4];
assign o_b_iod_7seg_units = bcd_value[3:0];
assign o_b_iod_7seg_flags = flag_display;

endmodule

```

4.6.9 Test Plan

| No | Test Case | Description of Test Vector Generation | Expected Operation | Status |
|----|-----------------------|--|---|--------|
| 1 | Reset | i_b_iod_reset = 1, Wait for 4 clock cycle, I_b_iod_reset=0 | //display o_iod_7seg_flags=7'b00000000, o_iod_7seg_hundreds=7'b00000000, o_iod_7seg_tens=7'b00000000, o_iod_7seg_units=7'b00000000 | pass |
| 2 | Display first number | /a=110, I_b_opcode= 4'b1111, I_b_iod_a= 8' b01101110, //Wait for 10 clock cycle | //display o_b_iod_7seg_flags=7'b00000000, o_b_iod_7seg_hundreds=7'b0000110, o_b_iod_7seg_tens =7'b0000110, o_b_iod_7seg_units =7'b0111111 | pass |
| 3 | Display second number | //b=28, i_b_iod_opcode = 4'b1110; i_b_iod_b=8'b00011100; //Wait for 10 clock cycle | //display o_b_iod_7seg_flags=7'b00000000, o_b_iod_7seg_hundreds=7'b0111111, o_b_iod_7seg_tens =7'b1011011, o_b_iod_7seg_units =7'b1111111, | pass |

| | | | | |
|---|---------------------------|--|--|------|
| | | i_b_iod_b=8'b00000000; | | |
| 4 | ALU operation | //cout=125,opcode=- tb_b_iod_opcode = 4'b0010, tb_b_iod_cout= 8'b1111101, Wait for 10 clock cycle, i_b_iod_opcode = 4'b0000; i_b_iod_cout= 8'b00000000; | //display o_b_iod_7seg_flags=7'b00000000, o_b_iod_7seg_hundreds=7'b0000110, o_b_iod_7seg_tens =7'b1011011, o_b_iod_7seg_units =7'b1101101, | pass |
| 5 | Barrier shifter operation | //data=114, opcode=<< i_b_iod_opcode =4'b1001; i_b_iod_data= 8'b1110010; //Wait for 10 clock cycle i_b_iod_opcode = 4'b0000; i_b_iod_data= 8'b00000000; | //display o_b_iod_7seg_flags=7'b00000000, o_b_iod_7seg_hundreds=7'b0000110, o_iod_7seg_tens =7'b0000110, o_iod_7seg_units =7'b1100110, | pass |
| 6 | Negative Result | //neg=1, //opcode=-,cout=50 i_b_iod_neg =1; i_b_iod_opcode = 4'b0010; i_b_iod_cout= 8'b00110010; //Wait for 2 clock cycle i_b_iod_neg =0; i_b_iod_opcode = 4'b0000; i_b_iod_cout= 8'b00000000; | //display o_b_iod_7seg_flags=7'b10000000, o_b_iod_7seg_hundreds=7'b0000110, o_b_iod_7seg_tens =7'b0000110, o_b_iod_7seg_units =7'b1100110, | pass |
| 7 | Hexpad | i_b_iod_hex_overflow=1 | //display 'E' | pass |

| | | | | |
|---|-----------------|--|--|------|
| | overflow | //Wait for 2 clock cycle i_b_iod_hex_overflow=0 | o_b_iod_7seg_flags=7'b1111001, o_b_iod_7seg_hundreds=7'b0111111, o_iod_7seg_tens = 7'b0111111, o_iod_7seg_units = 7'b0111111 | |
| 8 | Overflow | i_b_iod_overflow = 1 //Wait for 2 clock cycle i_b_iod_overflow = 0 | //display 'E' o_b_iod_7seg_flags=7'b1111001, o_b_iod_7seg_hundreds=7'b0111111, o_iod_7seg_tens = 7'b0111111, o_iod_7seg_units = 7'b0111111 | pass |

4.6.10 TestBench

```

////////////////////////////////////
//COMPANY:UTAR
//ENGINEER:CHONG BING HONG
//CREATE DATE: 07/05/2025
//MODULE NAME:tb_iod
//PROJECT NAME:tb_iod
////////////////////////////////////

```

```
`define PERIOD_CLK 10
```

```
module tb_iod();
```

```

logic tb_system_clk;
logic tb_system_reset;
logic tb_b_iod_overflow;
logic tb_b_iod_neg;
logic tb_b_iod_hex_overflow;
logic [7:0] tb_b_iod_a;
logic [7:0] tb_b_iod_b;
logic [7:0] tb_b_iod_data;
logic [7:0] tb_b_iod_cout;
logic [3:0] tb_b_iod_opcode;
logic [6:0] tb_b_iod_7seg_hundreds;
logic [6:0] tb_b_iod_7seg_tens;
logic [6:0] tb_b_iod_7seg_units;
logic [6:0] tb_b_iod_7seg_flags;

```

```
iod
```

```
dut_iod
```

```
(
```

```

.i_system_clk(tb_system_clk),
.i_system_reset(tb_system_reset),
.i_b_iod_overflow(tb_b_iod_overflow),
.i_b_iod_neg(tb_b_iod_neg),
.i_b_iod_hex_overflow(tb_b_iod_hex_overflow),
.i_b_iod_a(tb_b_iod_a),
.i_b_iod_b(tb_b_iod_b),
.i_b_iod_data(tb_b_iod_data),
.i_b_iod_cout(tb_b_iod_cout),
.i_b_iod_opcode(tb_b_iod_opcode),
.o_b_iod_7seg_hundreds(tb_b_iod_7seg_hundreds), .o_b_iod_7seg_tens(tb_b_iod_7
seg_tens),
.o_b_iod_7seg_units(tb_b_iod_7seg_units),

```

```

.o_b_iod_7seg_flags(tb_b_iod_7seg_flags)
);

initial tb_system_clk=0;
always #(`PERIOD_CLK) tb_system_clk <= ~tb_system_clk;

initial begin
//default tb_system_reset = 0;
tb_b_iod_overflow = 0;
tb_b_iod_neg = 0;
tb_b_iod_hex_overflow=0;
tb_b_iod_a=8'b00000000;
tb_b_iod_b=8'b00000000;
tb_b_iod_data=8'b00000000;
tb_b_iod_cout=8'b00000000;
tb_b_iod_opcode=4'b0000;
tb_b_iod_7seg_hundreds=7'b0000000;
tb_b_iod_7seg_tens=7'b0000000;
tb_b_iod_7seg_units=7'b0000000;
tb_b_iod_7seg_flags=7'b0000000;

//testcase1, reset
tb_system_reset = 1;
#(`PERIOD_CLK * 4);
tb_system_reset = 0;
#(`PERIOD_CLK * 5);

//testcase2, A=(110)
tb_b_iod_opcode = 4'b1111;
tb_b_iod_a=8'b01101110;
#(`PERIOD_CLK * 10);
tb_b_iod_a=8'b00000000;

//testcase3, B=(28)
tb_b_iod_opcode = 4'b1110;
tb_b_iod_b=8'b00011100;
#(`PERIOD_CLK * 10);
tb_b_iod_b=8'b00000000;

//testcase4, ALU result(125), opcode(-)
tb_b_iod_opcode = 4'b0010;
tb_b_iod_cout= 8'b1111101;
#(`PERIOD_CLK * 10);
tb_b_iod_opcode = 4'b0000;
tb_b_iod_cout= 8'b00000000;

//testcase5, shift result(114),opcode=(<<)
tb_b_iod_opcode =4'b1001;
tb_b_iod_data= 8'b1110010;
#(`PERIOD_CLK * 10);
tb_b_iod_opcode = 4'b0000;
tb_b_iod_data= 8'b00000000;

//testcase6, neg(1),ALU result(50),opcode(-)

tb_b_iod_neg =1;
tb_b_iod_opcode = 4'b0010;

```

```

tb_b_iod_cout= 8'b00110010;
#(`PERIOD_CLK * 2);
tb_b_iod_neg =0;
tb_b_iod_opcode = 4'b0000;
tb_b_iod_cout= 8'b00000000;

```

```

//testcase7, overflow
tb_b_iod_hex_overflow = 1;
#(`PERIOD_CLK * 2);
tb_b_iod_hex_overflow = 0;

```

```

//testcase8, ALU overflow
tb_b_iod_overflow = 1;
#(`PERIOD_CLK * 2);
tb_b_iod_overflow = 0;

```

```

//End simulation
#(`PERIOD_CLK*100);
$finish;
end
endmodule


```

4.6.11 Test Result Timing Diagram

```

//testcase1, reset


```

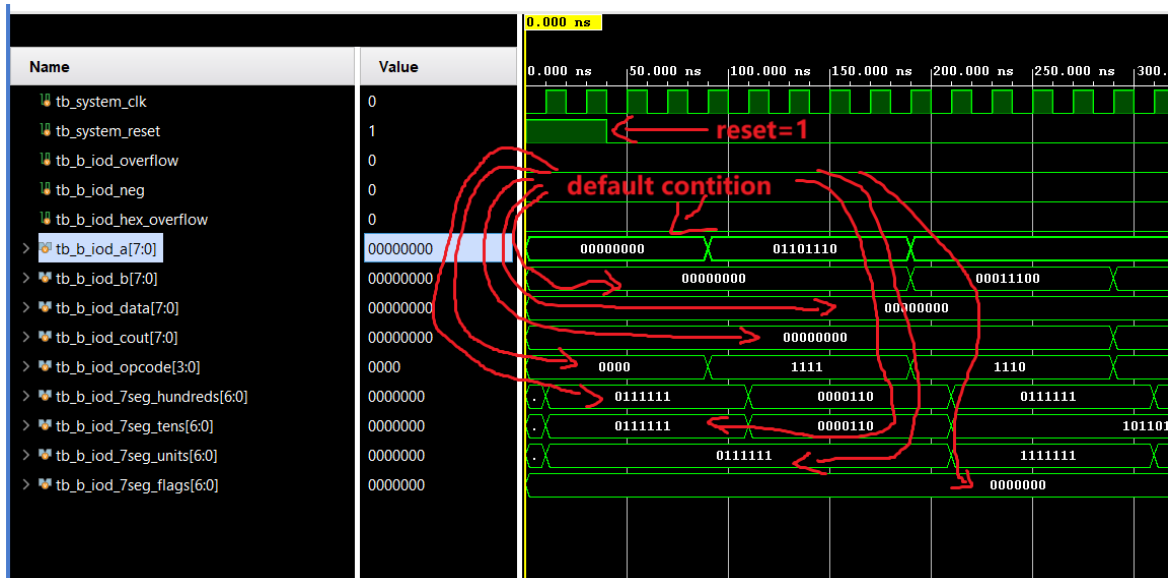


```

//testcase2, A=(110)


```

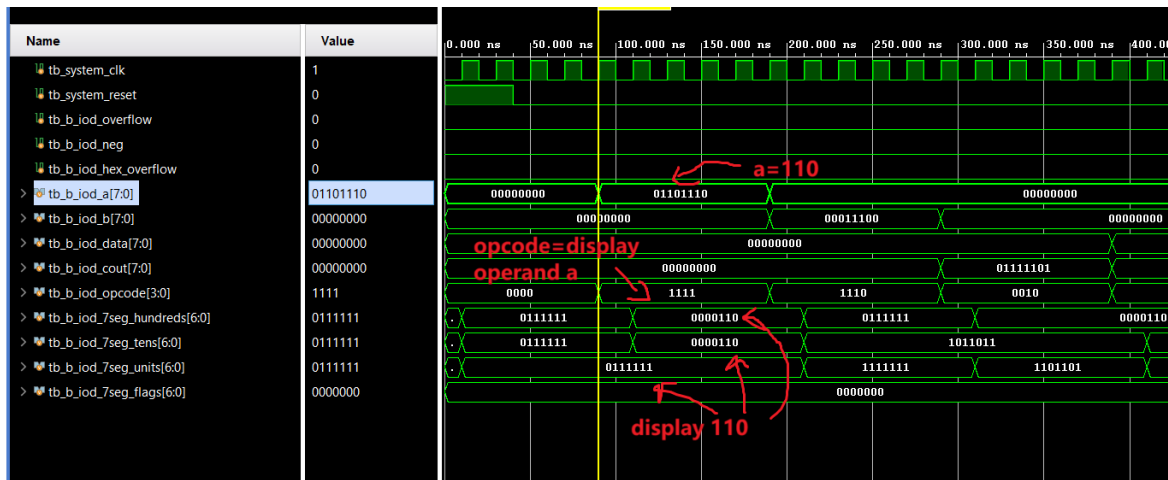


//testcase3, B=(28)

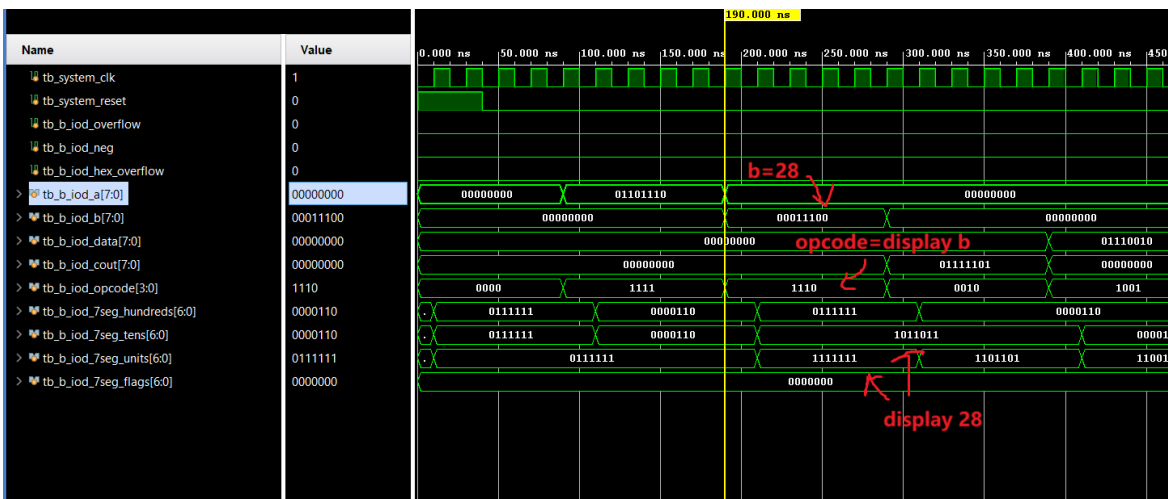


//testcase4, ALU result(125), opcode(-)

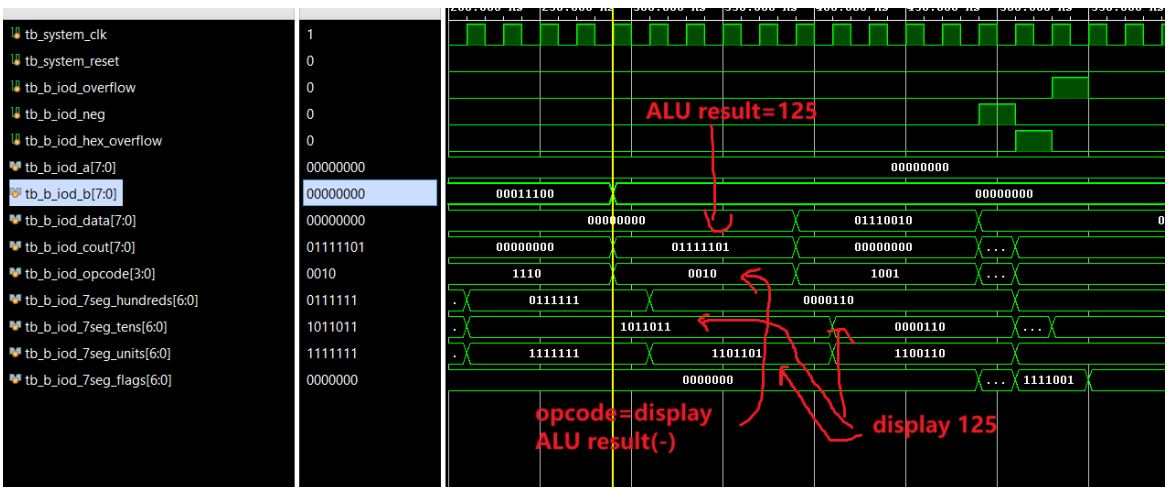

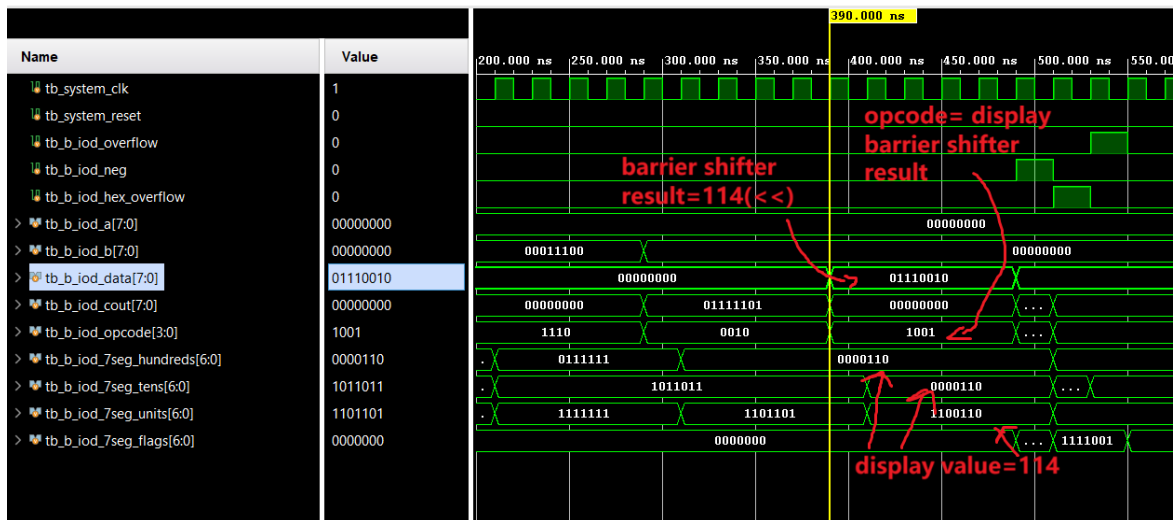
//testcase5, shift result(114),opcode=(<<)



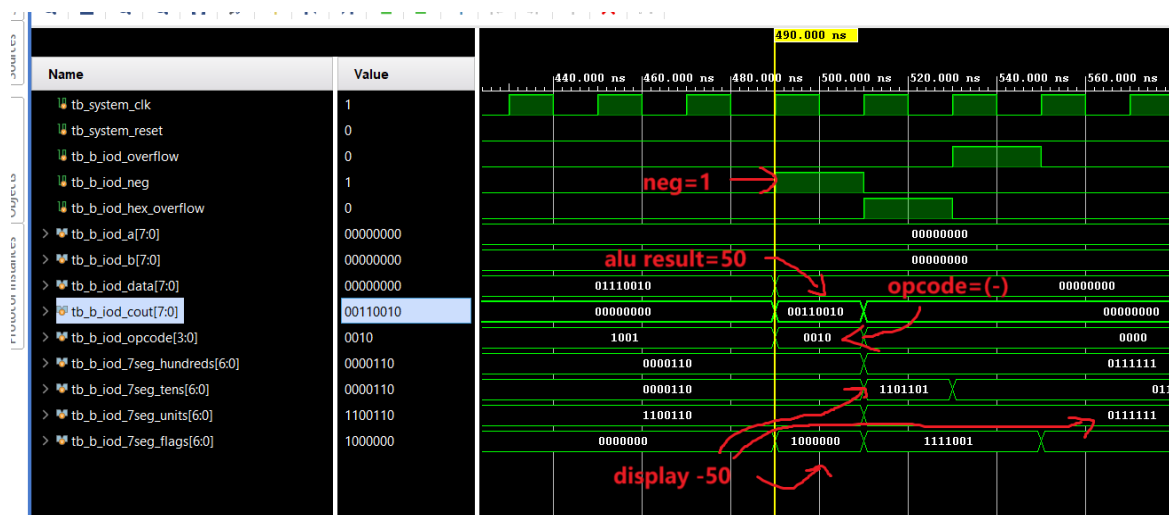//testcase6, neg(1),ALU result(50),opcode(-)



//testcase7, overflow

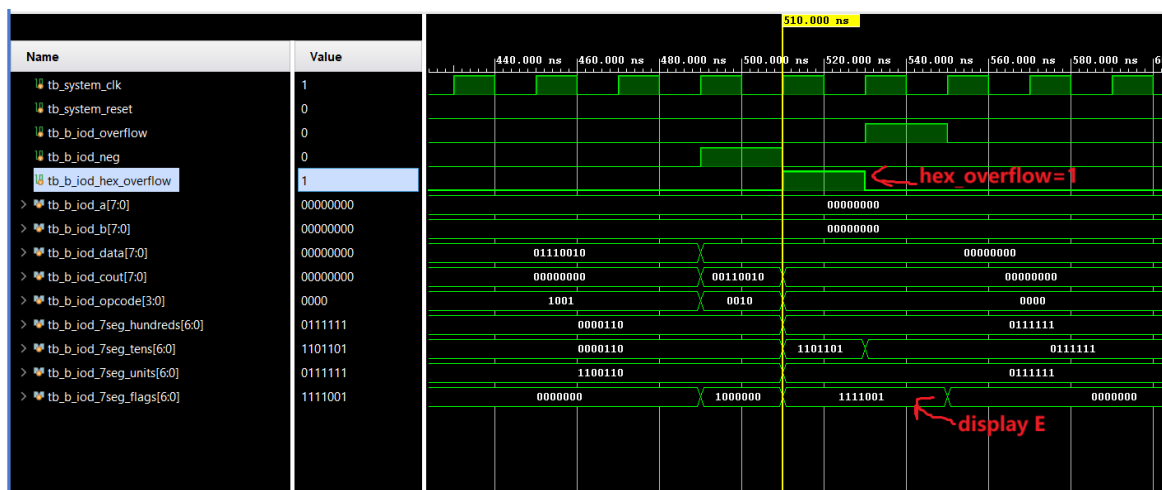

//testcase8, ALU overflow

